
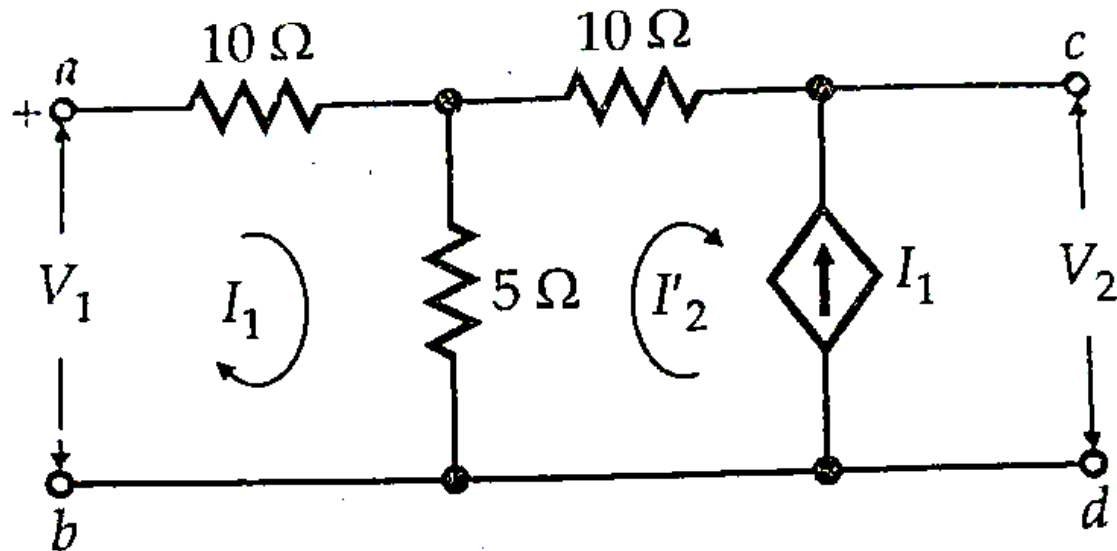


Determine the Z parameters of the network

PROBLEM 1

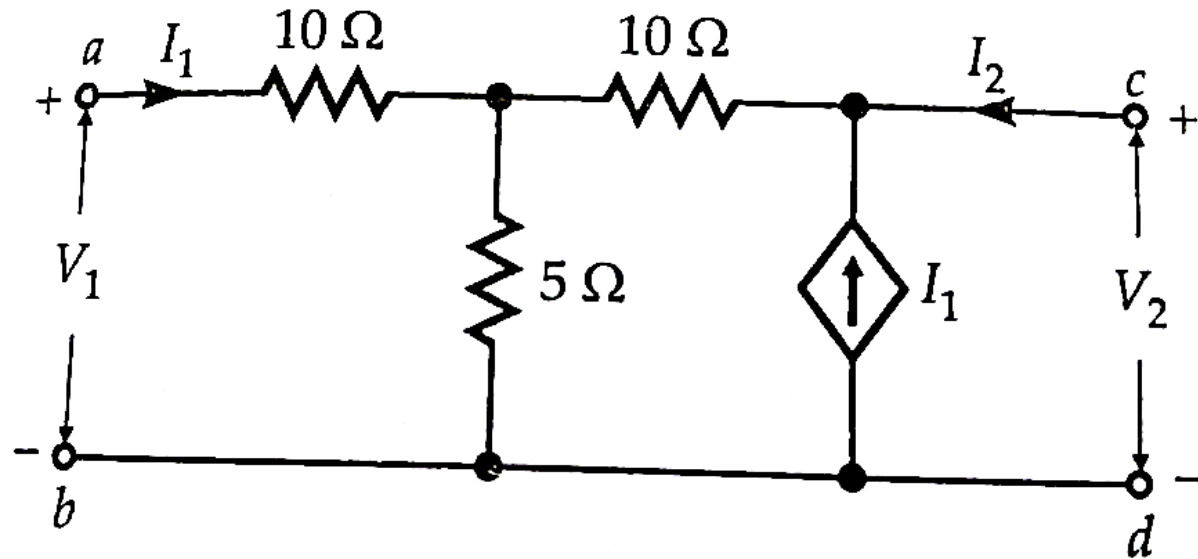


(a b) \rightarrow Input port (i/p)
(c d) \rightarrow output port (o/p)

Apply V_1 in the (i/p) port
o/p port is open

Assume loop current as shown

$$\therefore V_1 = 10I_1 + 5I_1 - 5I_2'$$
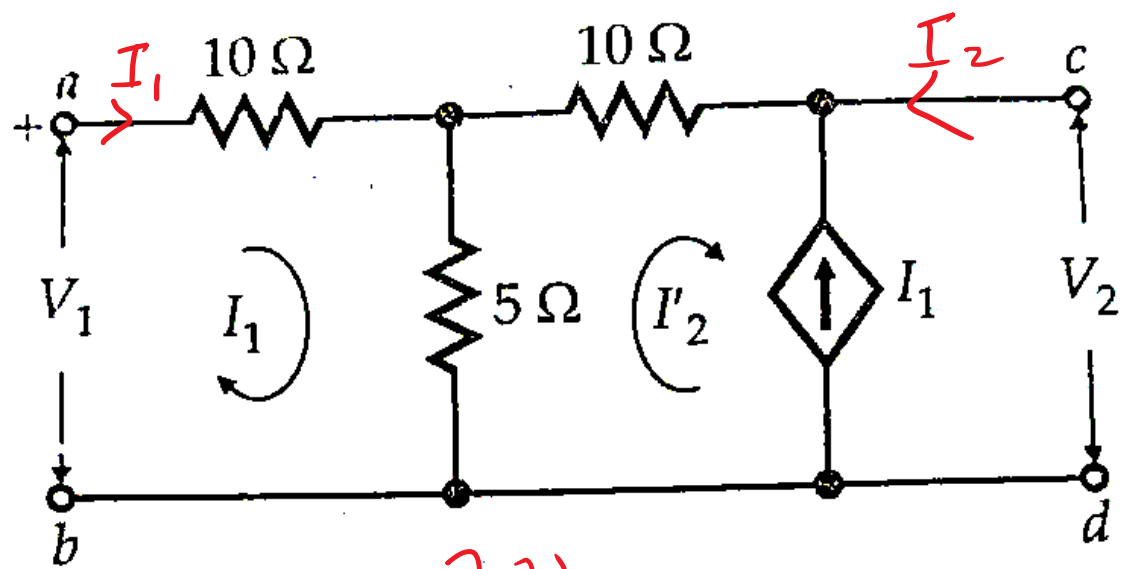
$$V_1 = 15I_1 - 5I_2' \rightarrow \textcircled{1}$$



find V_{th} & Z_{th}

$$V_1 = 15I_1 - 5I_2' \rightarrow \textcircled{1}$$

Since (c,d) is open, $I_2 = 0$

See the dependent source in the figure, I_1 is opposite to $-I_2'$

$$\boxed{\therefore -I_2' = I_1} \quad (\text{Note } I_2 = 0)$$

$\rightarrow \textcircled{2}$

Using $\textcircled{2}$ in $\textcircled{1} \Rightarrow V_1 = 15I_1 + 5I_1 = 20I_1$

$$V_1 = 20I_1 \rightarrow \textcircled{3}$$

$$\text{From } \textcircled{3} \Rightarrow \left(\frac{V_1}{I_1} \right)_{I_2=0} = Z_{11} = 10 \Omega$$

$$\text{From eqn } \textcircled{2} \Rightarrow I_2' = -I_1$$


$$\text{From eqn } \textcircled{3} \Rightarrow I_1 = \frac{V_1}{20} \text{ (A)}$$

$$\therefore \boxed{I_2' = -\frac{V_1}{20} \text{ (A)}}$$

A \rightarrow Ampere.

$$-I_1 = -\frac{V_1}{20}$$

$$I_1 = V_1/20$$

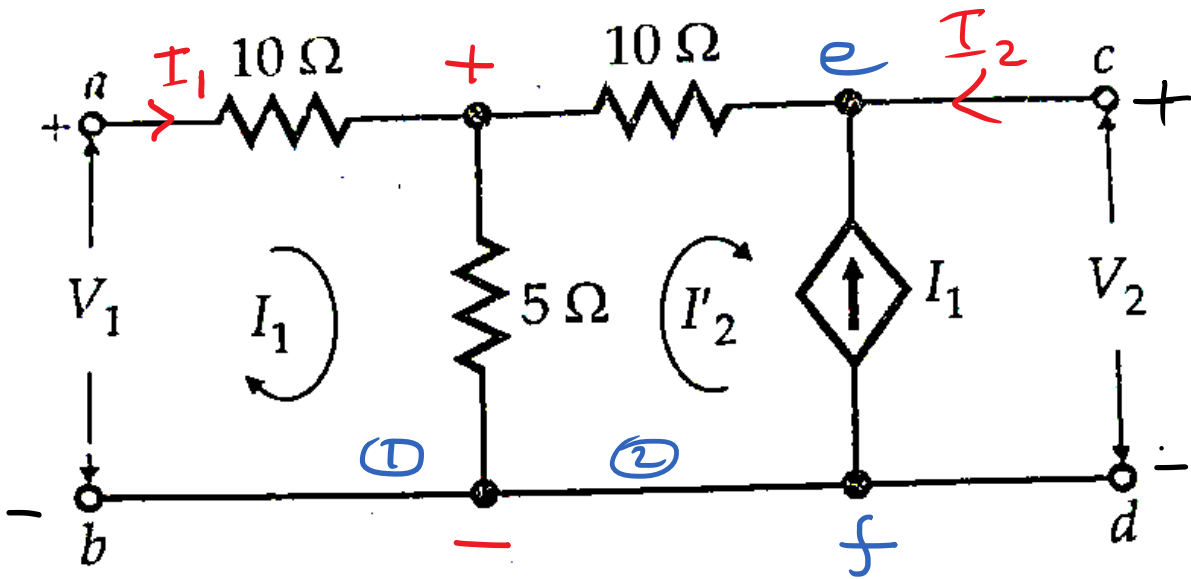

Since (c-d) is open $I_2 = 0$

Here $I'_2 = -I_1$ and voltage between e & d = V_2

$V_2 =$ Voltage drop across 5Ω
+ Voltage drop across 10Ω
in loop ②


$$V_2 = 5I_1 - 5I'_2 - 10I'_2$$

$$= 5I_1 + 5I_1 + 10I_1 = 20I_1$$

$$V_2 = 20I_1 \text{ and } I_1 = \frac{V_2}{20} \text{ (A)}$$


$$\left(\frac{V_2}{I_1} \right)_{I_1=0} = Z_{21}$$

$$= \frac{V_2}{V_2/20} = 20\Omega$$

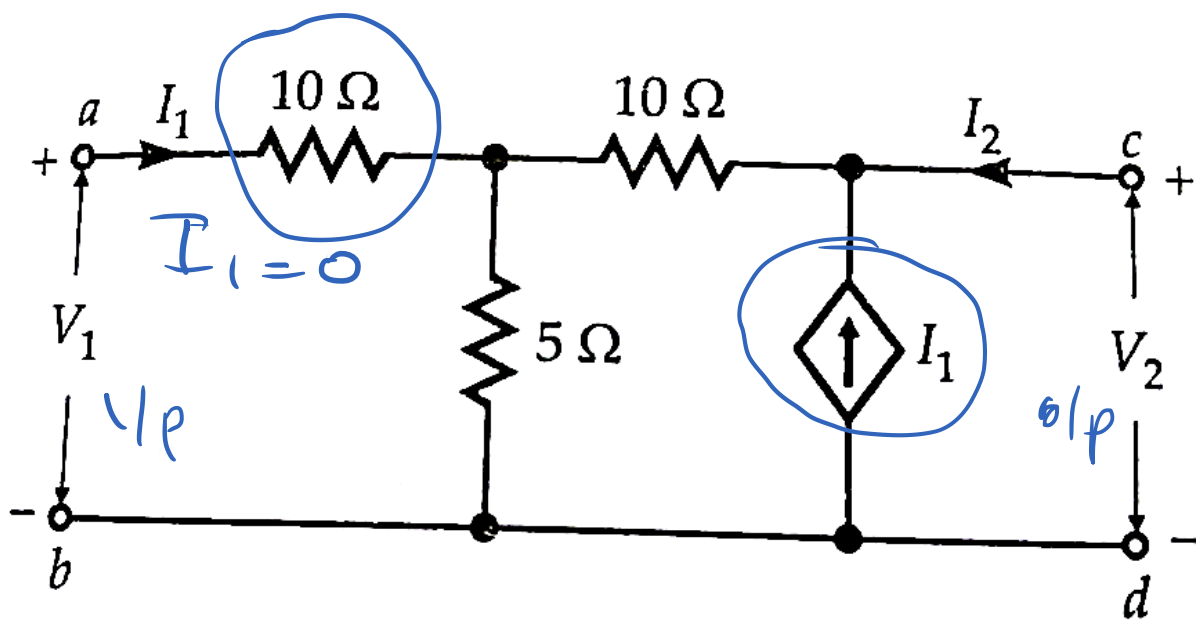


To find Z_{22} and Z_{12}
 i/p is open ; $\therefore I_1 = 0$
 V_2 is applied between c & d
 Since $I_1 = 0$; the dependent current source is useless

Thus the circuit can be redrawn

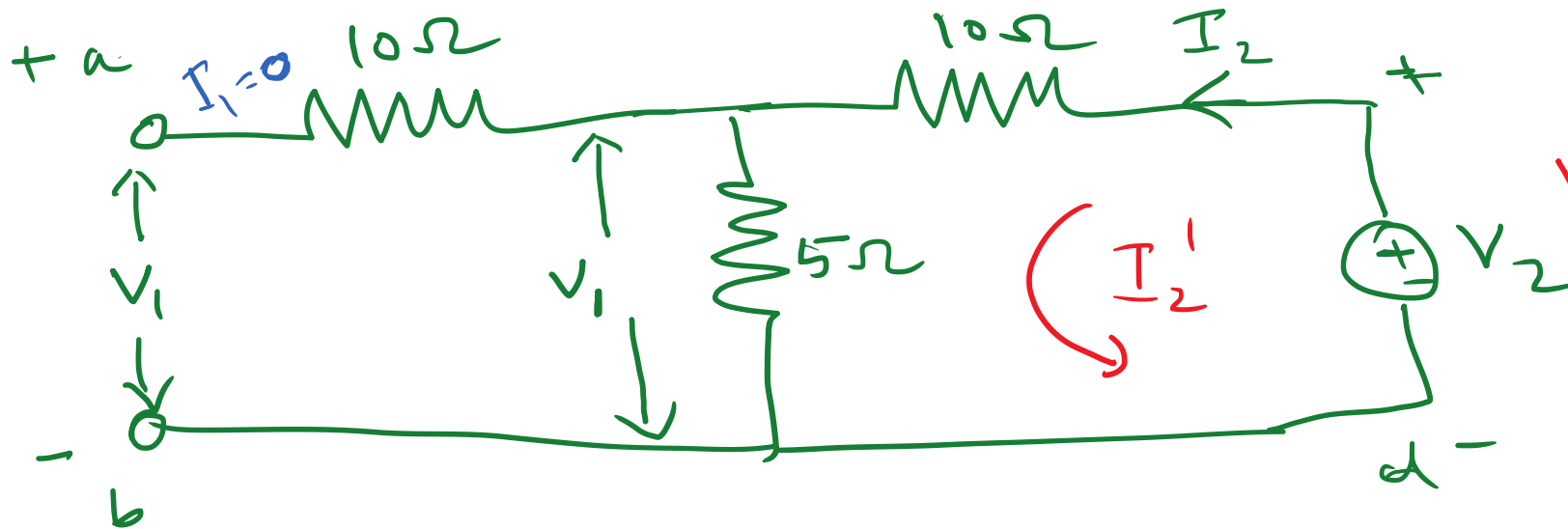

Here $I_2 = I_2'$
 $V_2 = (10 + 5) I_2$
 $= 15 I_2$
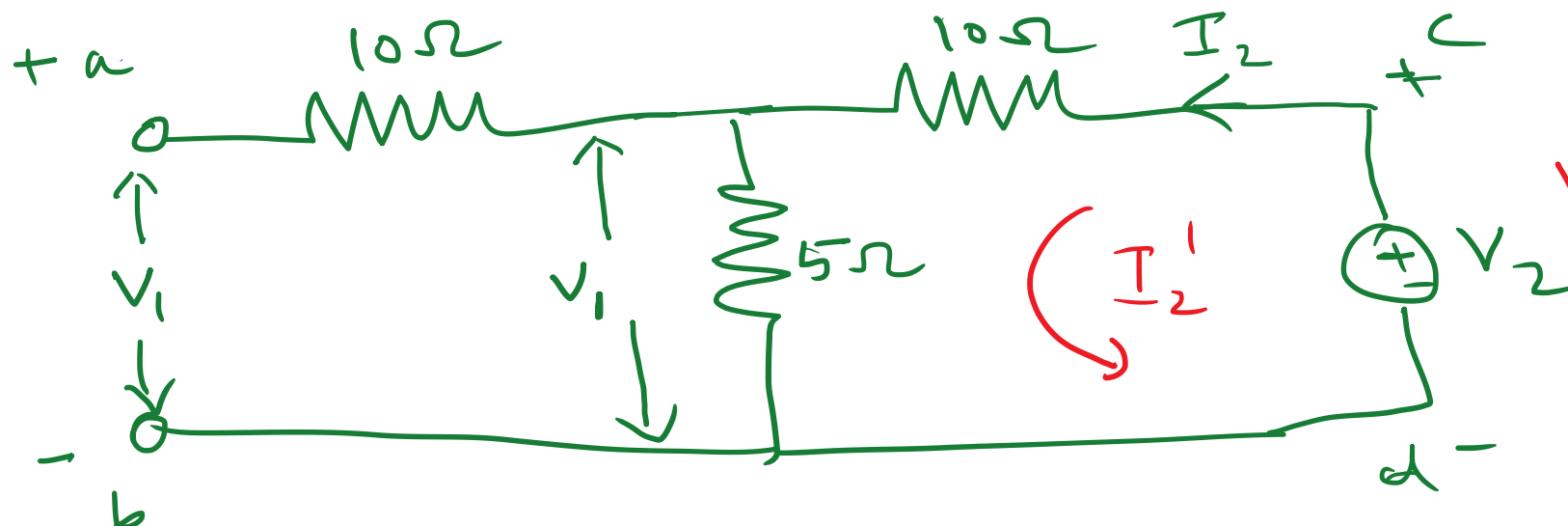
$$Z_c = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 20\Omega & 5\Omega \\ 20\Omega & 15\Omega \end{bmatrix}$$



Here $I_2 = I_2'$

$$V_2 = (10 + 5) I_2$$

$$= 15 I_2 \text{ (V)}$$

V_1 is the voltage drop across 5Ω resistance

$$\therefore V_1 = 5 I_2$$


$$Z_{12} = \left(\frac{V_1}{I_2} \right)_{I_1=0}$$

$$= \frac{5 I_2}{I_2} = 5\Omega$$

$$Z_{22} = \left(\frac{V_2}{I_2} \right)_{I_1=0}$$

$$= \frac{15 I_2}{I_2} = 15\Omega$$

PROBLEM 2

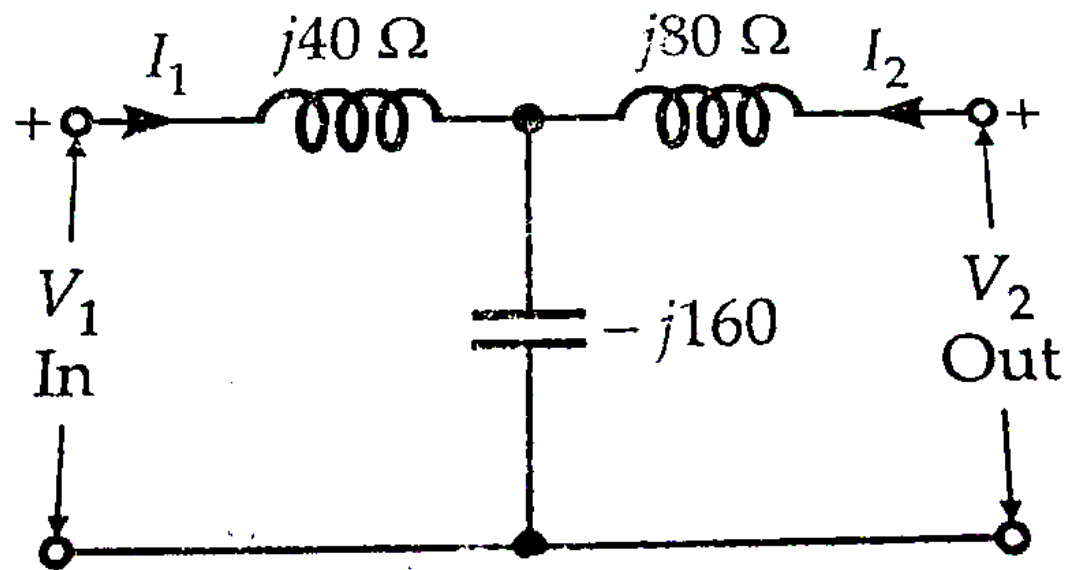


Find the open circuit parameters of the circuit (Z parameters)

Since $I_2 = 0$; $j80$ is excluded

$$V_1 = I_1 (j40 + -j160) \\ = I_1 j(40 - 160) \text{ V}$$


Z_{11} and Z_{22}

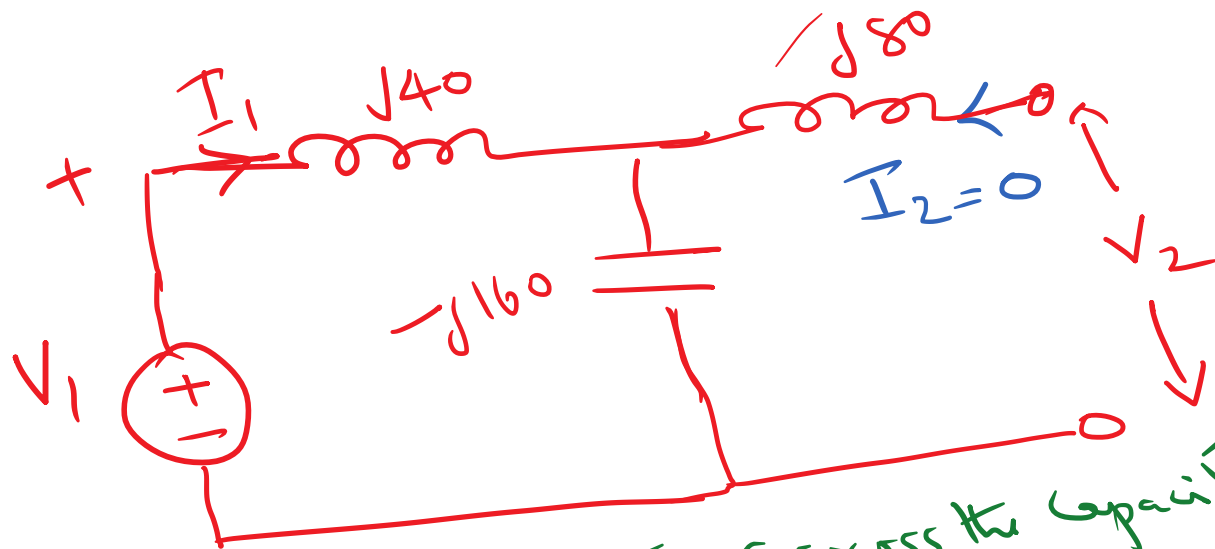

Since $I_2 = 0$; V_2 is the voltage across the capacitor
 $V_2 = I_1 (-j160) \text{ V}$

$$Z_{11} = \left(\frac{V_1}{I_1} \right)_{I_2=0}$$
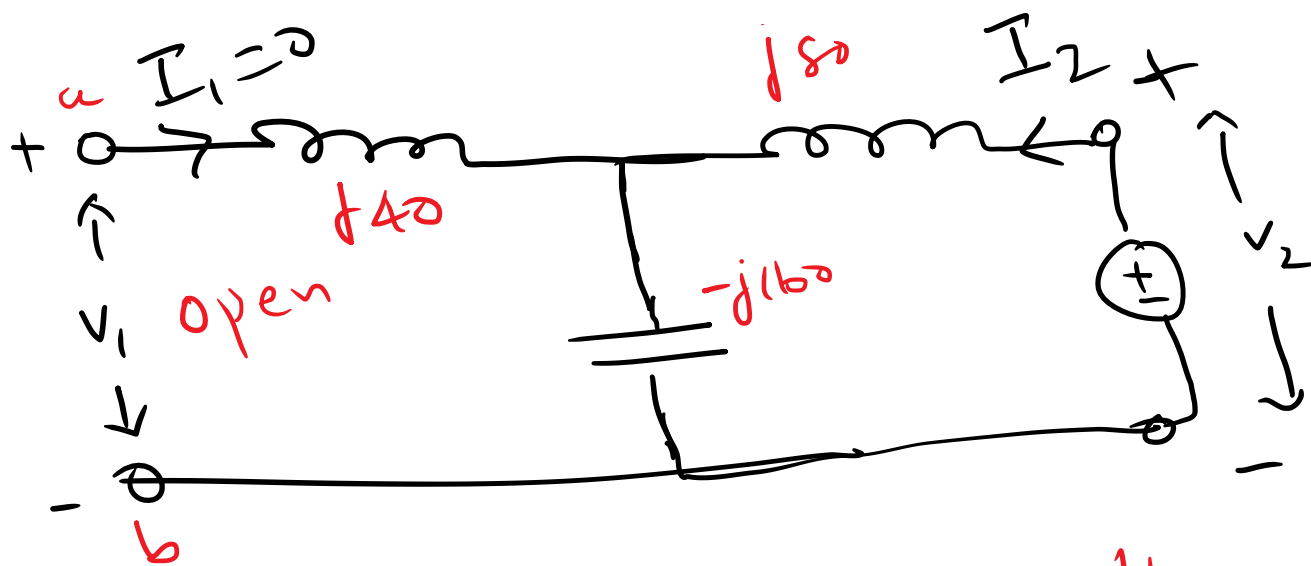
$$Z_{22} = \left(\frac{V_2}{I_1} \right)_{I_2=0}$$



To find Z_{22} & Z_{12}

Since (a,b) is open, $I_1 = 0$
 $\therefore j40$ is excluded.

Also the voltage V_1 is
 the voltage across the capacitor.

$$\begin{aligned}
 V_2 &= I_2 (j80 + -j160) \\
 &= I_2 (j80 - j160) \text{ V} \\
 V_2 &= I_2 j(80 - 160) \text{ V} \\
 \underline{\underline{V_2 &= I_2 (-j80)}} \\
 \underline{\underline{V_1 &= I_2 (-j160)}}
 \end{aligned}$$

$$Z_{22} = \left(\frac{V_2}{I_2} \right)_{I_1=0}$$

$$Z_{12} = \left(\frac{V_1}{I_2} \right)_{I_1=0}$$

Finally $Z = \begin{bmatrix} -j120 \Omega & -j160 \Omega \\ -j160 \Omega & -j80 \Omega \end{bmatrix}$