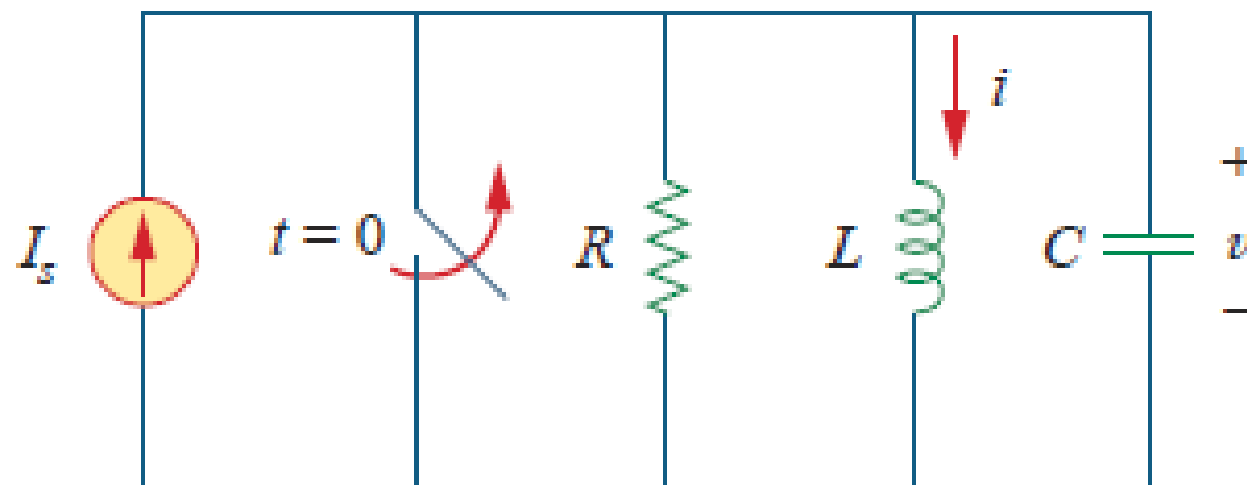


Step Response of a Parallel RLC Circuit



Consider the parallel RLC circuit shown in Fig. We want to find i due to a sudden application of a dc current. Applying KCL at the top node for $t > 0$,

$$\frac{v}{R} + i + C \frac{dv}{dt} = I_s$$

$$v = L \frac{di}{dt}$$

Substituting for v in Eq.

$$\frac{d^2 i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{i}{LC} = \frac{I_s}{LC}$$

The complete solution to Eq. consists of the transient response $i_t(t)$ and the steady-state response i_{ss} ; that is,

$$i(t) = i_t(t) + i_{ss}(t)$$

The steady-state response is the final value of i , *the final value of the current through the inductor is the same as the source current I_s*

The steady-state response is the final value of i , *the final value of the current through the inductor is the same as the source current I_s*

$$i(t) = I_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{Overdamped})$$

$$i(t) = I_s + (A_1 + A_2 t) e^{-\alpha t} \quad (\text{Critically damped})$$

$$i(t) = I_s + (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t} \quad (\text{Underdamped})$$

The constants A_1 and A_2 in each case can be determined from the initial conditions for i and di/dt .

