

Tutorial Sheet-1

①


① Find the phasors corresponding to the following signals:

- A.
- ① $v(t) = 21 \cos(4t - 15^\circ) \text{ V}$
 - ② $i(t) = -8 \sin(10t + 70^\circ) \text{ mA}$
 - ③ $v(t) = 120 \sin(10t - 50^\circ) \text{ V}$
 - ④ $i(t) = -60 \cos(30t + 10^\circ) \text{ mA}$

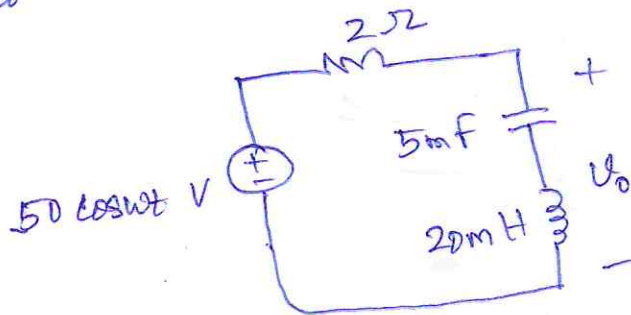
B. Using phasors, find:

- ① $3 \cos(20t + 10^\circ) - 5 \cos(20t - 30^\circ)$
- ② $40 \sin 50t + 30 \cos(50t - 45^\circ)$
- ③ $20 \sin 400t + 10 \cos(400t + 60^\circ) - 5 \sin(400t - 20^\circ)$


② What value of ω will cause the forced response v_o to be zero in the circuit below.



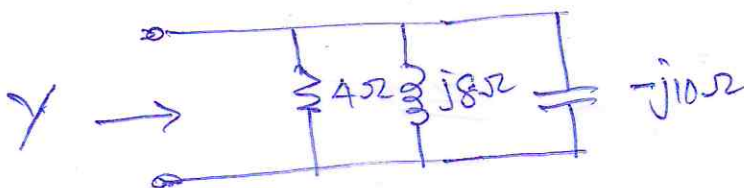
③ Determine the admittance Y for the circuit below.



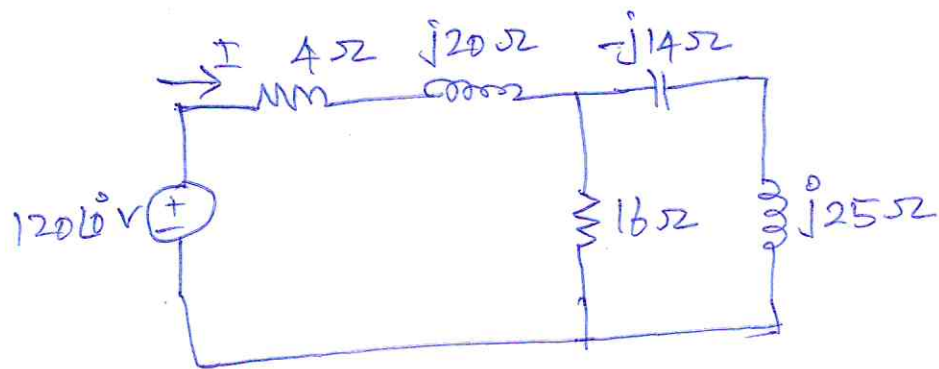
- ④ For the circuit shown below, find Z_{eq} and use that to find current I . Let $\omega = 10 \text{ rad/s}$.




- ⑤ Find I_0 in the circuit below

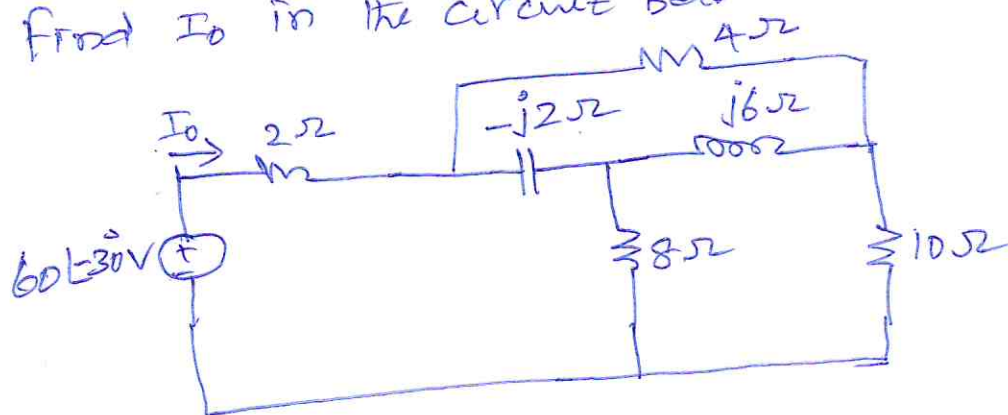

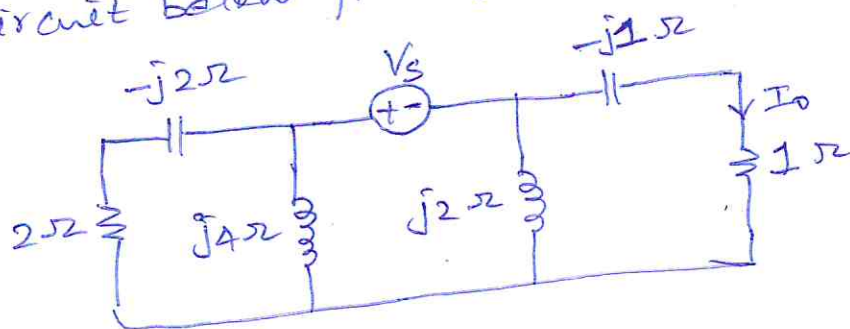- ⑥ In the circuit below find V_s if $I_0 = 2 \angle 0^\circ \text{ A}$.




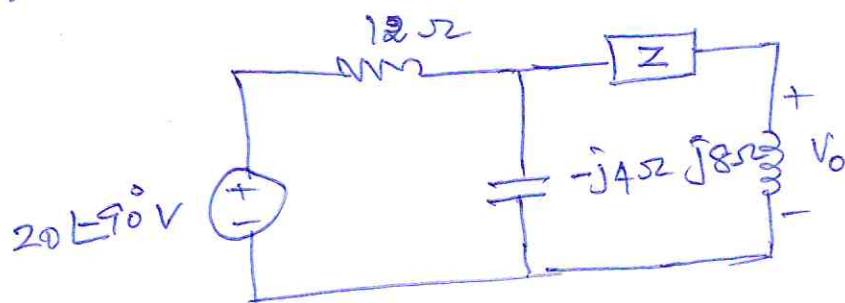- ⑦ Find Z in the network below, given that $V_0 = 4 \angle 0^\circ \text{ V}$.



- 8 A coil with impedance $(8+j6)\Omega$ is connected in series with a capacitive reactance X . The series combination is connected in parallel with a resistor R . Given that the equivalent impedance of the resulting circuit is $5\angle 0^\circ \Omega$. Find the value of R and X .

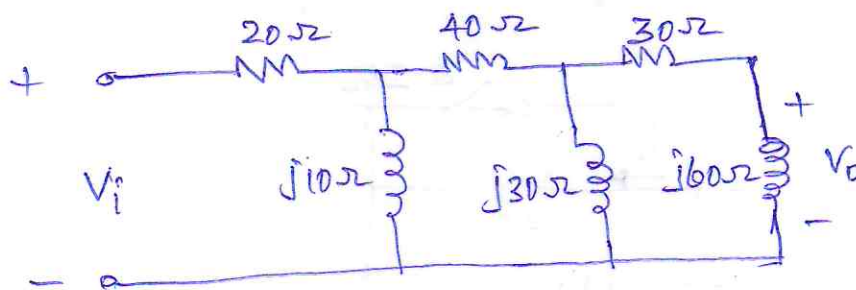- 9 ¹⁰ a Calculate the phase shift of the circuit below.
 b State whether the phase shift is leading or lagging (output with respect to input)
 c Determine the magnitude of the output when the input is 120V.



- 10 The circuit below shows a parallel combination of an inductance and a resistance. If it is desired to connect a capacitor in series with the parallel combination such that the net impedance is negative at 10MHz, what is the required value of C ?

