

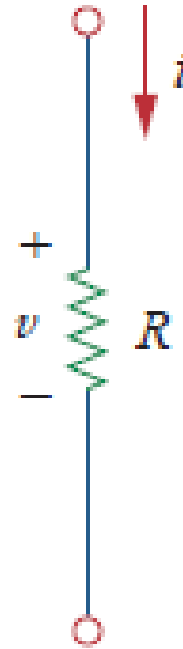


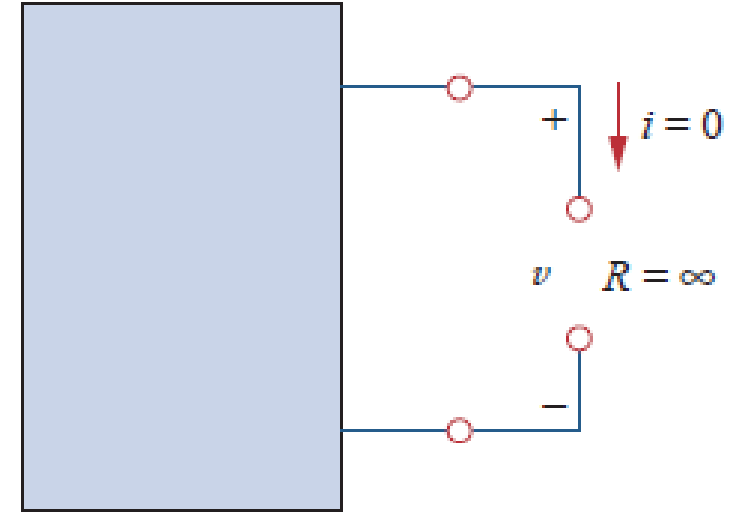To apply Ohm's law, we must pay careful attention to the current direction and voltage polarity.



Open Circuit & Short Circuit

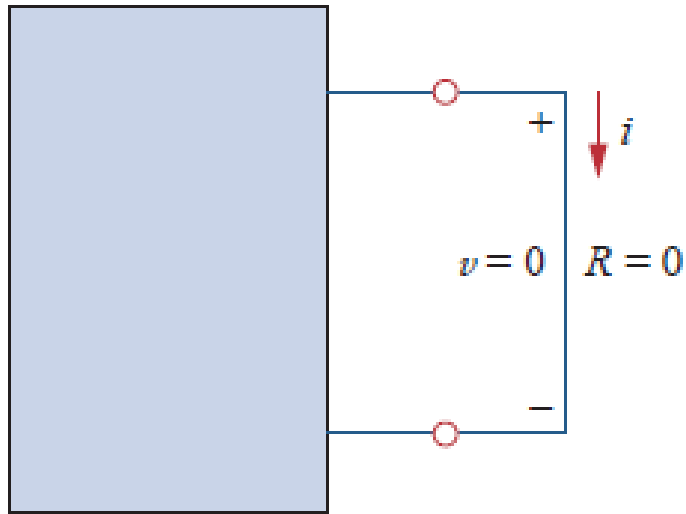

$$v = iR = 0$$

A **short circuit** is a circuit element with resistance approaching zero.

$$i = \lim_{R \rightarrow \infty} \frac{v}{R} = 0$$


An **open circuit** is a circuit element with resistance approaching infinity.

Conductance

Conductance is the ability of an element to conduct electric current; it is measured in mhos (\mathfrak{U}) or siemens (S).

$$G = \frac{1}{R} = \frac{i}{v}$$

Series Resistors and Voltage Division

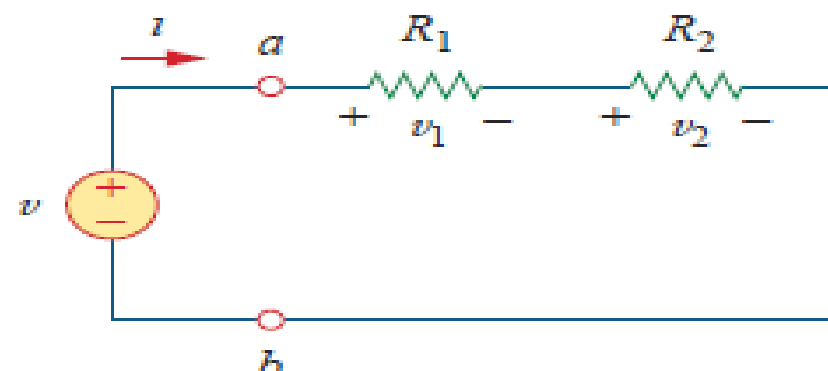

$$v = v_1 + v_2 = i(R_1 + R_2)$$

$$i = \frac{v}{R_1 + R_2}$$


$$v = iR_{\text{eq}} \quad R_{\text{eq}} = R_1 + R_2$$

Ohm's law to each of the resistors, we obtain

$$v_1 = iR_1, \quad v_2 = iR_2$$

KVL to the loop (moving in the clockwise direction)

$$-v + v_1 + v_2 = 0$$

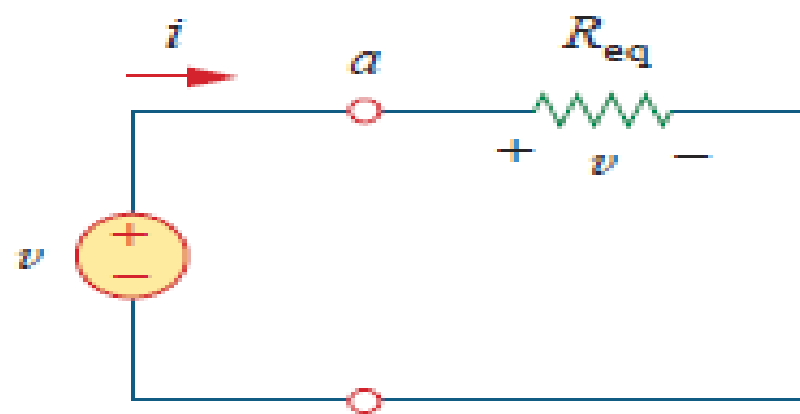

The **equivalent resistance** of any number of resistors connected in series is the sum of the individual resistances.


For N resistors in series then,

$$R_{\text{eq}} = R_1 + R_2 + \cdots + R_N = \sum_{n=1}^N R_n$$

$$v_1 = iR_1,$$

$$v_2 = iR_2$$
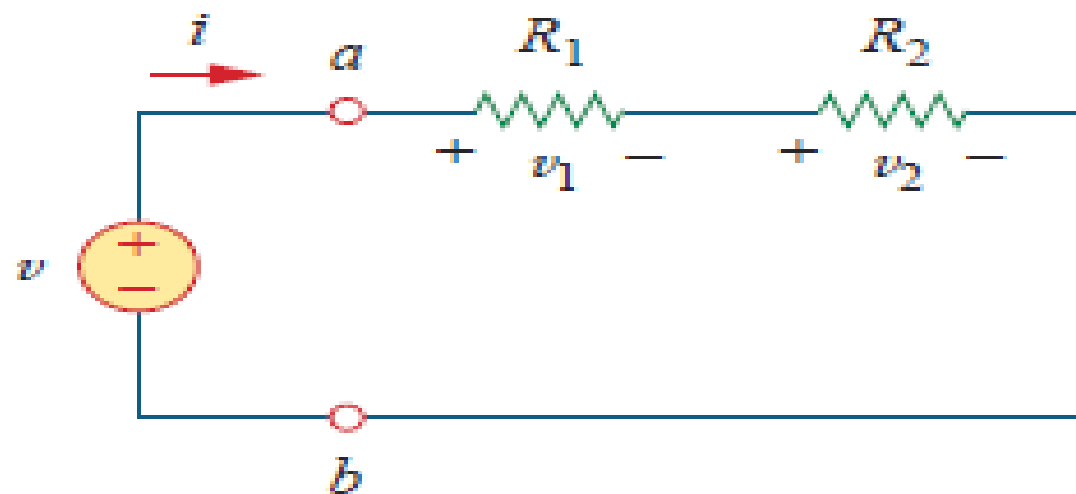
$$v_1 = \frac{R_1}{R_1 + R_2} v, \quad v_2 = \frac{R_2}{R_1 + R_2} v$$



the *principle of voltage division*,
voltage divider.

$$v_n = \frac{R_n}{R_1 + R_2 + \cdots + R_N} v$$

Parallel Resistors and Current Division

$$v = i_1 R_1 = i_2 R_2$$

$$i_1 = \frac{v}{R_1}, \quad i_2 = \frac{v}{R_2}$$


KCL at node a gives the total current i as

$$i = i_1 + i_2$$

$$i = \frac{v}{R_1} + \frac{v}{R_2} = v \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{v}{R_{\text{eq}}}$$


$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2}$$
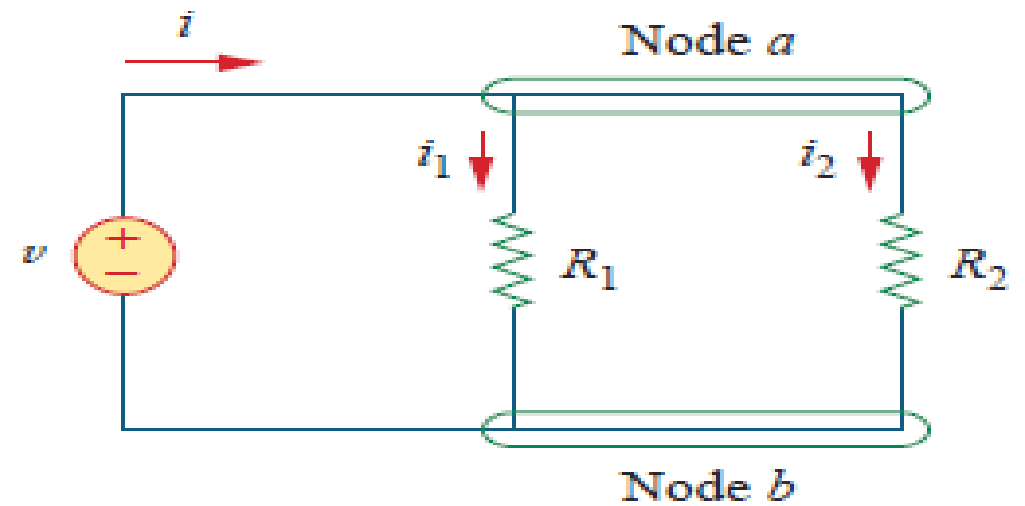
$$\frac{1}{R_{\text{eq}}} = \frac{R_1 + R_2}{R_1 R_2}$$



$$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2}$$

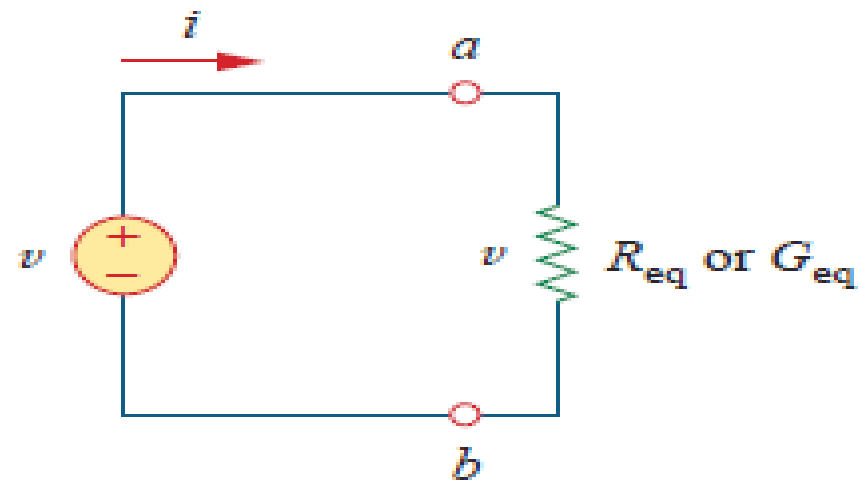The **equivalent resistance** of two parallel resistors is equal to the product of their resistances divided by their sum.



$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \cdots + \frac{1}{R_N}$$

$$G_{eq} = G_1 + G_2 + G_3 + \cdots + G_N$$

The **equivalent conductance** of resistors connected in parallel is the sum of their individual conductances.

equivalent conductance G_{eq} of N resistors in series

$$\frac{1}{G_{eq}} = \frac{1}{G_1} + \frac{1}{G_2} + \frac{1}{G_3} + \cdots + \frac{1}{G_N}$$

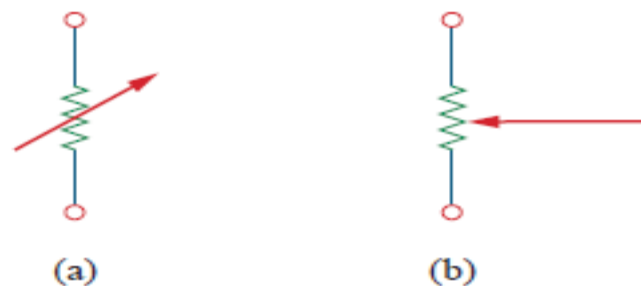


Figure 2.4

Circuit symbol for: (a) a variable resistor in general, (b) a potentiometer.

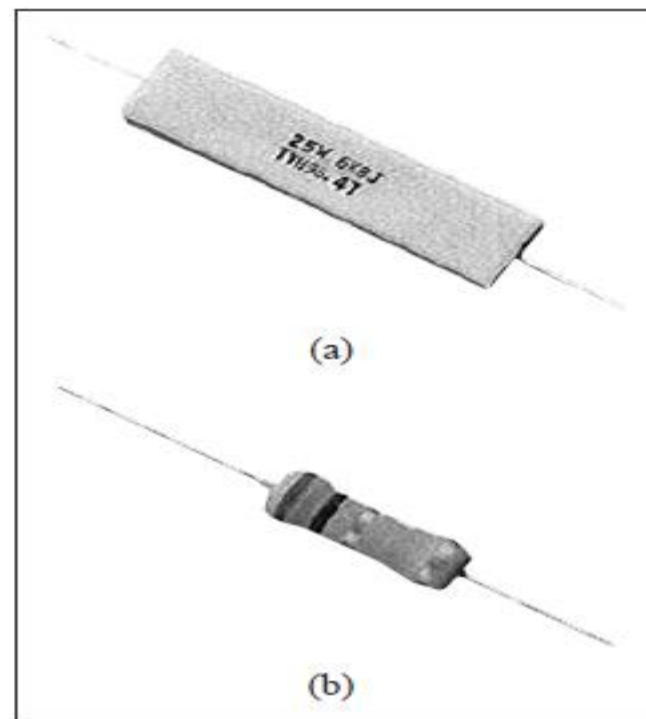


Figure 2.3

Fixed resistors: (a) wirewound type, (b) carbon film type.
Courtesy of Tech America.



Figure 2.5

Variable resistors: (a) composition type, (b) slider pot.
Courtesy of Tech America.

$$G = \frac{1}{R} = \frac{i}{v}$$

$$1 \text{ S} = 1 \text{ } \mathfrak{U} = 1 \text{ A/V}$$


Conductance is the ability of an element to conduct electric current; it is measured in mhos (\mathfrak{U}) or siemens (S).

$$i = Gv$$


$$p = vi = i^2 R = \frac{v^2}{R}$$



$$p = vi = v^2 G = \frac{i^2}{G}$$

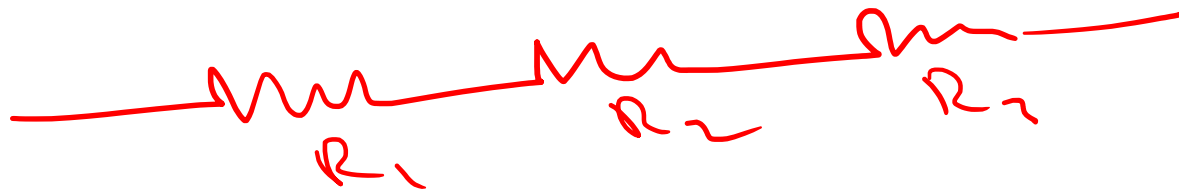1. The power dissipated in a resistor is a nonlinear function of either current or voltage.
2. Since R and G are positive quantities, the power dissipated in a resistor is always positive. Thus, a resistor always absorbs power from the circuit. This confirms the idea that a resistor is a passive element, incapable of generating energy.








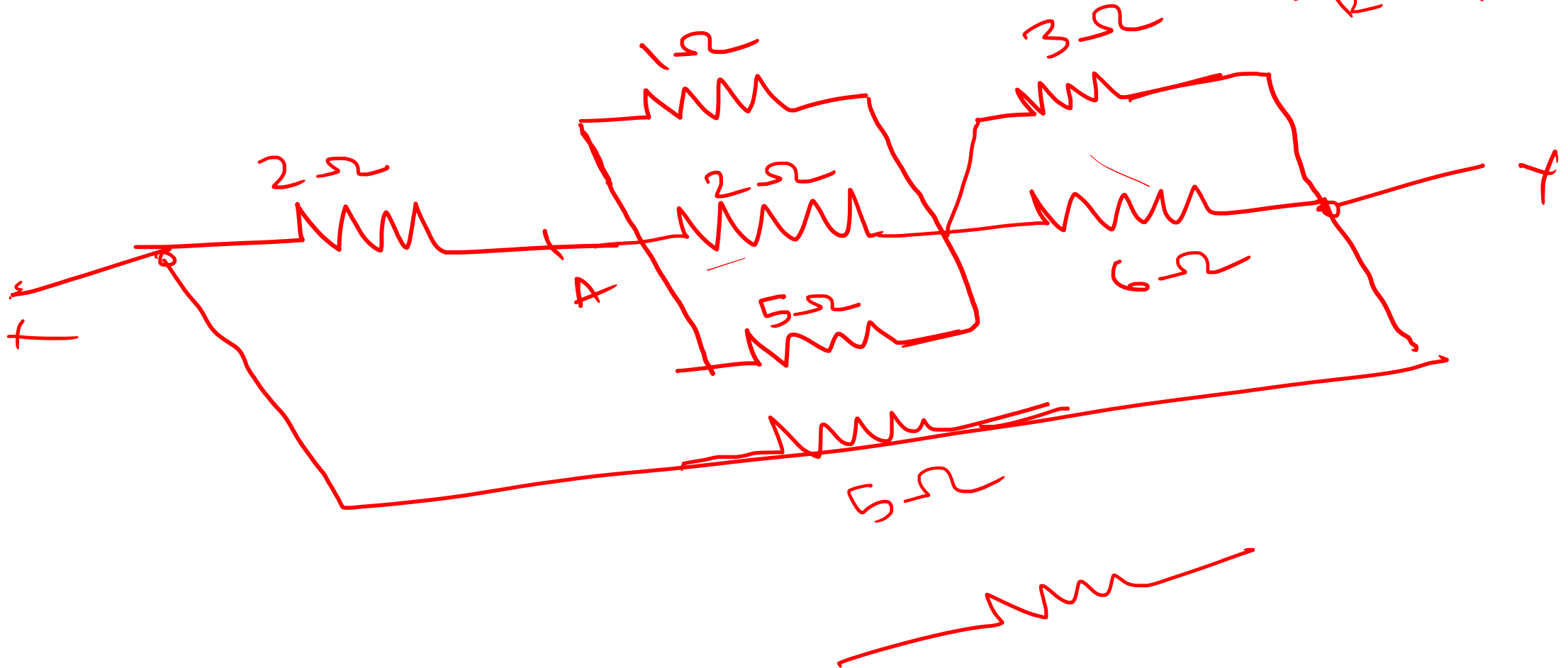
$$R_1 + R_2 + R_3$$
$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$



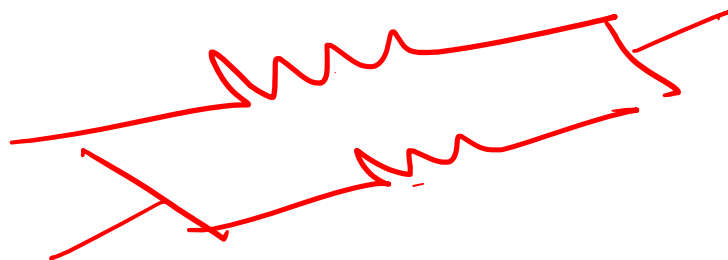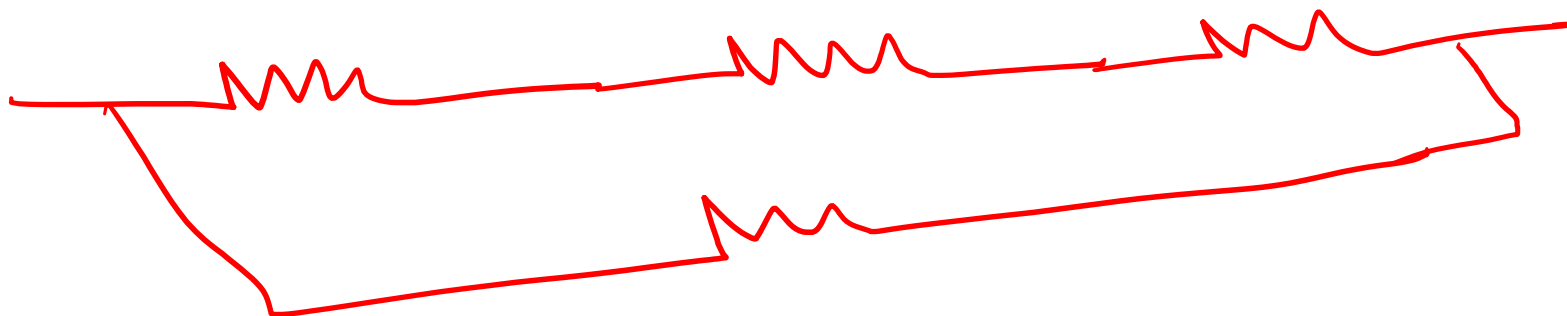


2.39 Ω

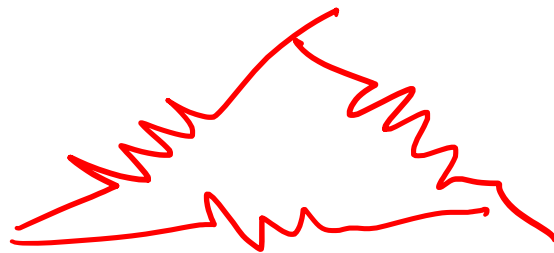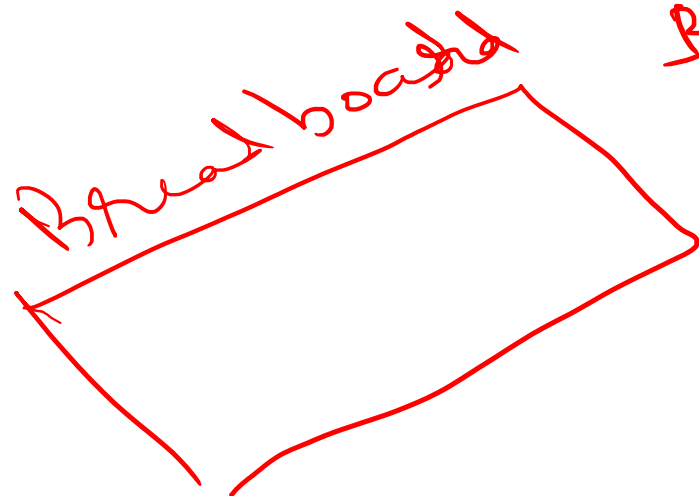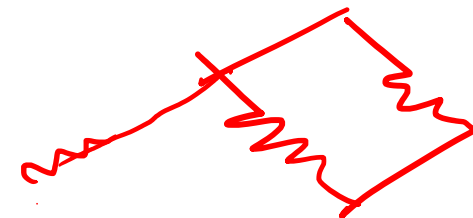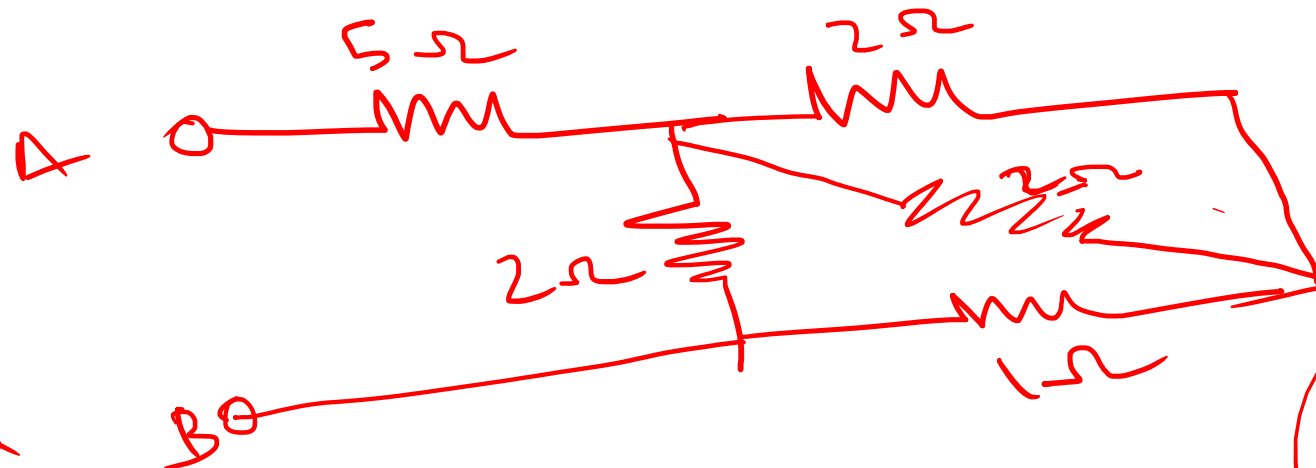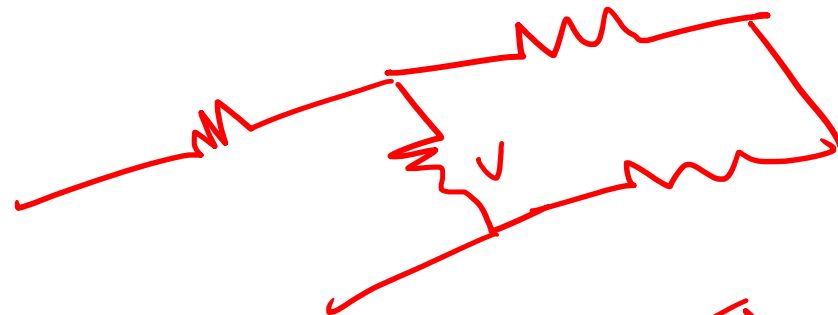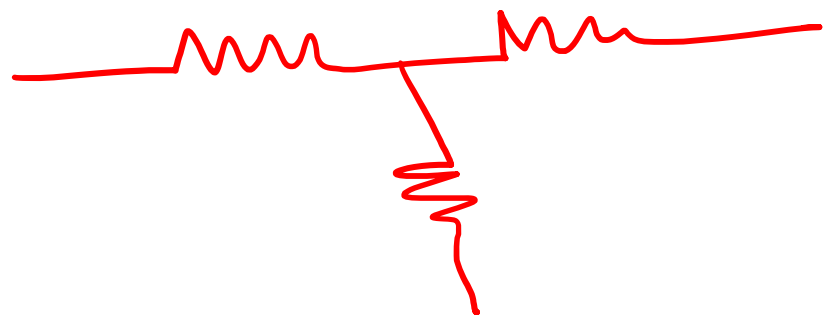

6Ω

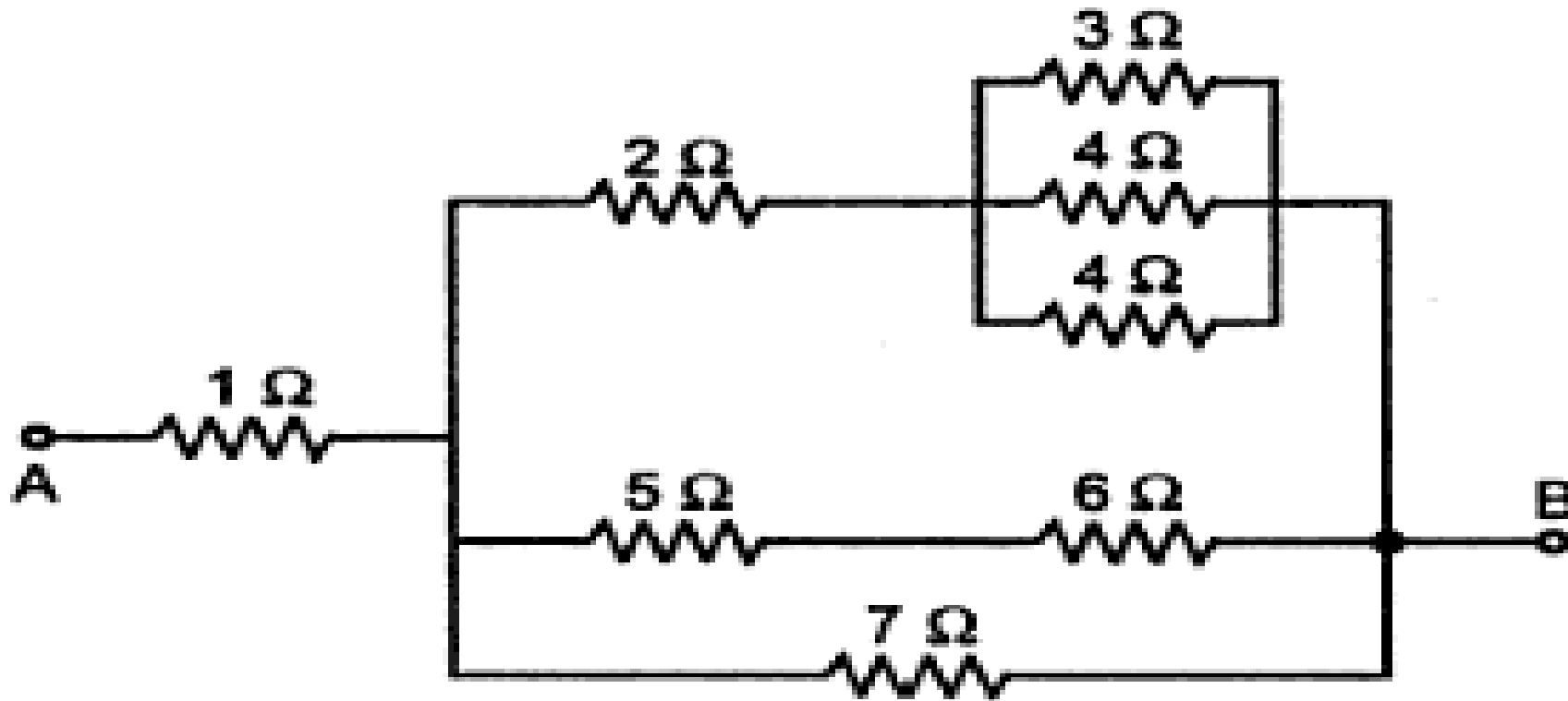
Find the equivalent resistance between the two points A & B



**Find the equivalent resistance between the two
points A & B**

Ans : 2.8 Ohms

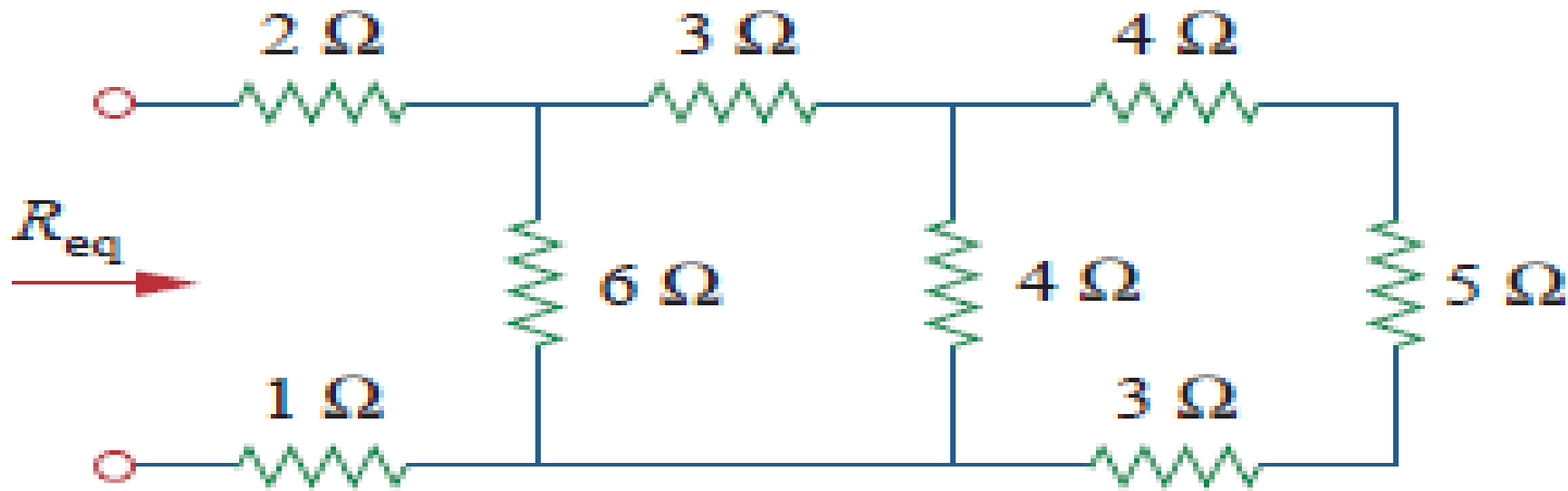
Find the equivalent resistance for the circuit shown in figure




**Find the equivalent resistance for the circuit shown
in figure**

Ans: 6 Ohms

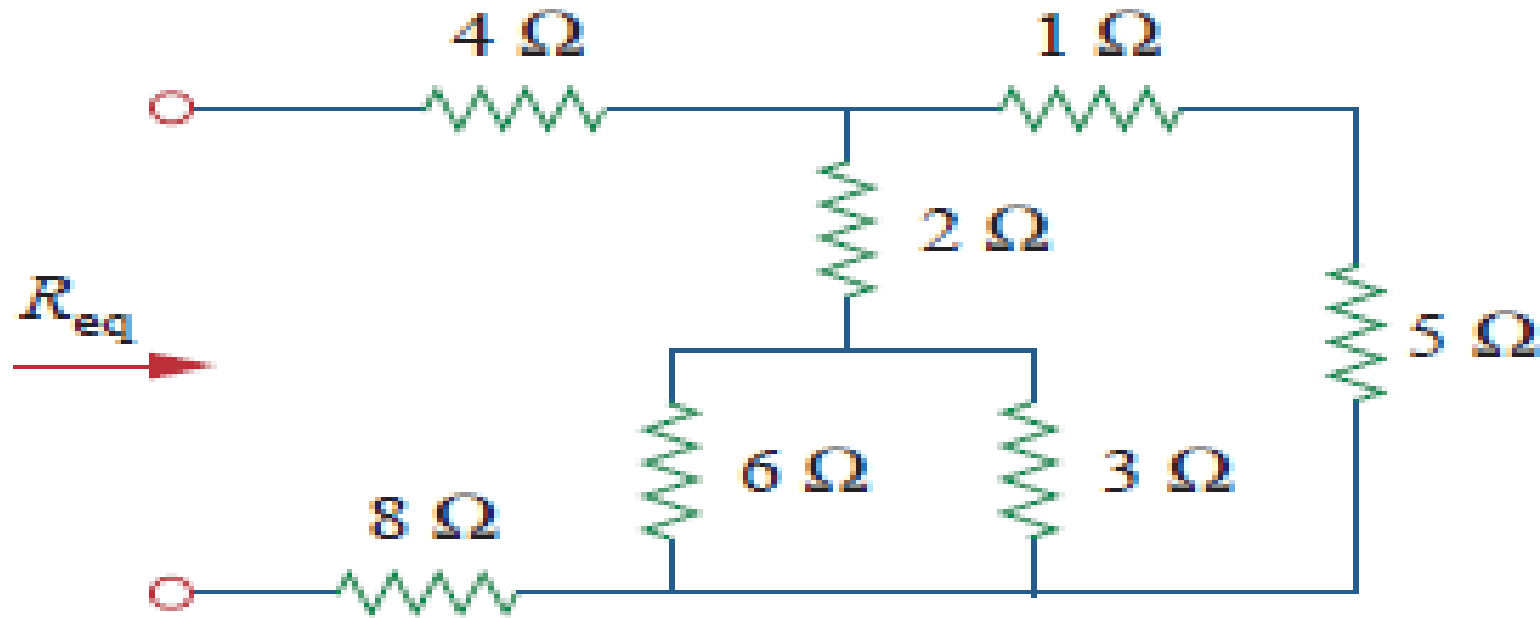
Find the equivalent resistance for the circuit shown in figure



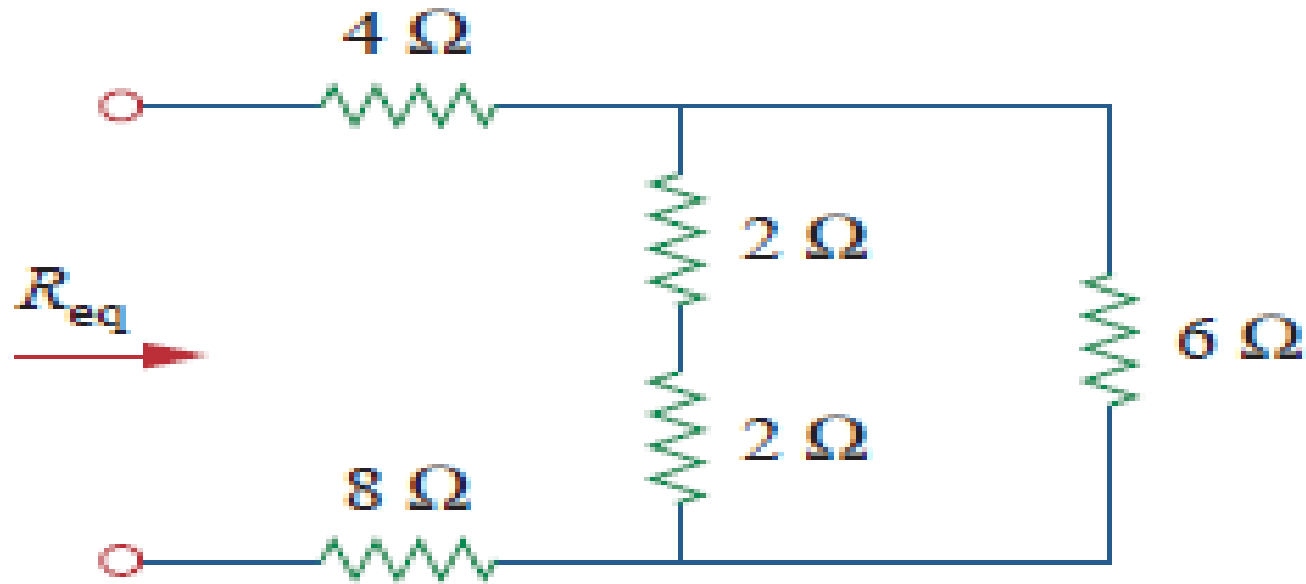Find the equivalent resistance for the circuit shown in figure




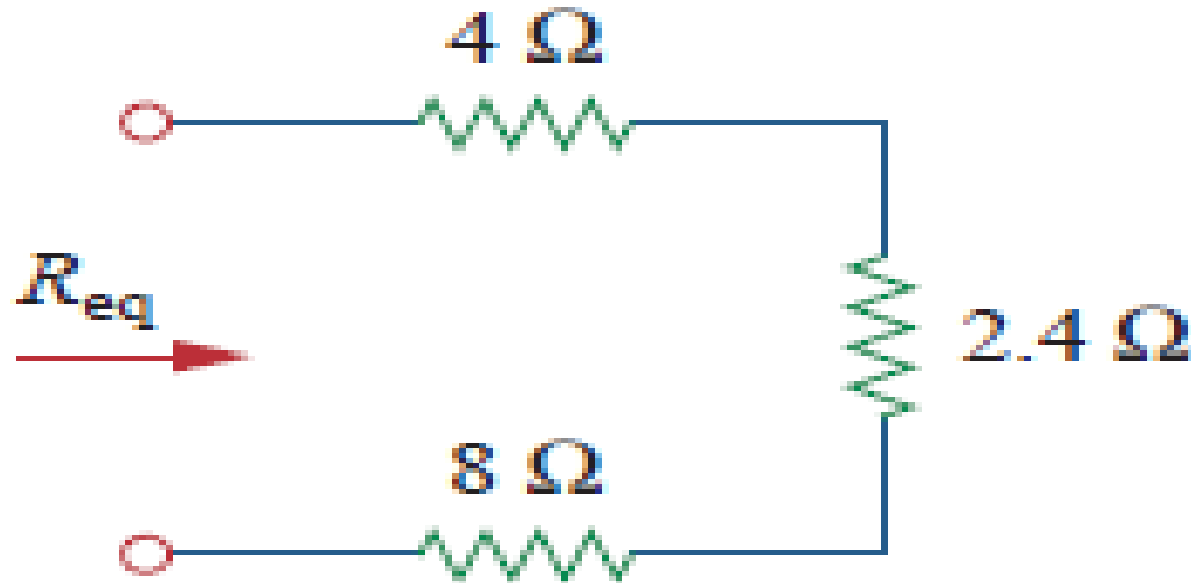Find the equivalent resistance for the circuit shown in figure




Ans: 14.4 Ohms

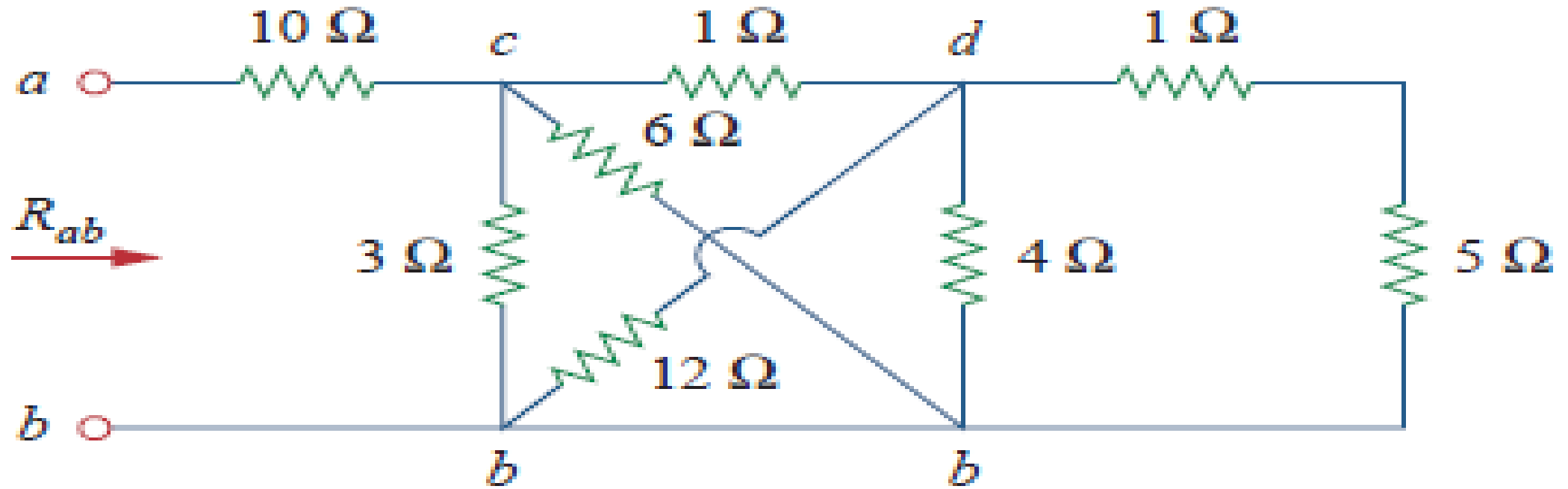
Find the equivalent resistance for the circuit shown in figure



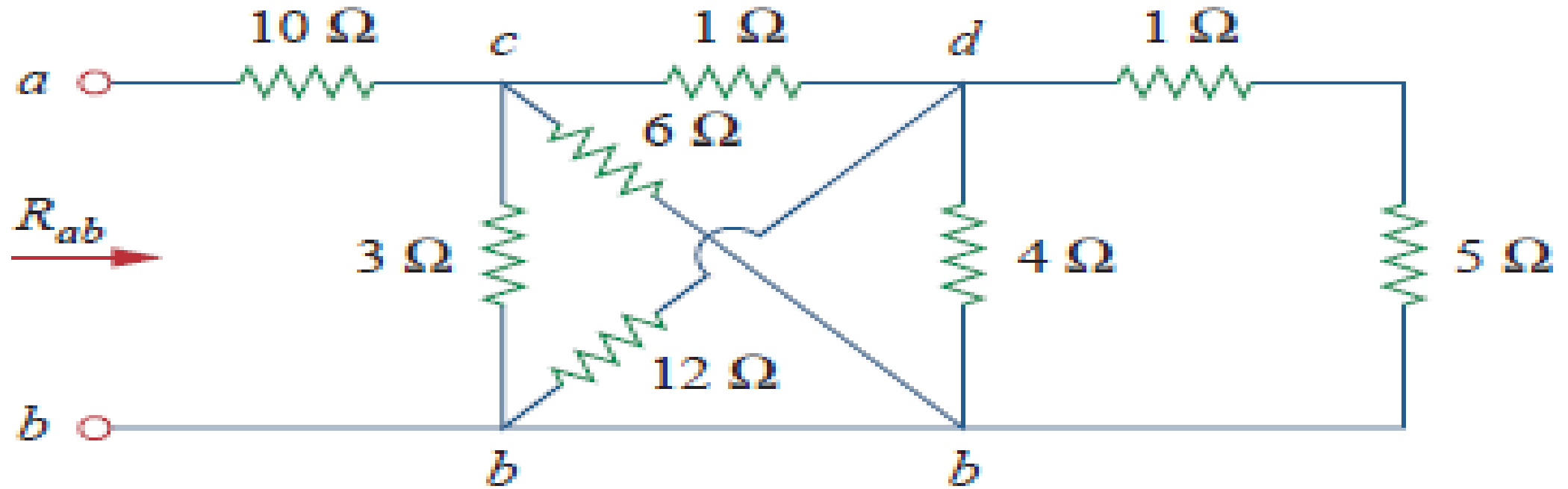
Find the equivalent resistance for the circuit shown in figure



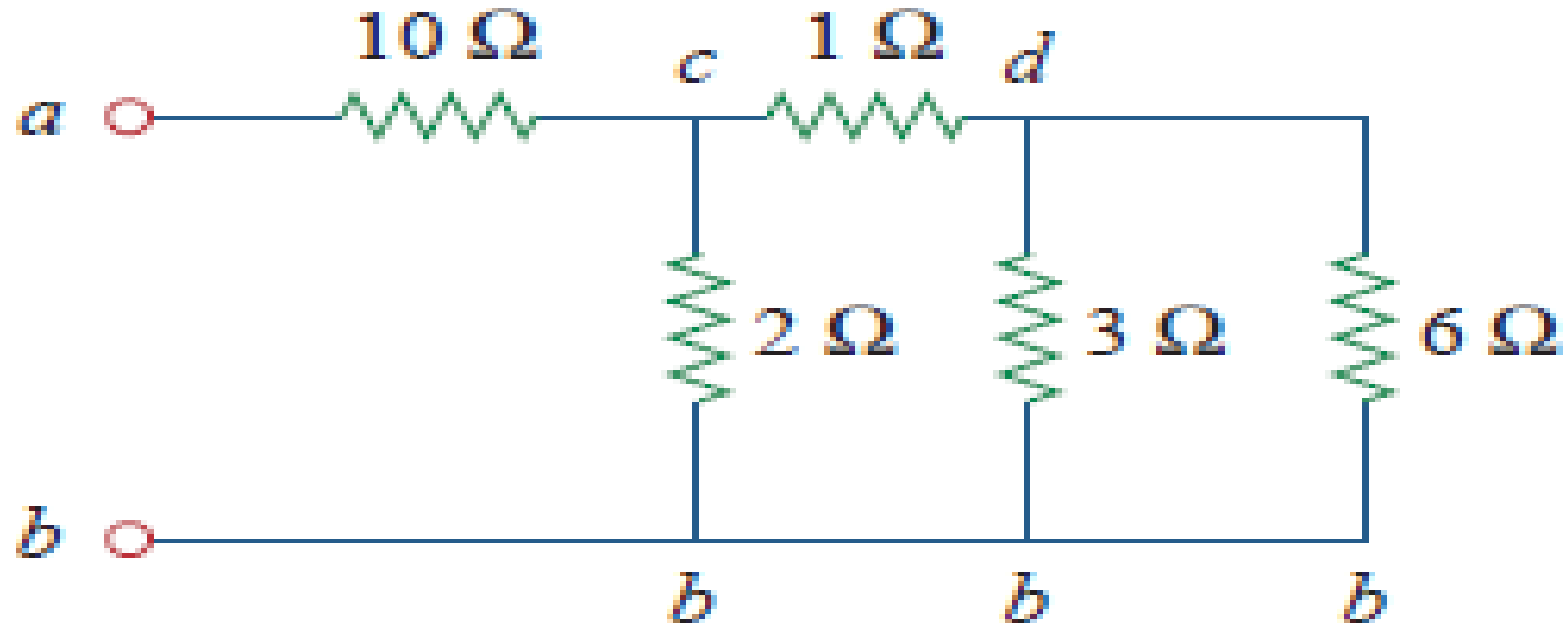Find the equivalent resistance for the circuit shown in figure




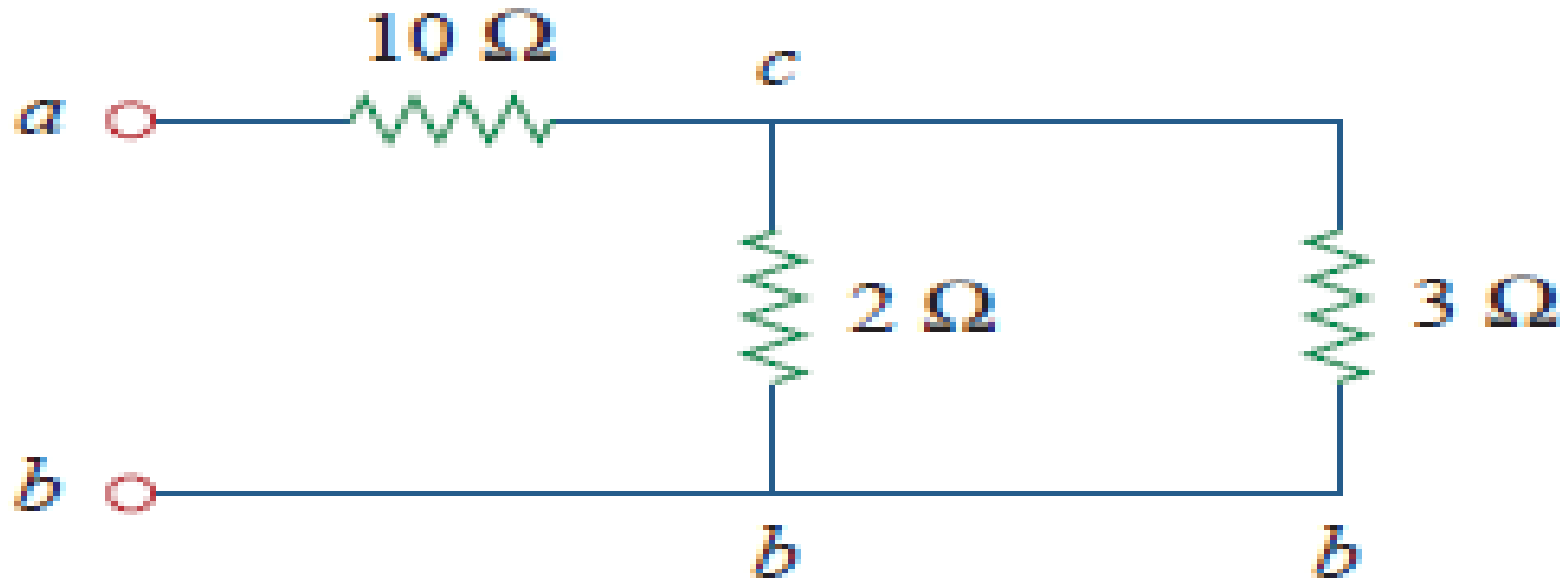Find the equivalent resistance for the circuit shown in figure




Ans: 11.2 Ohms

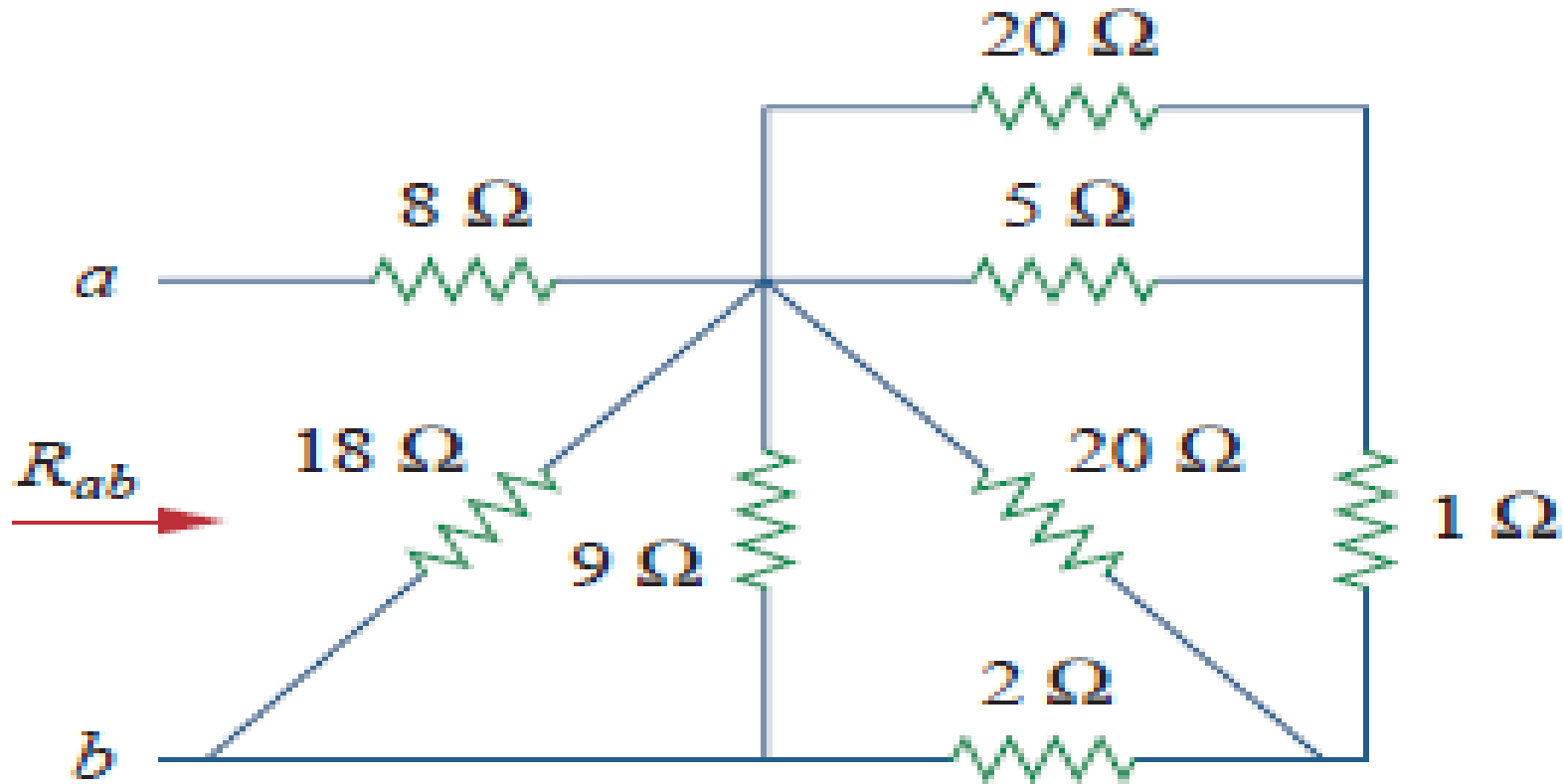Find the equivalent resistance for the circuit shown in figure




Ans: 11 Ohms

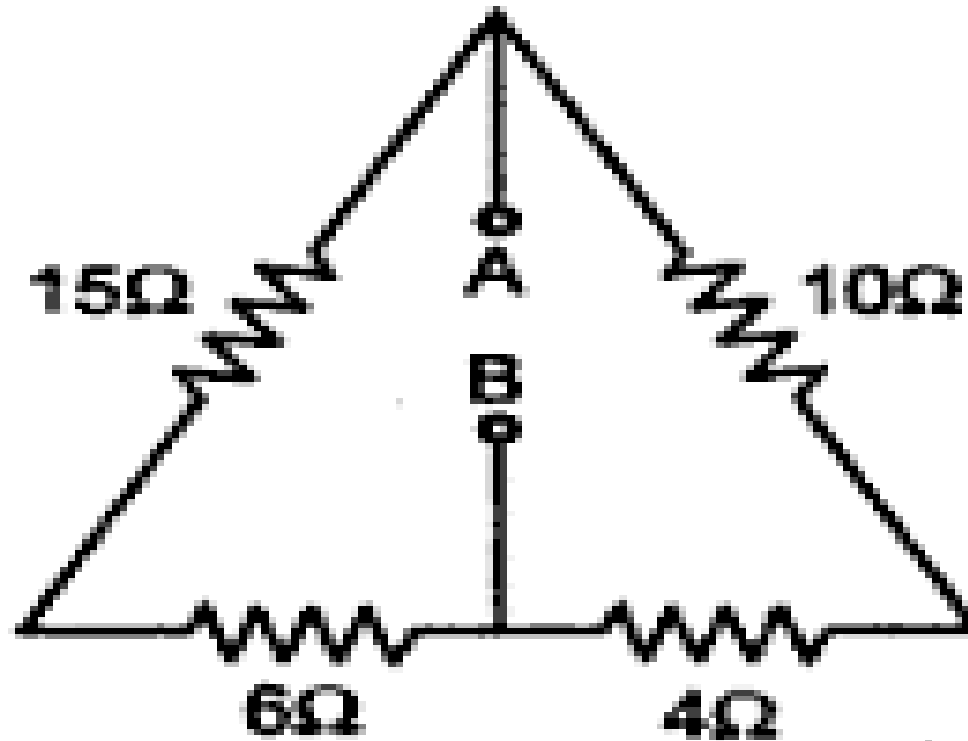
Find the equivalent resistance for the circuit shown in figure



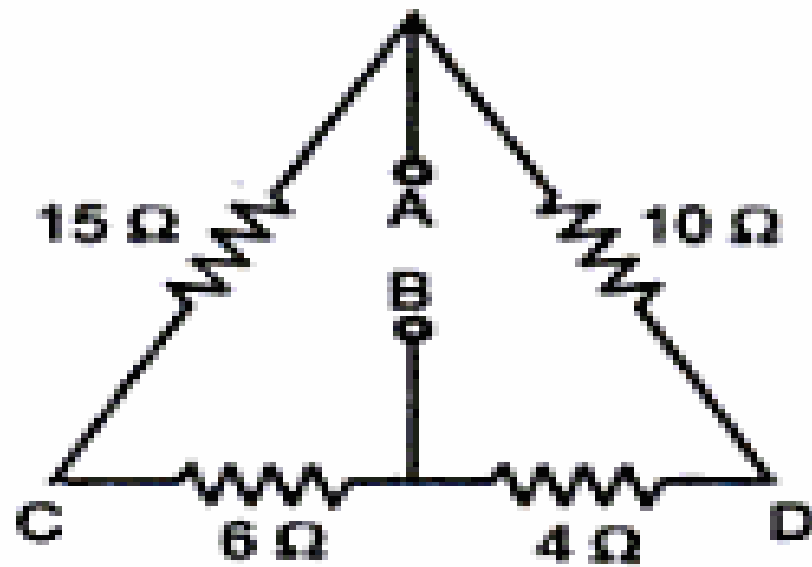
Find the equivalent resistance for the circuit shown in figure



\approx

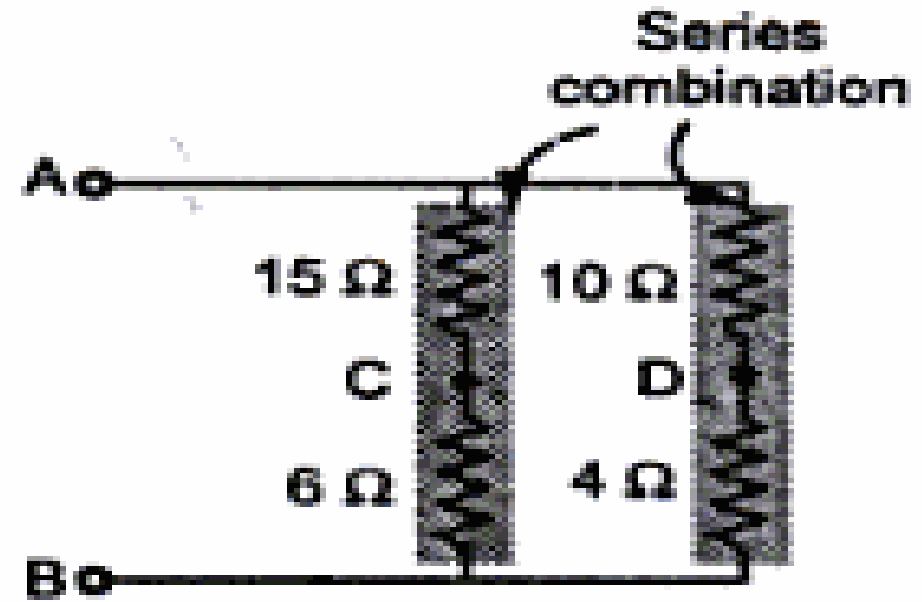


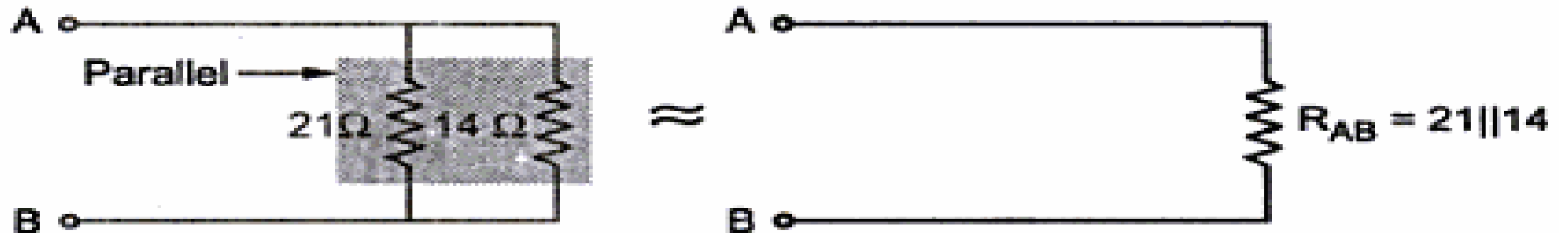Find the equivalent resistance for the circuit shown in figure




$$R_{AB} = \frac{21 \times 14}{21 + 14} = 8.4 \Omega$$

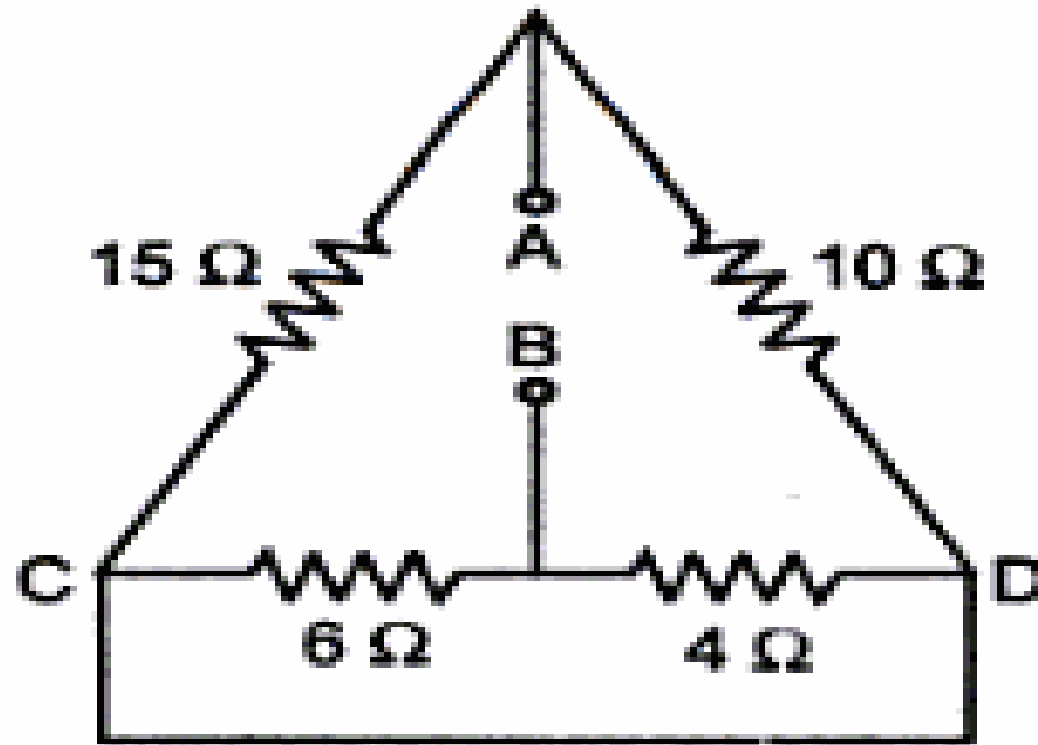
Find the equivalent resistance for the circuit shown in figure



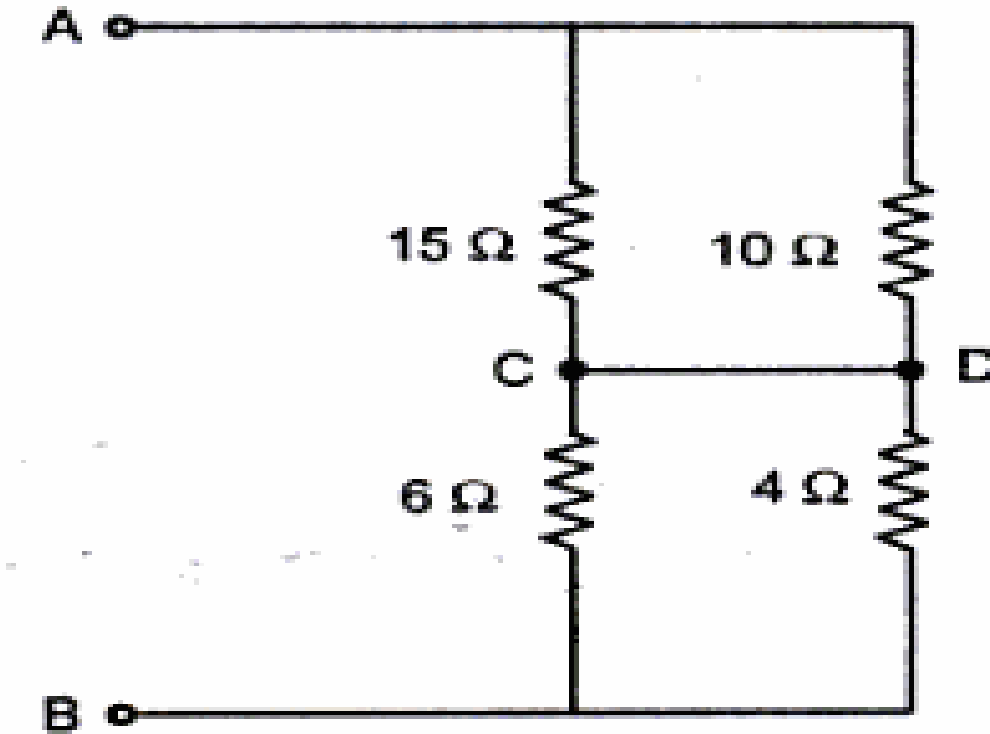
Find the equivalent resistance for the circuit shown.



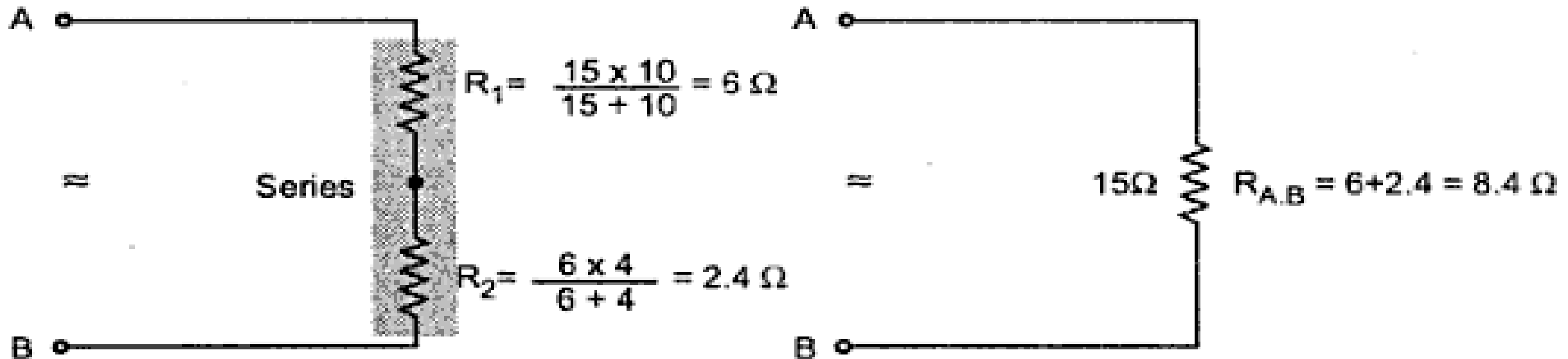
Find the equivalent resistance for the circuit shown in figure



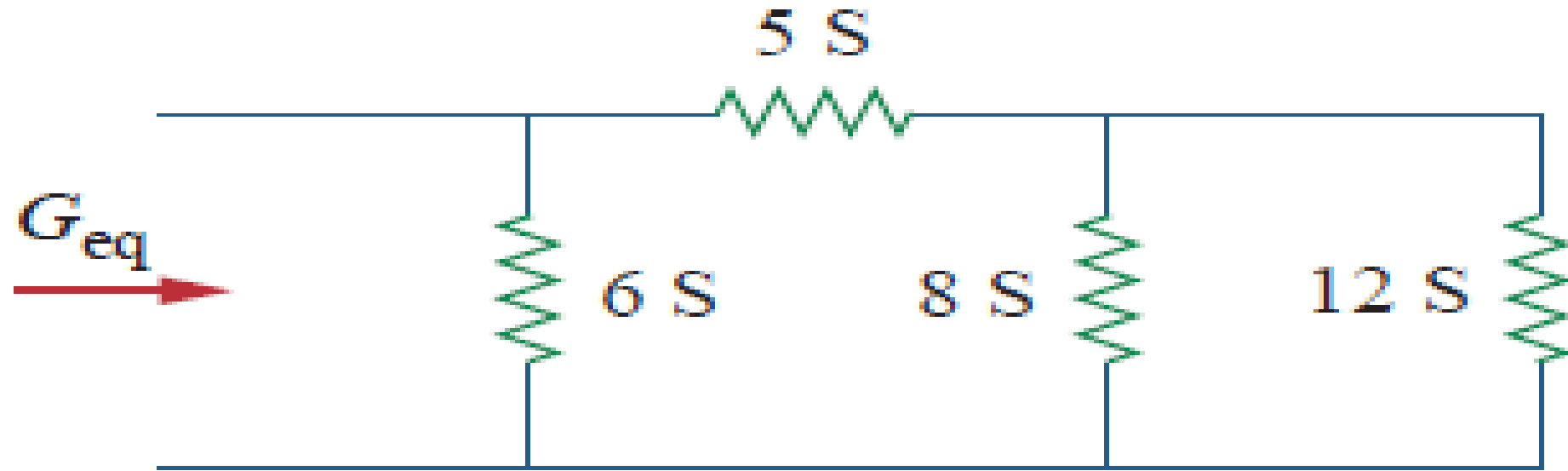Find the equivalent conductance for the circuit shown in figure




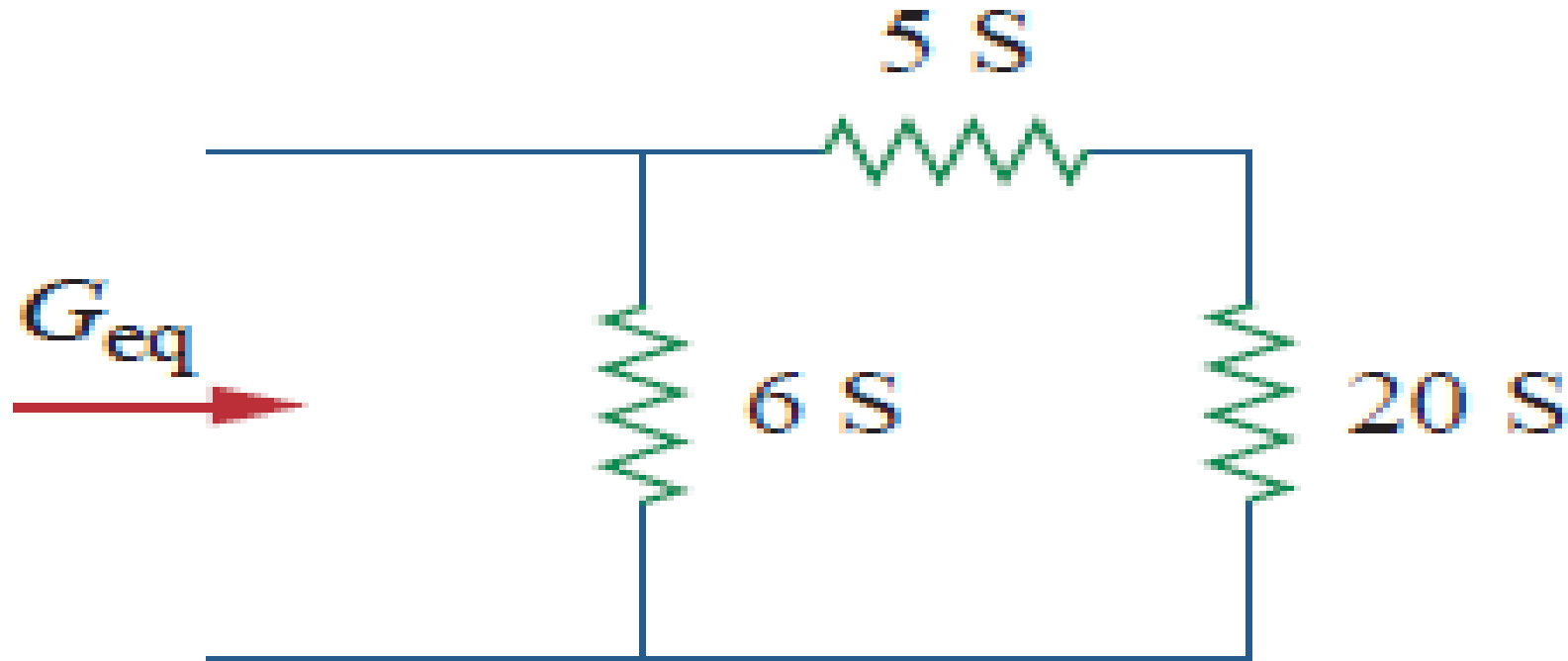Find the equivalent conductance for the circuit shown in figure



Ans: 10 S

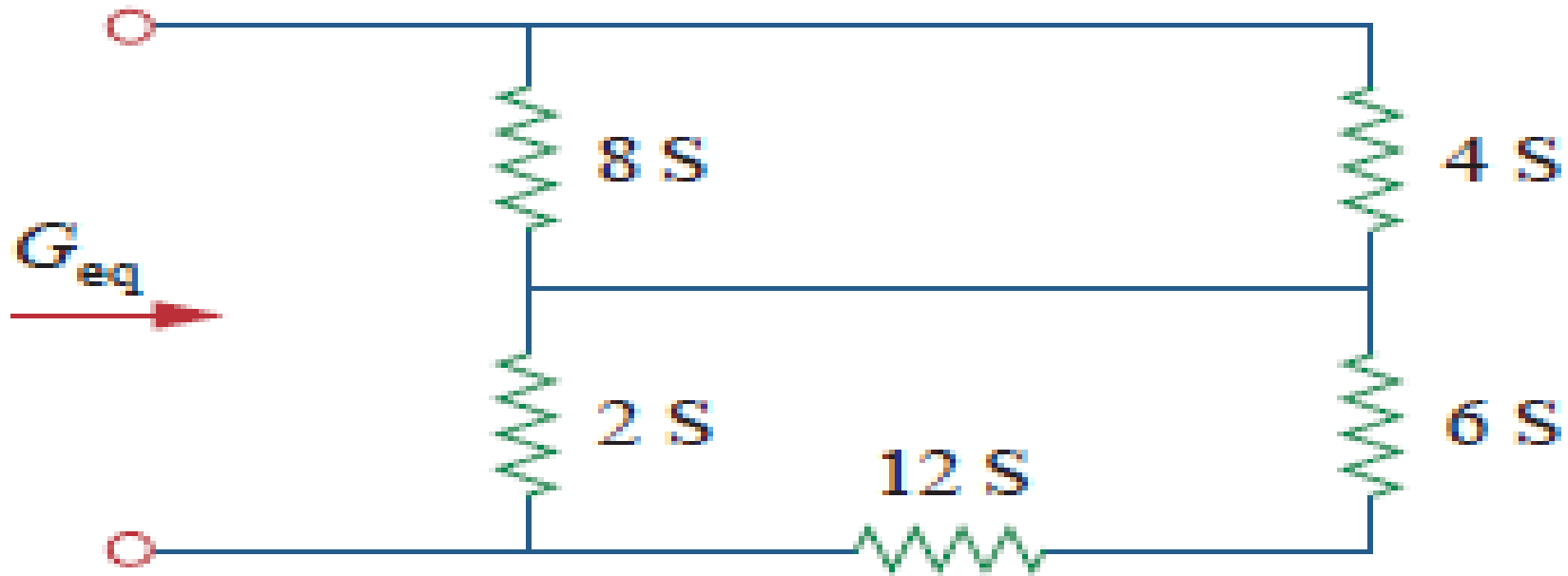Find the equivalent conductance for the circuit shown in figure



Ans: 4 S


Wye-Delta Transformations

Delta to Wye Conversion

Wye to Delta Conversion

circuit analysis when the resistors are neither in parallel nor in series.



Wye-Delta Transformations


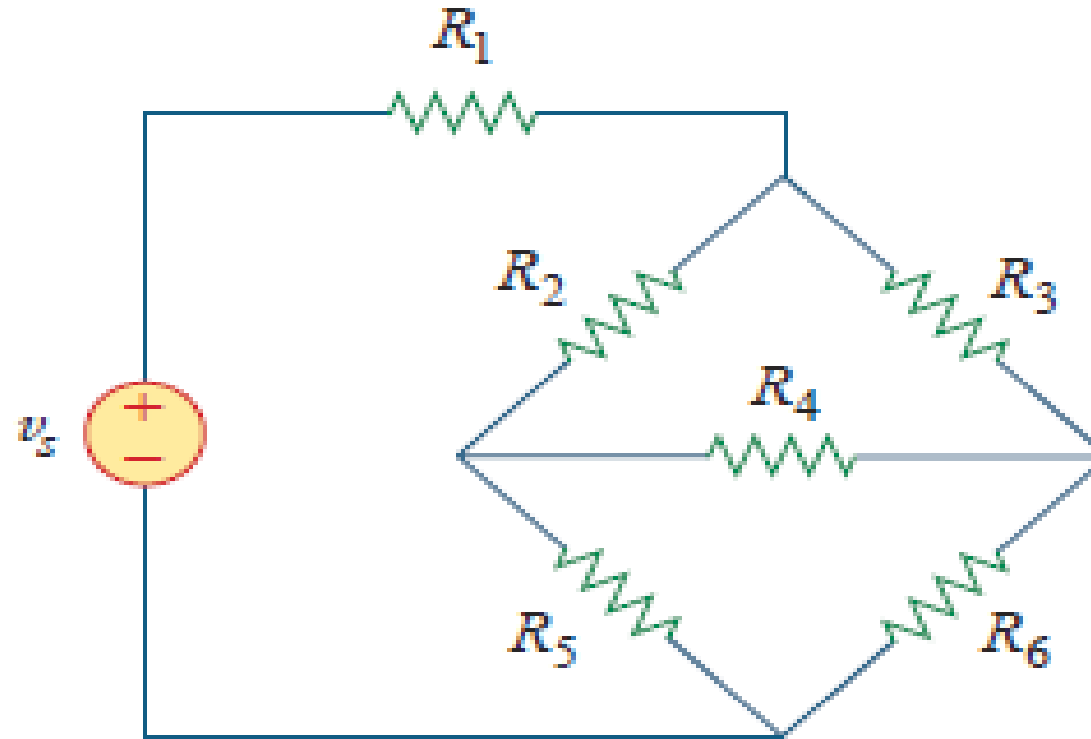




The bridge network.

How do we combine resistors R_1 through R_6 when the resistors are neither in series or parallel ?

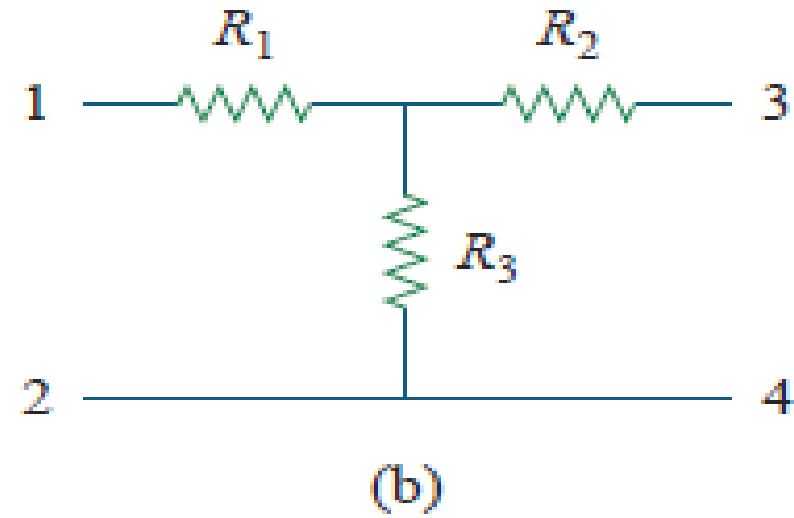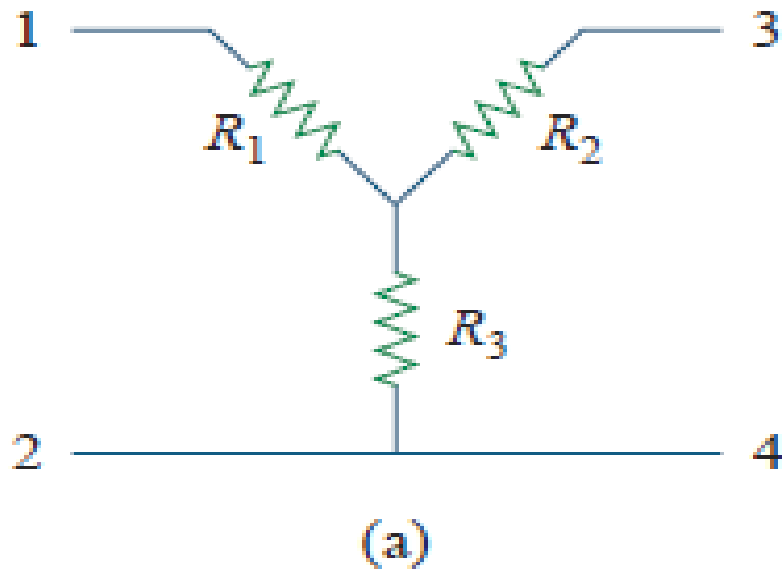Many circuits of the type can be simplified by using three-terminal networks





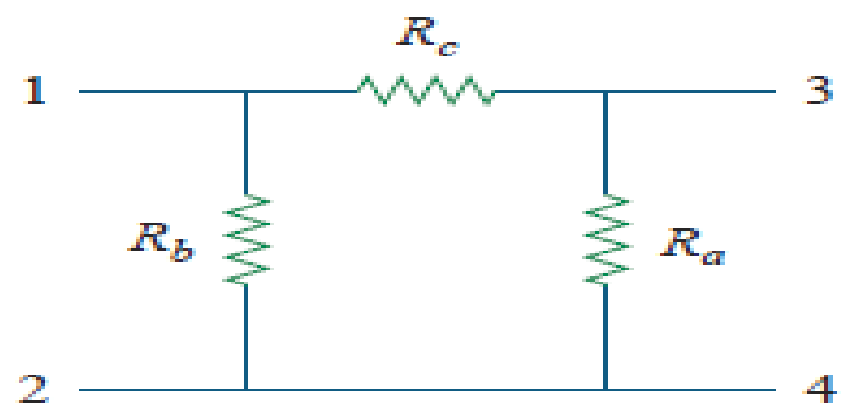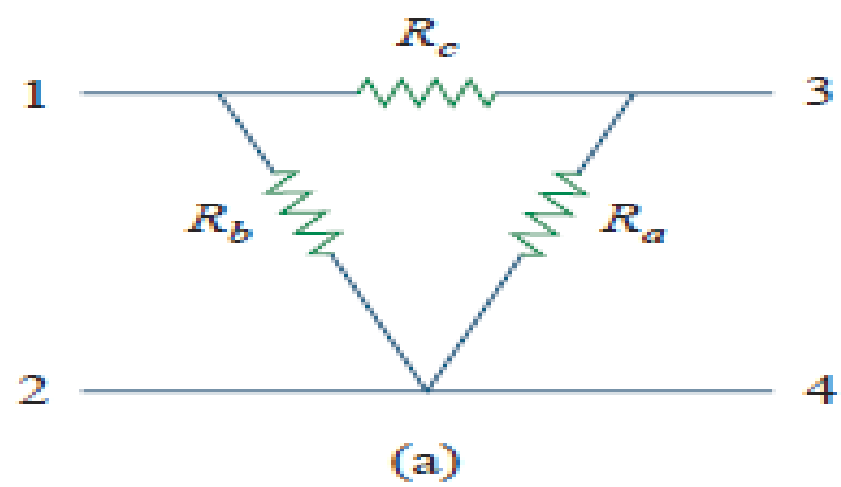

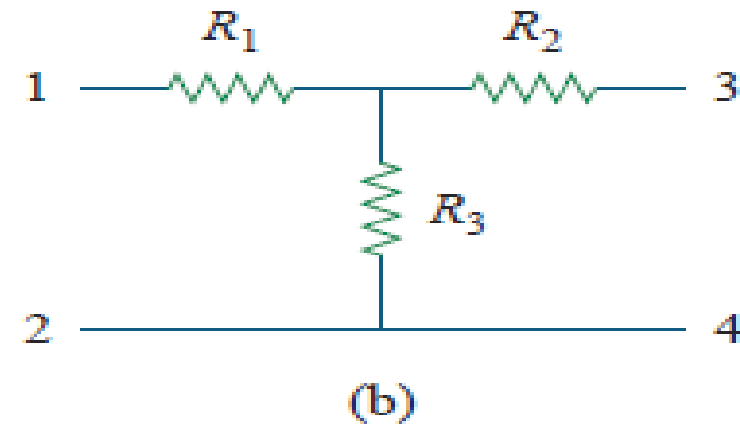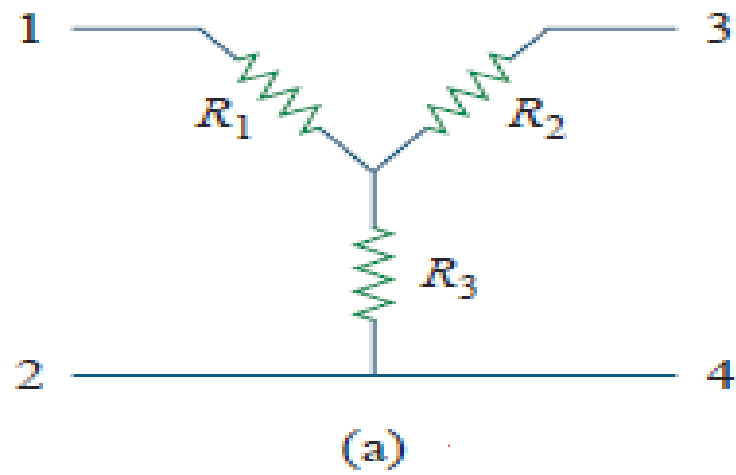



Two forms of the same network: (a) Y, (b) T.

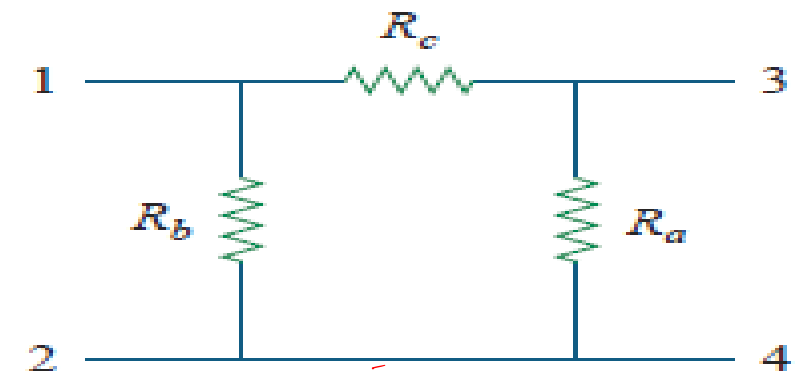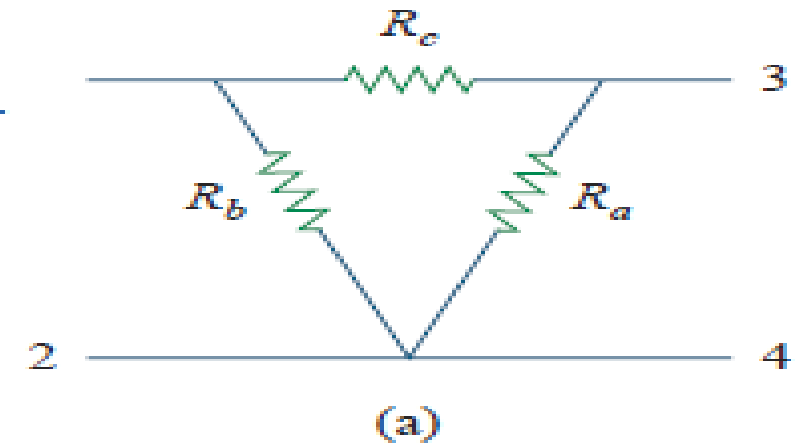Two forms of the same network: (a) Δ ,
(b) Π .




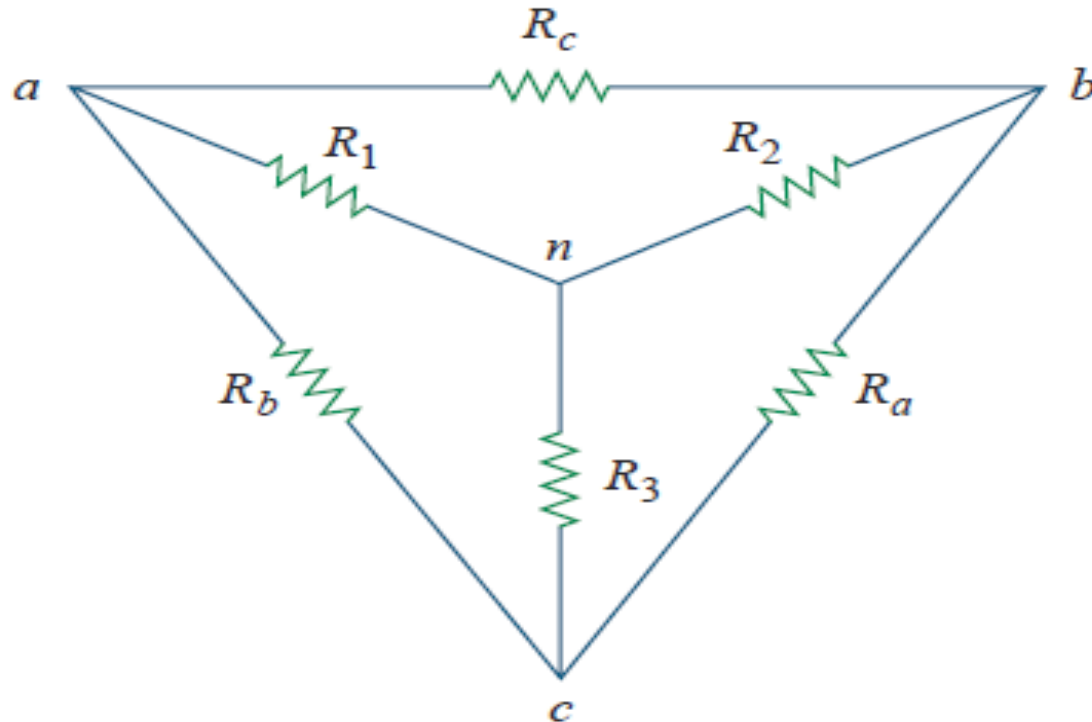- These networks occur by themselves or as part of a larger network
- To identify them when they occur as a part of a network and how to apply wye-delta transformation in the analysis of that network
- Convenient to work with a wye network in a place where the circuit contains delta configuration



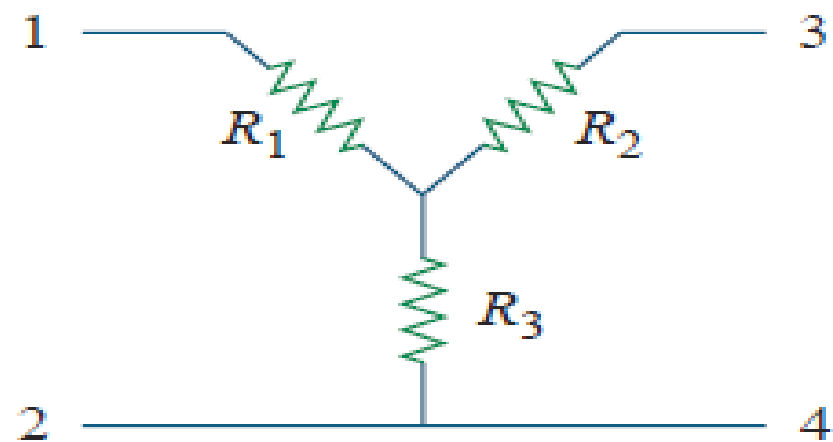

(a)

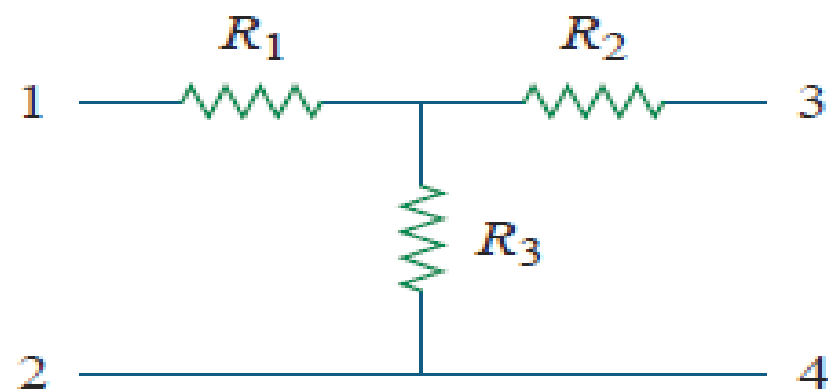


(b)

$$R_{12}(Y) = R_1 + R_3$$


$$R_{13} = R_1 + R_2$$

$$R_{34} = R_2 + R_3$$

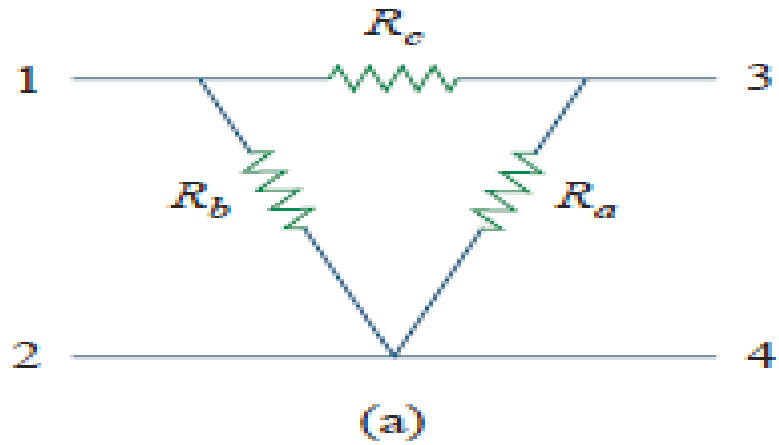

$$R_{12}(\Delta) = R_b \parallel (R_a + R_c)$$
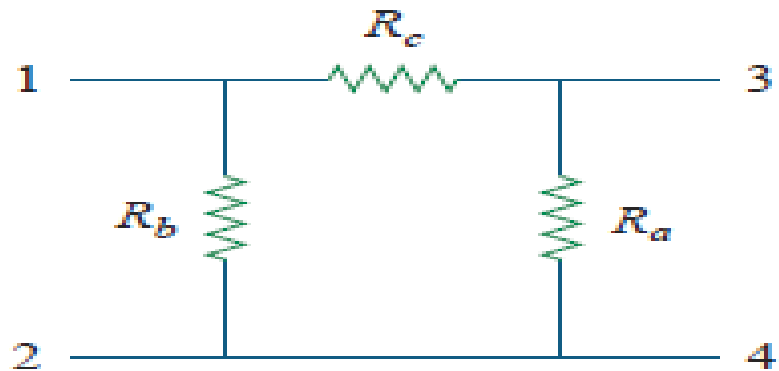
$$= \frac{R_b(R_a + R_c)}{R_a + R_b + R_c}$$



$$R_{13} = \frac{R_c(R_a + R_b)}{R_a + R_b + R_c}$$

$$R_{34} = \frac{R_a(R_b + R_c)}{R_a + R_b + R_c}$$

Delta to Wye Conversion

Setting $R_{12}(Y) = R_{12}(\Delta)$ gives



$$R_1 - R_2 = \frac{R_c(R_b - R_a)}{R_a + R_b + R_c}$$

$$R_{12} = R_1 + R_3 = \frac{R_b(R_a + R_c)}{R_a + R_b + R_c}$$

Similarly,

$$R_{13} = R_1 + R_2 = \frac{R_c(R_a + R_b)}{R_a + R_b + R_c}$$

$$R_{34} = R_2 + R_3 = \frac{R_a(R_b + R_c)}{R_a + R_b + R_c}$$


$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$
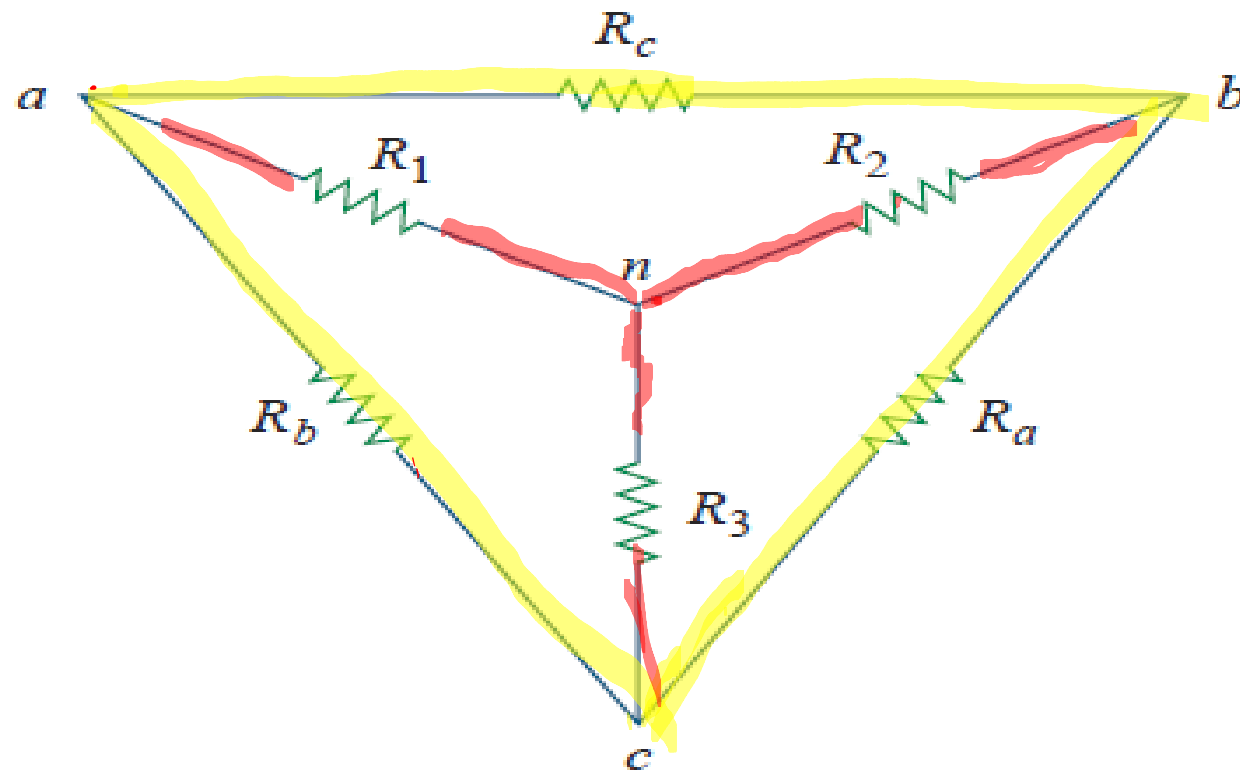
$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$



$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

Each resistor in the Y network is the product of the resistors in the two adjacent Δ branches, divided by the sum of the three Δ resistors.

Wye to Delta Conversion

$$\begin{aligned} R_1 R_2 + R_2 R_3 + R_3 R_1 &= \frac{R_a R_b R_c (R_a + R_b + R_c)}{(R_a + R_b + R_c)^2} \\ &= \frac{R_a R_b R_c}{R_a + R_b + R_c} \end{aligned}$$

Dividing Eq. by each of Eqs.

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

Each resistor in the Δ network is the sum of all possible products of Y resistors taken two at a time, divided by the opposite Y resistor.

The Y and Δ networks are said to be *balanced* when



$$R_1 = R_2 = R_3 = R_Y, \quad R_a = R_b = R_c = R_\Delta$$

Under these conditions, conversion formulas become

$$R_Y = \frac{R_\Delta}{3} \quad \text{or} \quad R_\Delta = 3R_Y$$

One may wonder why R_Y is less than R_Δ . Well, we notice that the Y-connection is like a “series” connection while the Δ -connection is like a “parallel” connection.

Example

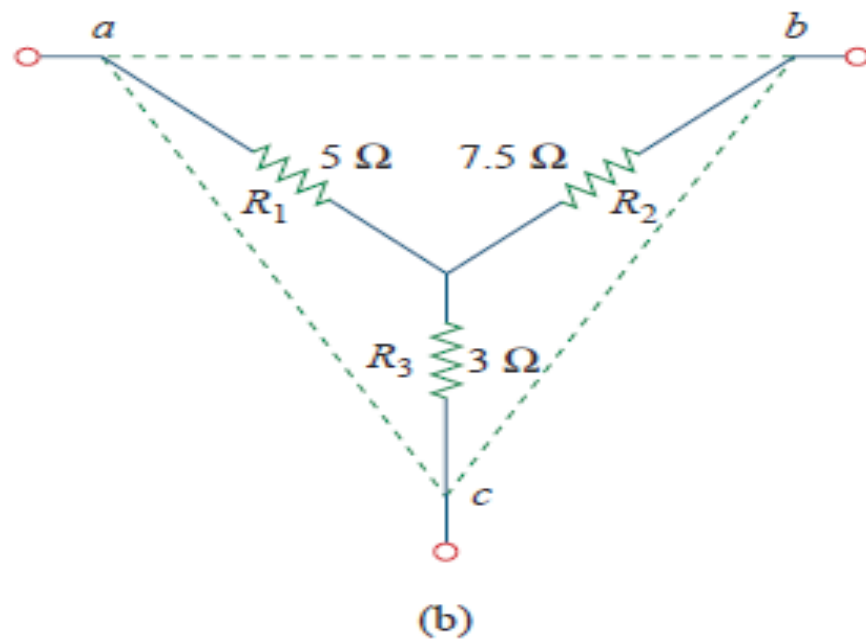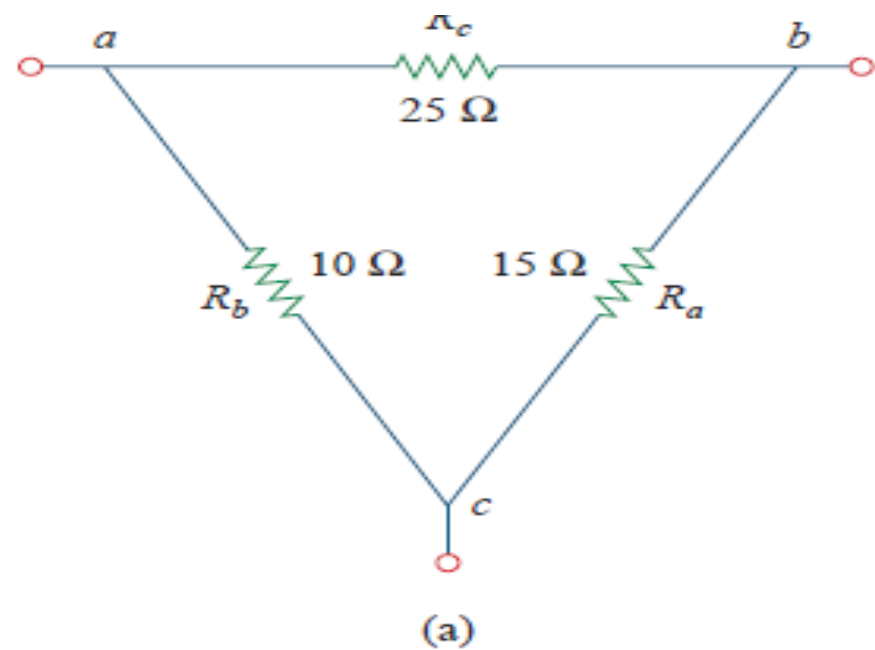


$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$


Example


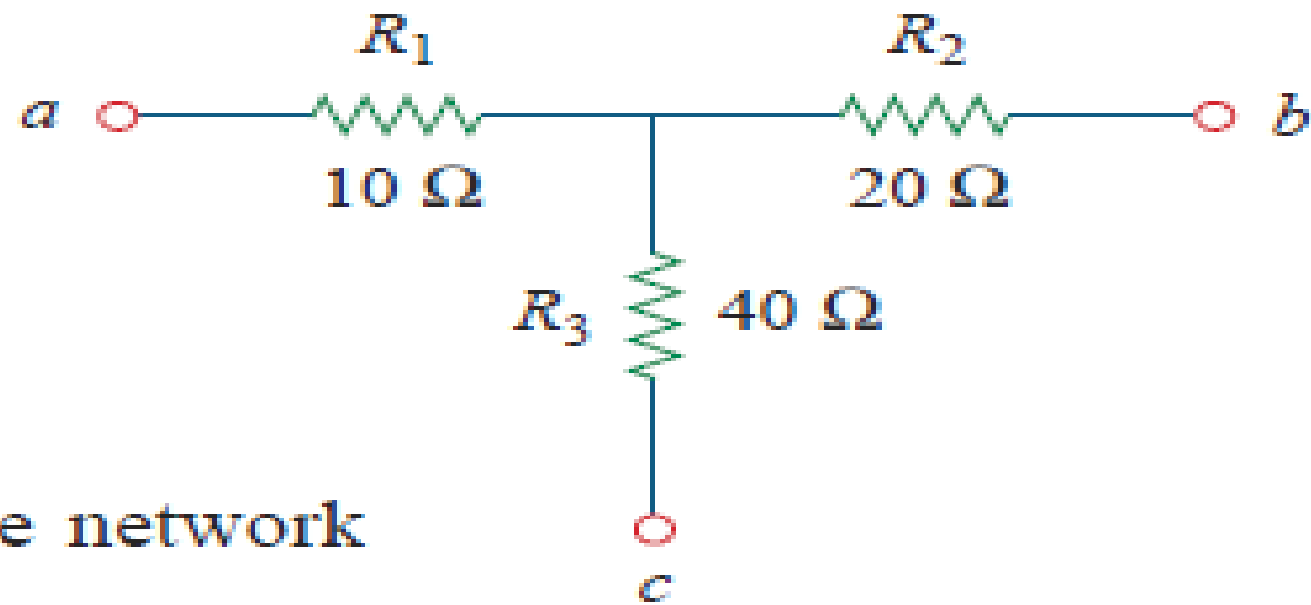


Transform the wye network to a delta network.

Answer: $R_a = 140\ \Omega$, $R_b = 70\ \Omega$, $R_c = 35\ \Omega$.




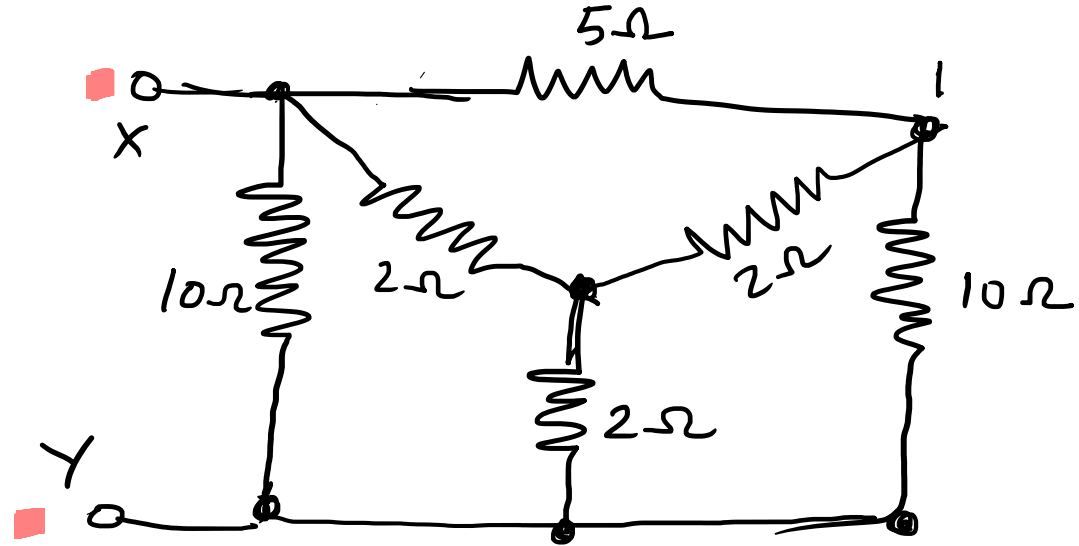
Find the equivalent resistance between terminals $x-y$ in the resistive network in fig



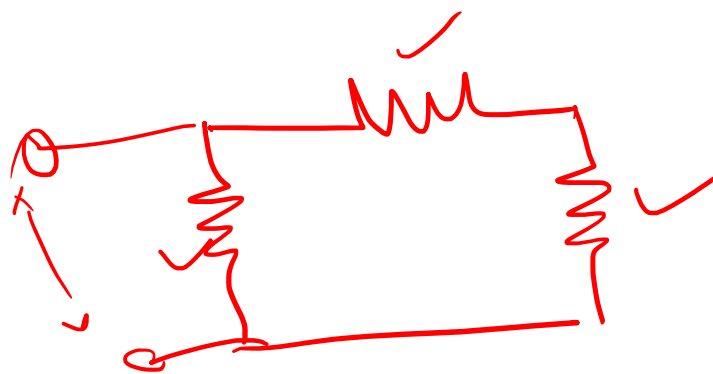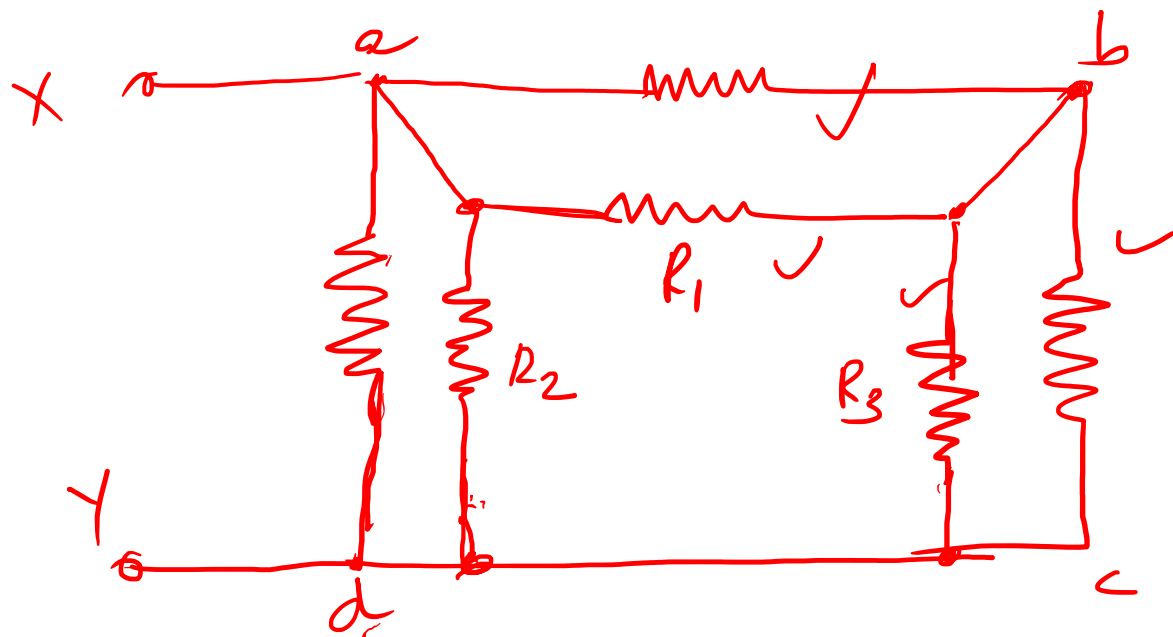



2.375 Ω

Find
Equivalent
Star network?

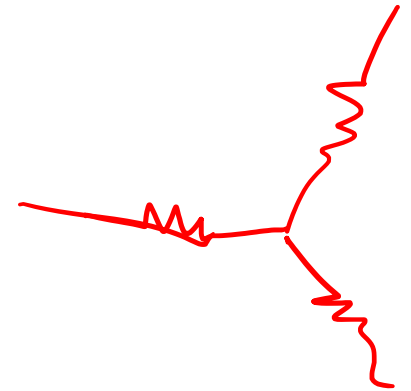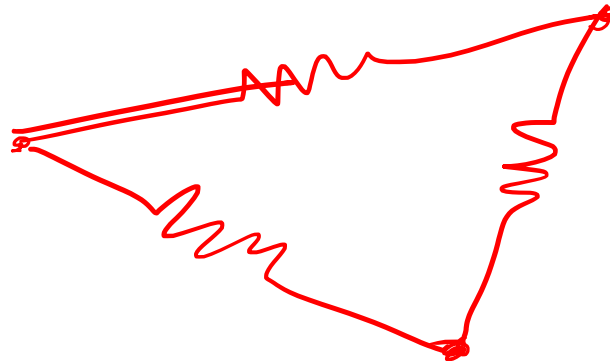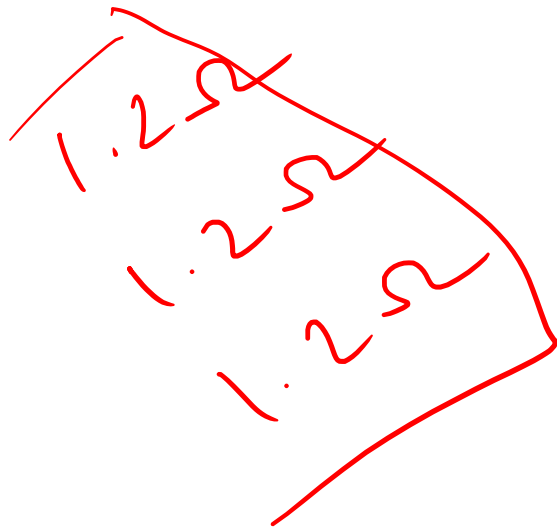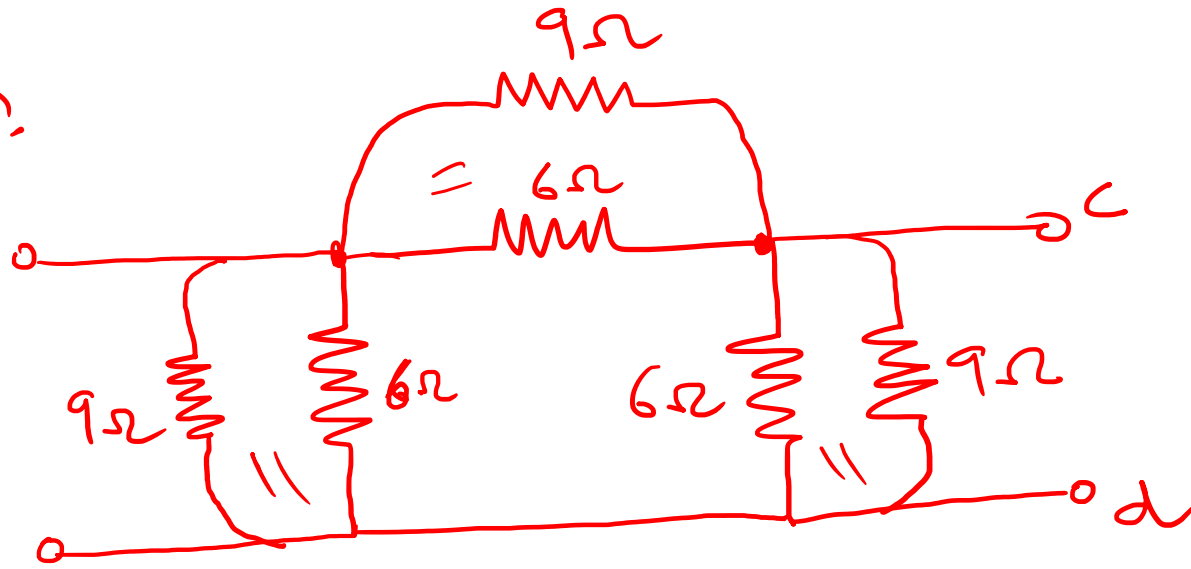

Find the power loss in 1Ω resistor

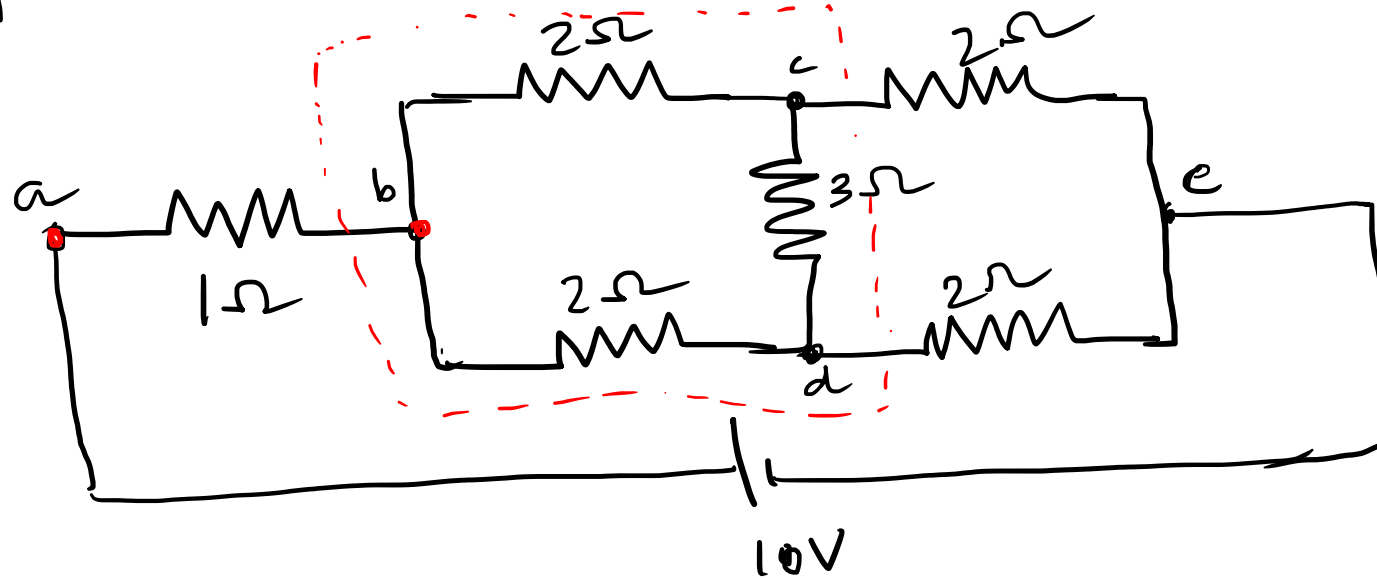


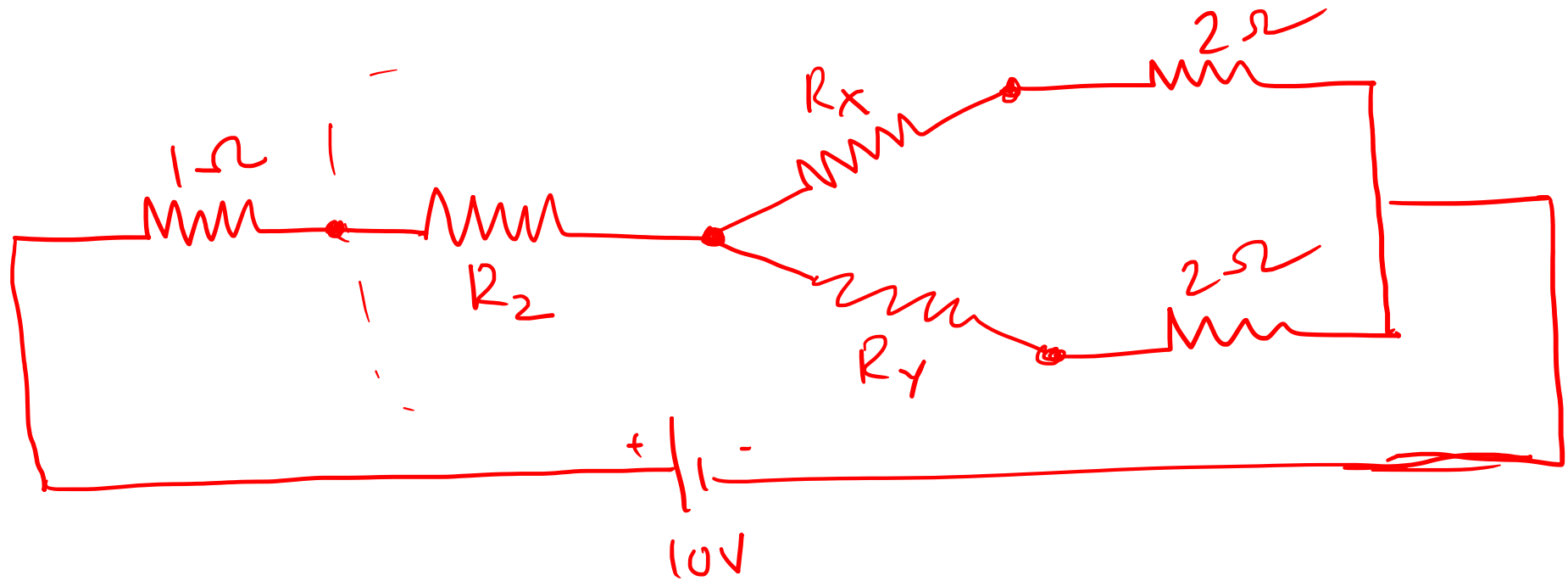

$$R_x = 0.86 \Omega$$

$$R_y = 0.86 \Omega$$

$$R_2 = 0.57 \Omega$$

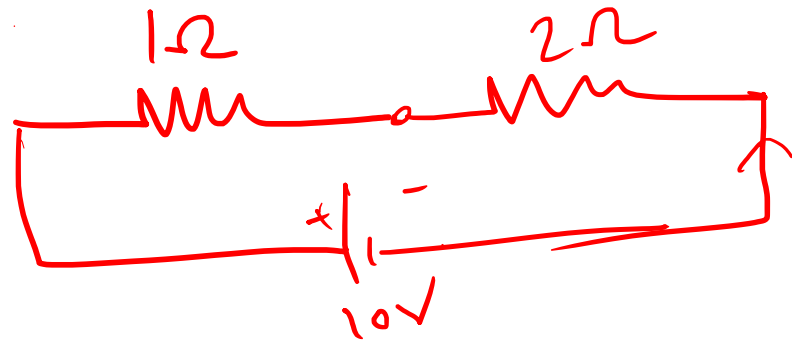

$$I = \frac{10V}{1+2} A$$

$$I^2 R$$