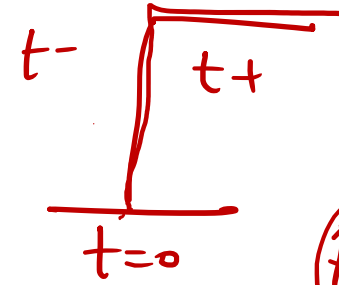








# Step Response of an RC Circuit


- ❑ DC source is suddenly introduced ✓
- ❑ Voltage /current will be a step function
- ❑ The response is Step response



Forced + Natural

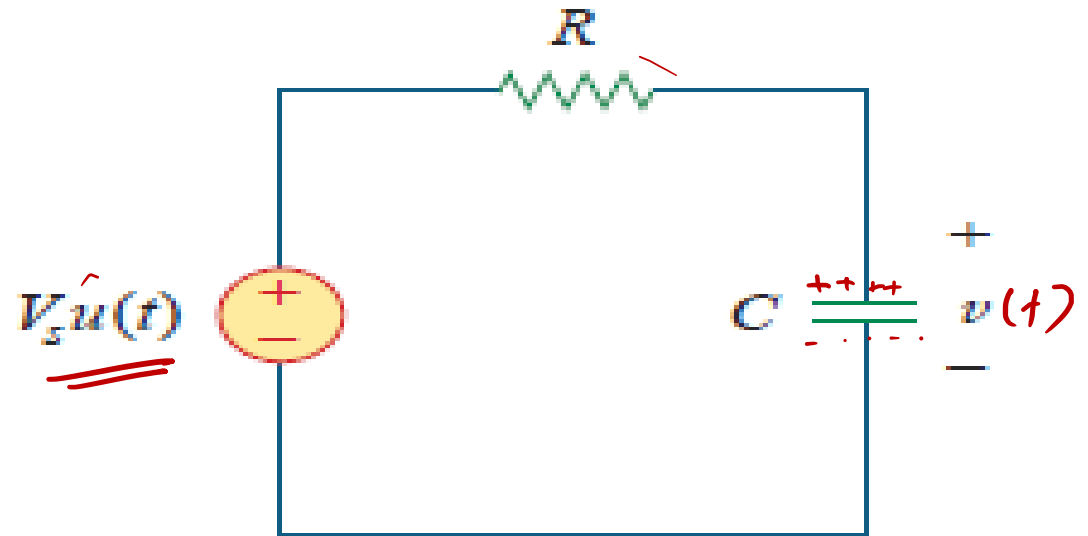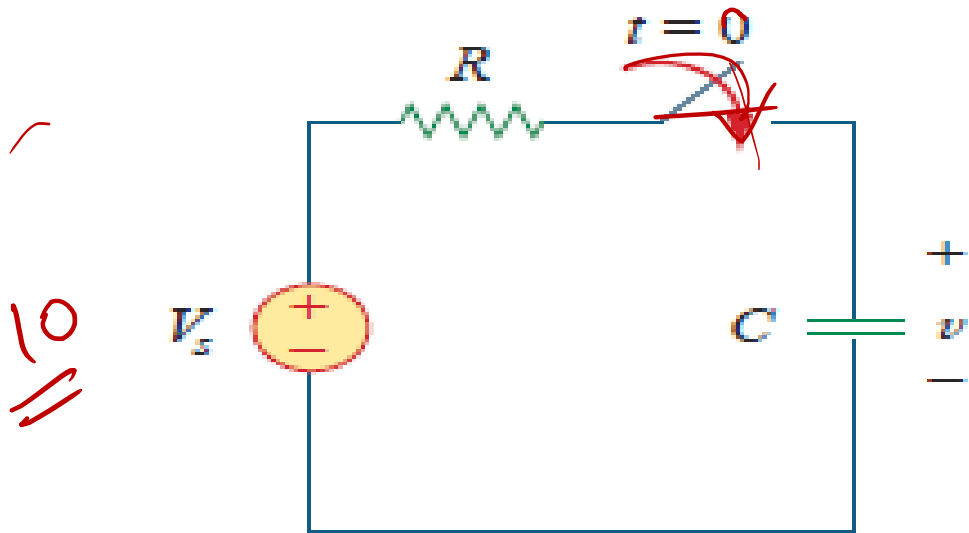The **step response** of a circuit is its behavior when the excitation is the step function, which may be a voltage or a current source.



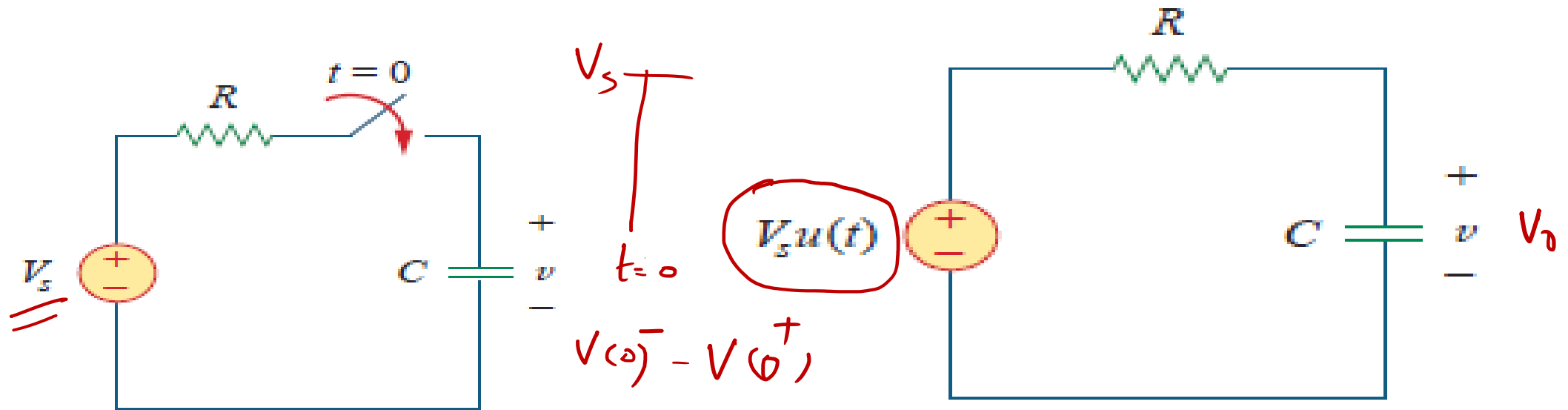

□ Let initial voltage on the capacitor,  $V_0$  (although this is not necessary for the step response).


□ Since the voltage of a capacitor cannot change instantaneously

$$v(0^-) = v(0^+) = V_0$$

Initial voltage

$v(0^-)$  is the voltage across the capacitor just before switching

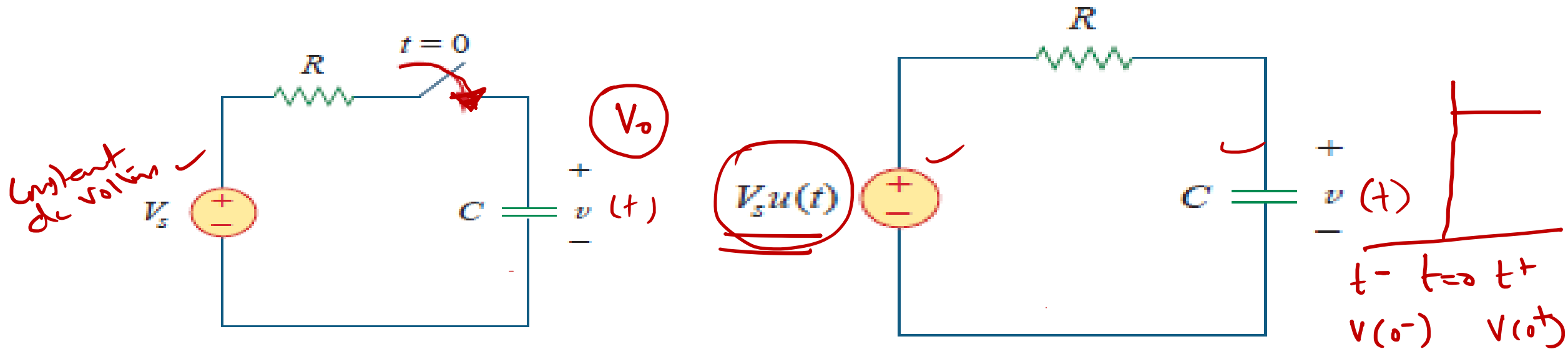$v(0^+)$  is its voltage immediately after switching



$$C \frac{dv}{dt} + \frac{v - V_s u(t)}{R} = 0 \quad \text{or} \quad \frac{dv}{dt} + \frac{v}{RC} = \frac{V_s}{RC} u(t) \quad \checkmark$$

where  $v$  is the voltage across the capacitor. For  $t > 0$ ,

$$\frac{dv}{dt} + \frac{v}{RC} = \frac{V_s}{RC}$$

$$\frac{dv}{dt} = -\frac{v - V_s}{RC} \quad \text{or}$$

$$\frac{dv}{v - V_s} = -\frac{dt}{RC}$$

$$\ln(v - V_s) \Big|_{V_0}^{v(t)} = - \frac{t}{RC} \Big|_0^t$$

$$\ln(v(t) - V_s) - \ln(V_0 - V_s) = - \frac{t}{RC} + 0$$

$$\ln \frac{v - V_s}{V_0 - V_s} = - \frac{t}{RC}$$


$$\frac{v - V_s}{V_0 - V_s} = e^{-t/\tau},$$

$$\tau = RC$$

$$v - V_s = (V_0 - V_s)e^{-t/\tau} \quad \checkmark$$

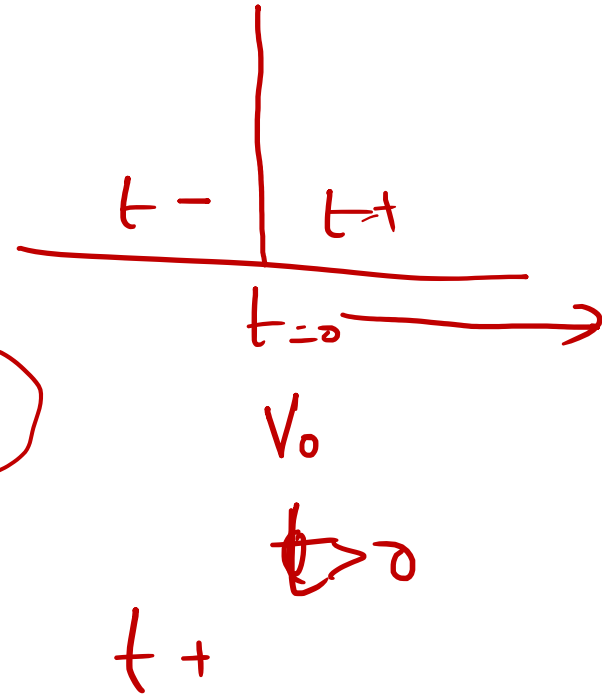
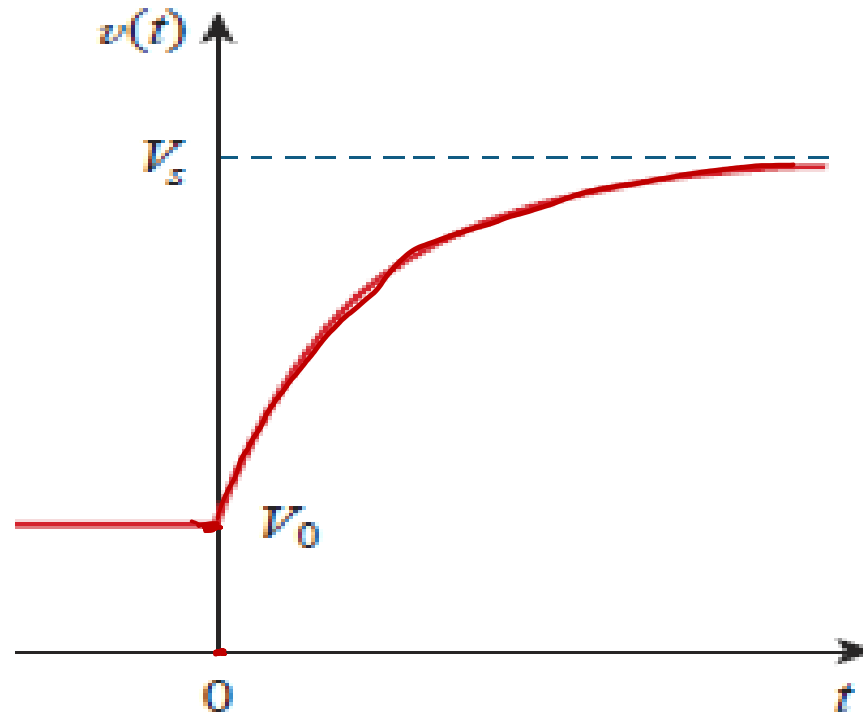
$$v(t) = V_s + (V_0 - V_s)e^{-t/\tau}, \quad t > 0$$

$V(s) u(t)$



$$v(t) = \begin{cases} V_0, & t < 0 \\ \underline{V_s + (V_0 - V_s)e^{-t/\tau}}, & t > 0 \end{cases}$$

$t_1$   
 $t_2$   
 $t_1$

Response of an *RC* circuit with initially charged capacitor.

This is known as the *complete response* (or total response) of the *RC* circuit to a sudden application of a dc voltage source, assuming the capacitor is initially charged.

$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau}, & t > 0 \end{cases}$$

If we assume that the capacitor is uncharged initially, we set  $V_0 = 0$

$$v(t) = \begin{cases} 0, & t < 0 \\ V_s(1 - e^{-t/\tau}), & t > 0 \end{cases}$$

which can be written alternatively as

$$v(t) = V_s(1 - e^{-t/\tau})u(t)$$

This is the complete step response of the  $RC$  circuit when the capacitor is initially uncharged

The current through the capacitor is obtained using  $i(t) = Cdv/dt$ .

$$i(t) = C \frac{dv}{dt} = \frac{C}{\tau} V_s e^{-t/\tau}, \quad \tau = RC, \quad t > 0$$

$$i(t) = \frac{V_s}{R} e^{-t/\tau} u(t)$$

$$V(t) = V_s (1 - e^{-t/\tau})$$

$$Q(t) = Q (1 - e^{-t/\tau})$$

$$0.8Q = Q(1 - e^{-t/\tau})$$

$$0.8 = 1 - e^{-t/\tau}$$


$$\tau = RC$$

$$10 \times 10^6$$




$$\underline{\underline{V_0 = 0}}$$
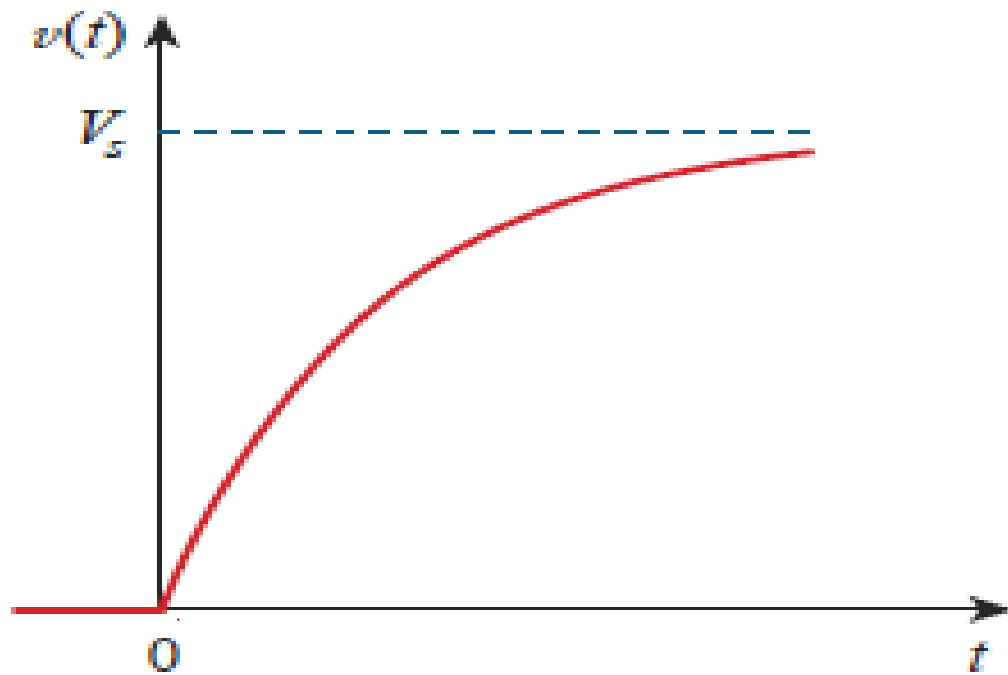
$$i(t) = \frac{V_s}{R} e^{-t/\tau} u(t)$$



(a)

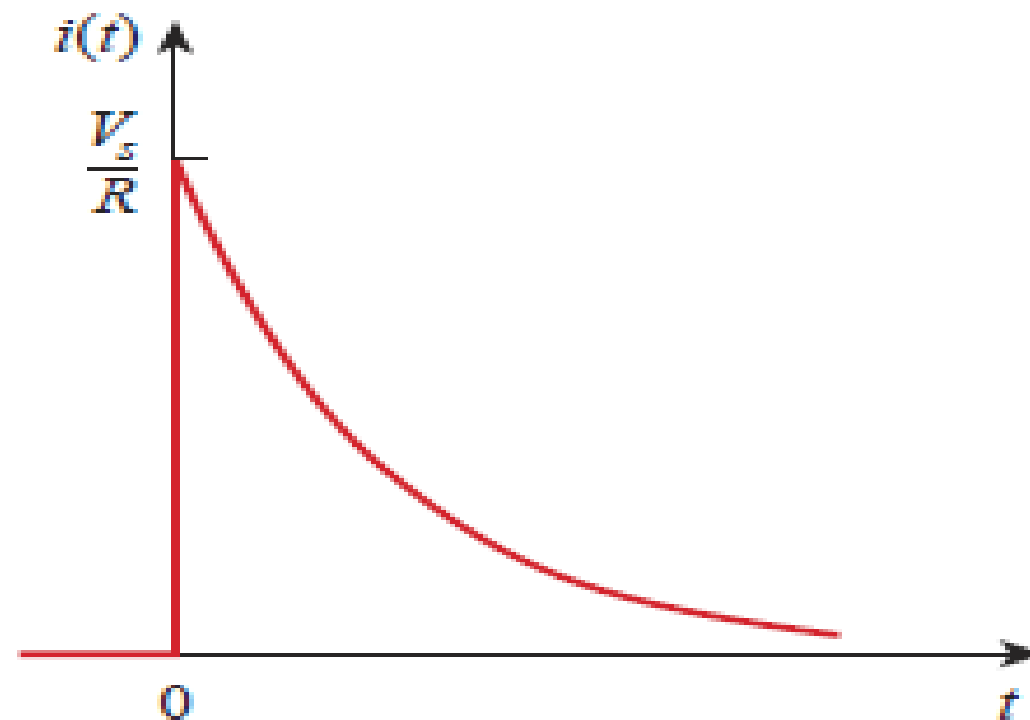

(b)

Step response of an  $RC$  circuit with initially uncharged capacitor:  
(a) Voltage response, (b) current response.

$$v(t) = V_s + (V_0 - V_s)e^{-t/\tau}, \quad t > 0$$

➤ It is evident that has two components.

Classically there are two ways of decomposing this into two components.

- The first is to break it into a “natural response and a forced response”
- The second is to break it into a “transient response and a steady-state response.”

Complete response = natural response + forced response  
stored energy                      independent source

$$v = v_n + v_f$$

$$v_n = V_0 e^{-t/\tau}$$

$$v_f = V_s(1 - e^{-t/\tau})$$

Another way of looking at the complete response is to break into two components—one temporary and the other permanent, i.e.,

$$\text{Complete response} = \underbrace{\text{transient response}}_{\text{temporary part}} + \underbrace{\text{steady-state response}}_{\text{permanent part}}$$

$$v = v_t + v_{ss} \qquad v_t = (V_o - V_s)e^{-t/\tau} \qquad v_{ss} = V_s$$

The *transient response*  $v_t$  is temporary; it is the portion of the complete response that decays to zero as time approaches infinity. Thus,

The **transient response** is the circuit's temporary response that will die out with time.

The *steady-state response*  $v_{ss}$  is the portion of the complete response that remains after the transient response has died out. Thus,

The **steady-state response** is the behavior of the circuit a long time after an external excitation is applied.

Eg = 7.15  
7.14  
Phoca book  
7.11

$$v(t) = V_s + (V_0 - V_s)e^{-t/\tau}, \quad t > 0$$


$t = 0, 1, 2, 3, \dots, \infty$

$$v(t) = \overset{V_s}{v(\infty)} + [v(0) - v(\infty)]e^{-t/\tau}$$



where  $v(0)$  is the initial voltage at  $t = 0^+$  and  $v(\infty)$  is the final or steady-state value. Thus, to find the step response of an  $RC$  circuit requires three things:

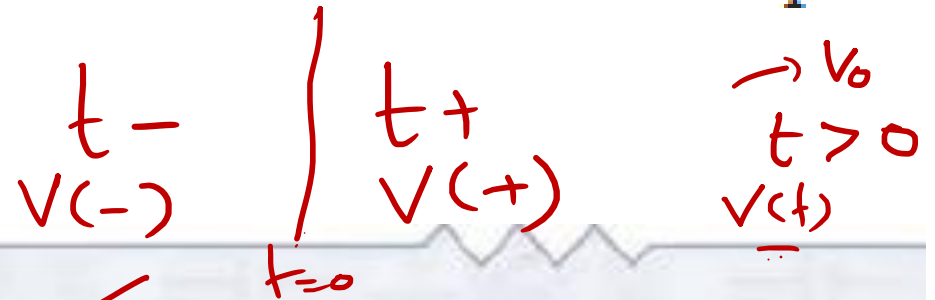1. The initial capacitor voltage  $v(0)$ .
2. The final capacitor voltage  $v(\infty)$ .
3. The time constant  $\tau$ .



Calculate the time taken by a capacitor  
 $1\mu\text{F}$  and in series with a  $1\text{M}\Omega$  resistance  
 to be charged up to  $80\%$  of the final value

$t = 1.6s$

$$C = Q/V ; Q = CV$$

$$V(t) = V_s (1 - e^{-t/RC})$$

$$CV(t) = CV_s [1 - e^{-t/RC}]$$

$$0.8 \times Q = Q [1 - e^{-t/RC}]$$

$$RC = 1 \times 10^{-6} \Omega \times 1 \times 10^6$$

$$Q = CV \quad C = Q/V$$

Charge stored in the  
 Capacitor during the  
 charging


$$0.8 = [1 - e^{-t}]$$



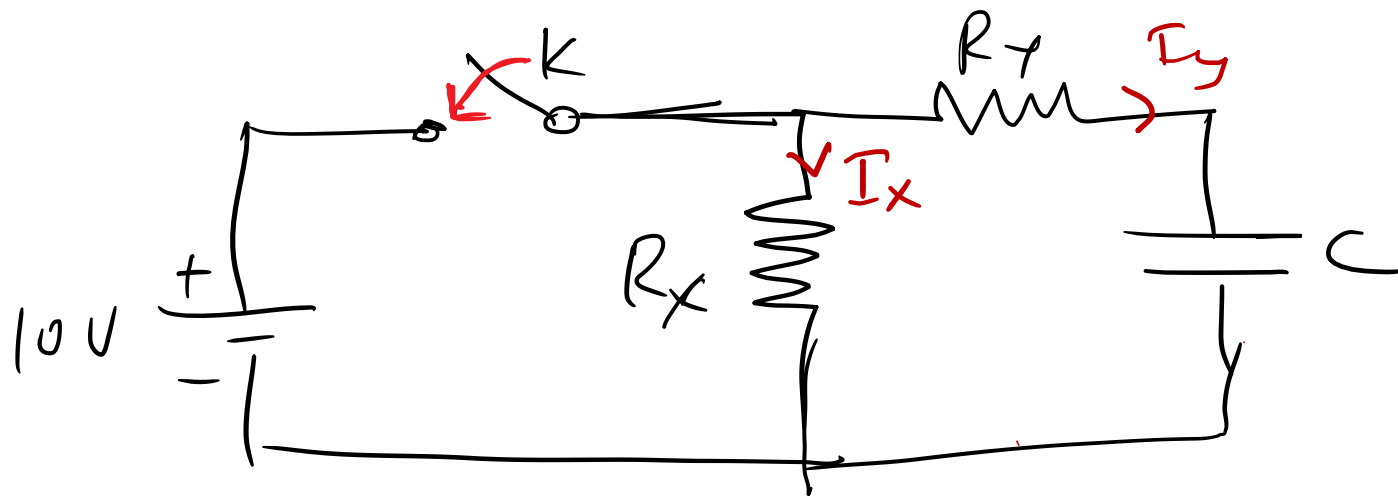A dc constant voltage source feeds a resistance of  $2000\text{ k}\Omega$  in series with a  $5\text{ }\mu\text{F}$  capacitor. Find the time taken for the capacitor when the charge retained will be decayed to 50% initial value, the voltage source being short circuited







Switch K is closed  
Find the time when  
the current  
from the battery  
reaches 500mA

$$I = I_x + I_y$$

$$500 = I_x + I_y$$

$$500 = \frac{10}{50} + I_y$$

$$I_y = \underline{\underline{300\text{mA}}}$$

$$R_x = 50\ \Omega$$

$$R_y = 70\ \Omega$$

$$C = 100\ \mu\text{F}$$

$$I_y = \frac{V}{R_y} (1 - e^{-t/\tau})$$

