




Nodal analysis applies KCL to find unknown voltages in a given circuit, while mesh analysis applies KVL to find unknown currents.

Mesh Analysis


Mesh analysis is also known as loop analysis or the mesh-current method.

- ❑ Loop is a closed path with no node passed more than once **OR**
Loop is a path for which the first node and last node are same
- ❑ A mesh is a loop does not contain any other loop with in it

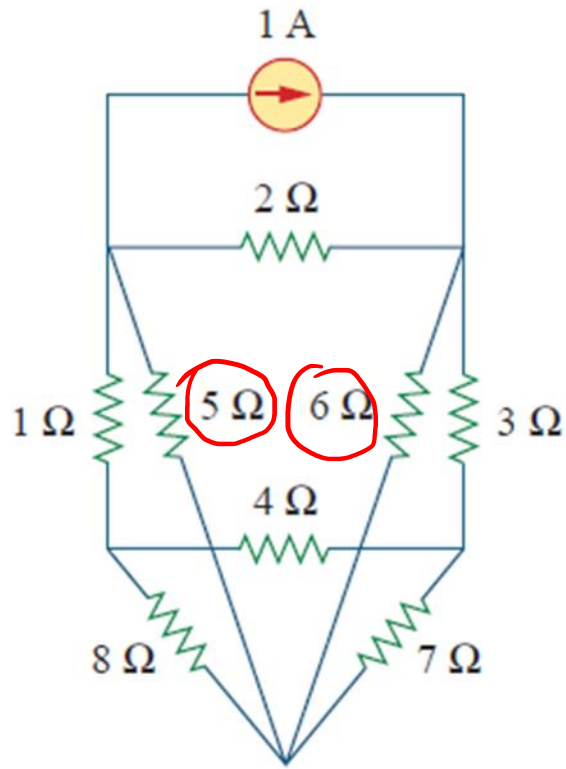
- ❑ Planar Circuit : A circuit can be drawn on a flat surface without crossed wires
- ❑ For planar circuits, we use the Mesh Current Method and write the equations based on meshes.




Planar

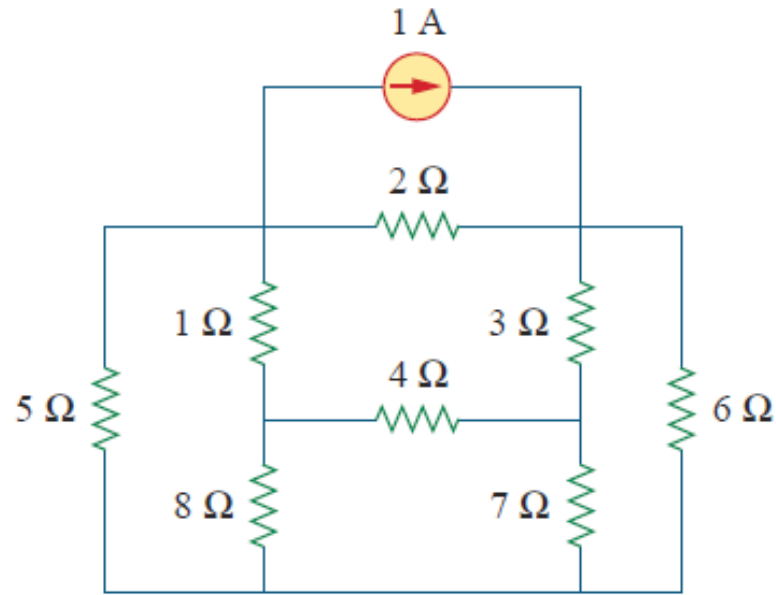


(b)

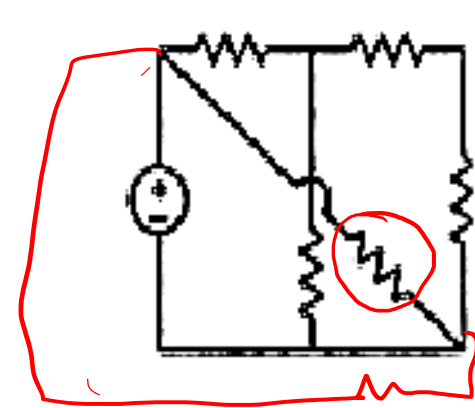


planar

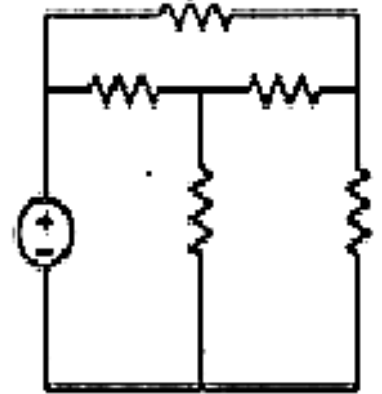

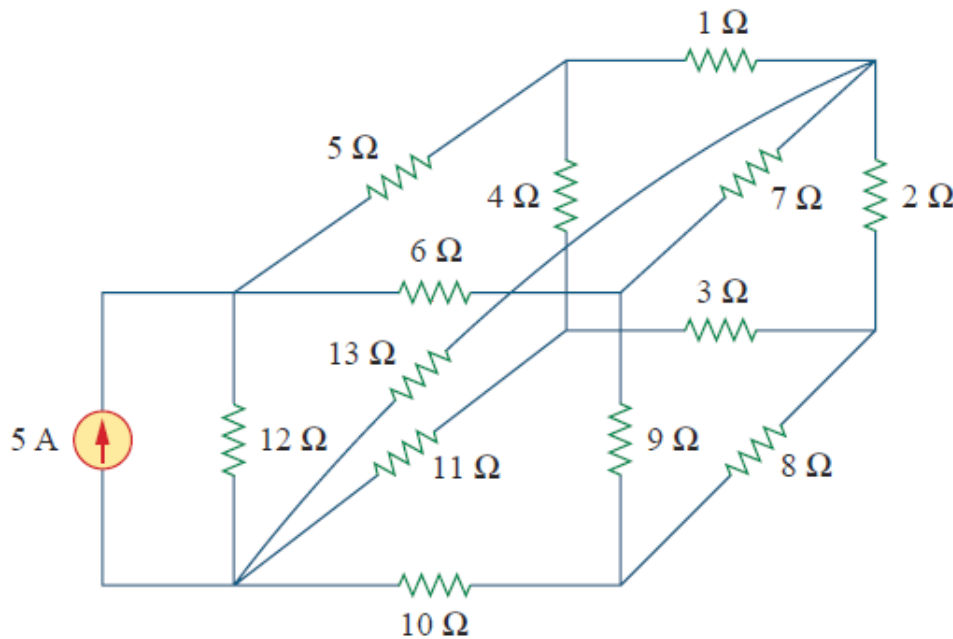- ❑ A non-planar circuit is one with at least one crossed wire
- ❑ Which cannot be drawn flat or no way to redraw the circuit to avoid a crossed wire




Non-planar

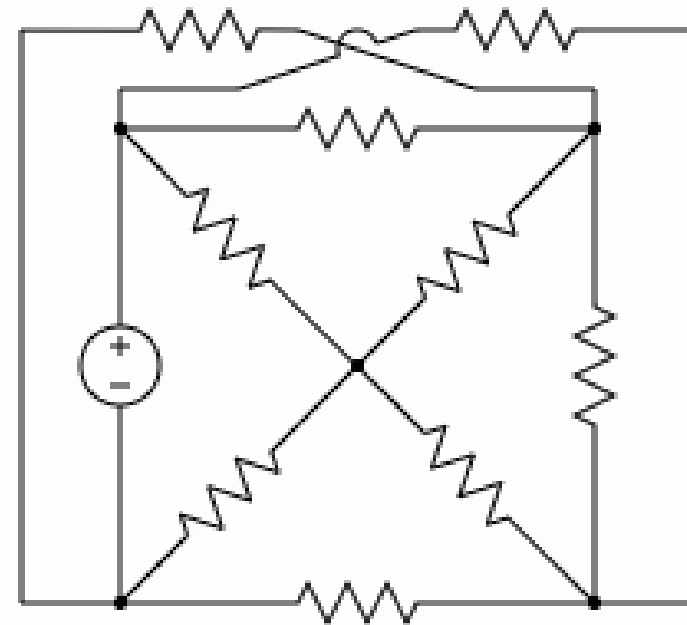

Non-planar

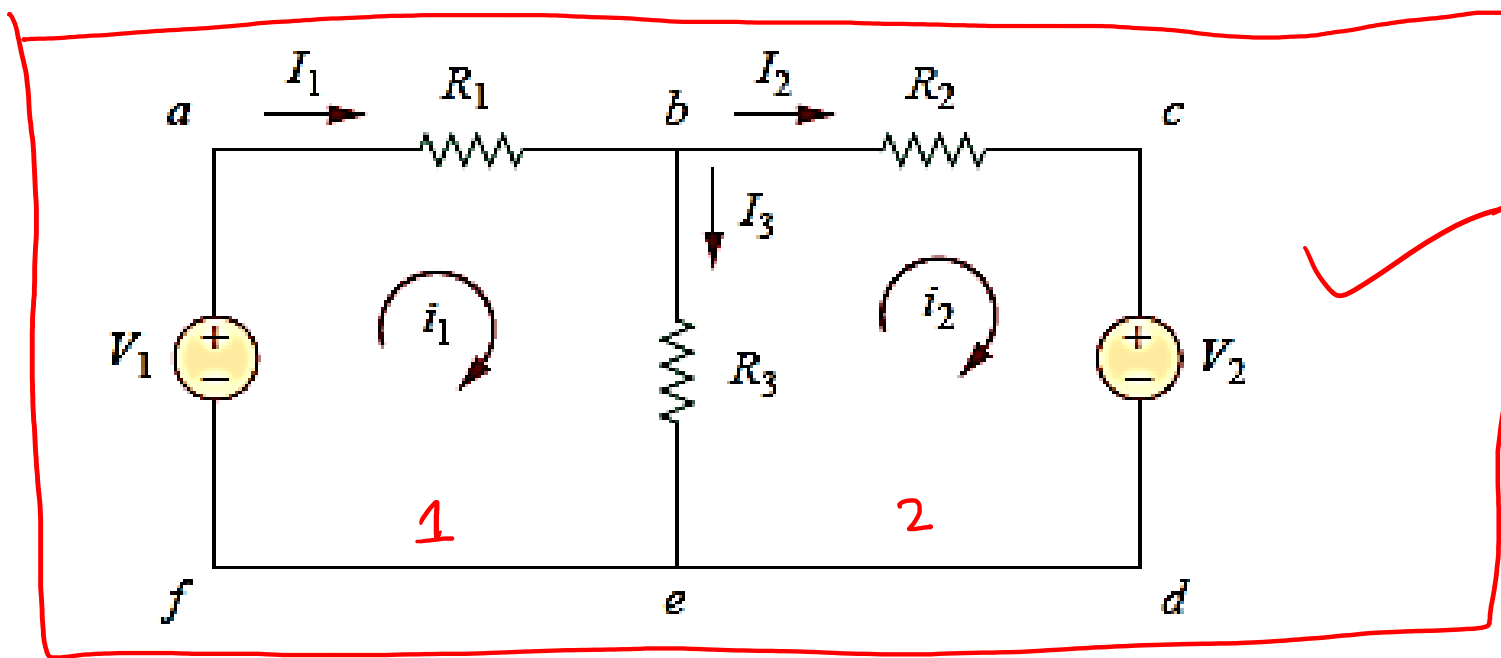A mesh is a loop which does not contain any other loops within it.




Steps to Determine Mesh Currents:

1. Assign mesh currents i_1, i_2, \dots, i_n to the n meshes.
2. Apply KVL to each of the n meshes. Use Ohm's law to express the voltages in terms of the mesh currents.
3. Solve the resulting n simultaneous equations to get the mesh currents.

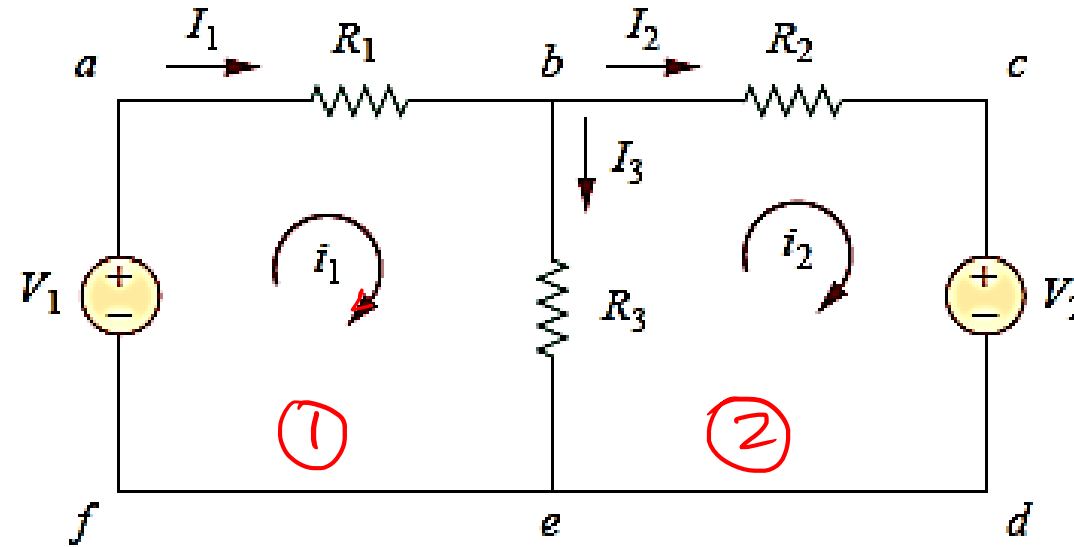1. Assign mesh currents i_1 , i_2 ,


$a b e f a$ — mesh 1
 $b c d e b$ → mesh 2



~~$a b c d e f a$~~

Outer loop cannot be considered as mesh because two loops are there within this loop

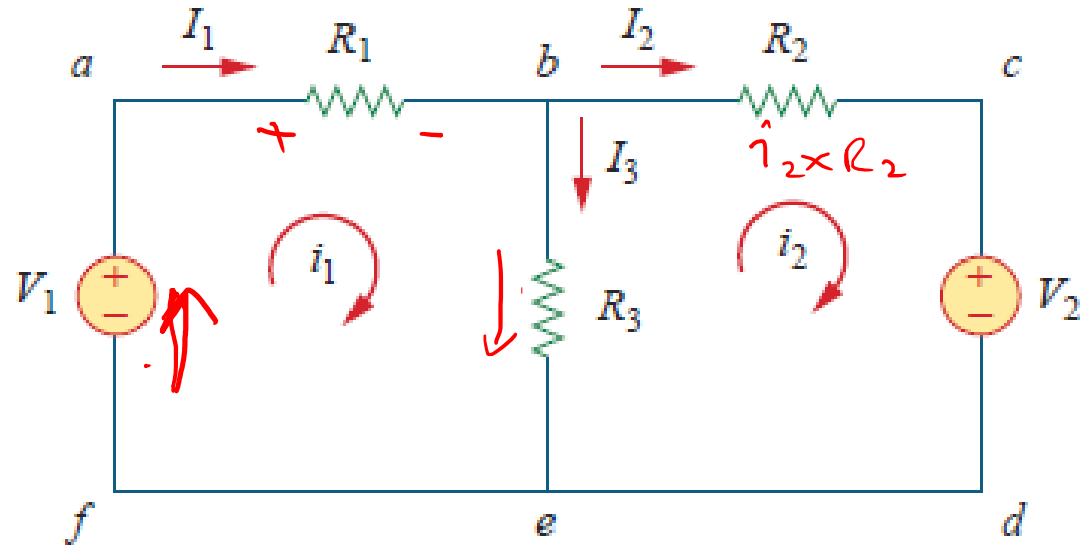2. Apply KVL to each of the n meshes. Use Ohm's law to express the voltages in terms of the mesh currents.



No of equations require to solve an electrical network using mesh analysis is equal to number of meshes

to mesh 1, we obtain

$$\underline{-V_1} + \underline{R_1 i_1} + \underline{R_3(i_1 - i_2)} = 0$$

or

$$(R_1 + R_3)i_1 - R_3i_2 = V_1$$

For mesh 2, applying KVL gives

$$\underline{R_2 i_2} + \underline{V_2} + R_3(i_2 - i_1) = 0$$

or

$$\checkmark -R_3 i_1 + (R_2 + R_3)i_2 = -V_2$$

3. Solve the resulting n simultaneous equations to get the mesh currents.


$$(R_1 + R_3)i_1 - R_3i_2 = V_1 \longrightarrow \textcircled{1}$$

$$-R_3i_1 + (R_2 + R_3)i_2 = -V_2 \longrightarrow \textcircled{2}$$

$$\begin{bmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ -V_2 \end{bmatrix}$$

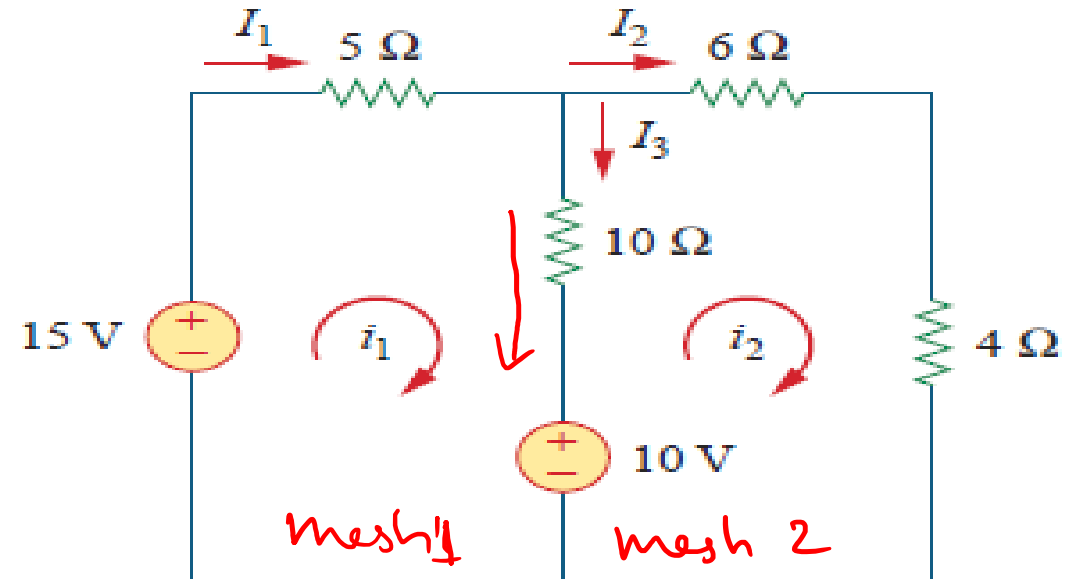Example

For the circuit in Fig. find the branch currents $\underline{I_1}$, $\underline{I_2}$, and $\underline{I_3}$ using mesh analysis.



We first obtain the mesh currents using KVL. For mesh 1,

$$\Rightarrow -15 + 5i_1 + 10(i_1 - i_2) + 10 = 0$$

or

$$3i_1 - 2i_2 = 1 \quad \checkmark \longrightarrow \textcircled{1}$$

For mesh 2,

$$\Rightarrow 6i_2 + 4i_2 + 10(i_2 - i_1) - 10 = 0$$

or

$$i_1 = 2i_2 - 1 \quad \checkmark \longrightarrow \textcircled{2}$$

$$i_2 - i_1$$

■ **METHOD 1** Using the substitution method, we substitute Eq. (3.5.2) into Eq. (3.5.1), and write

$$6i_2 - 3 - 2i_2 = 1 \quad \Rightarrow \quad i_2 = 1 \text{ A}$$

From Eq. (3.5.2), $i_1 = 2i_2 - 1 = 2 - 1 = 1 \text{ A}$. Thus,

$$I_1 = i_1 = \underline{1 \text{ A}}, \quad I_2 = \underline{i_2} = \underline{1 \text{ A}}, \quad I_3 = i_1 - i_2 = 0$$

■ **METHOD 2** To use Cramer's rule,

$$\begin{bmatrix} 3 & -2 \\ -1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \end{bmatrix} \quad \checkmark$$

We obtain the determinants

$$\Delta = \begin{vmatrix} 3 & -2 \\ -1 & 2 \end{vmatrix} = 6 - 2 = 4$$


$$\Delta_1 = \begin{vmatrix} 1 & -2 \\ 1 & 2 \end{vmatrix} = 2 + 2 = 4, \quad \Delta_2 = \begin{vmatrix} 3 & 1 \\ -1 & 1 \end{vmatrix} = 3 + 1 = 4$$


Thus,

$$i_1 = \frac{\Delta_1}{\Delta} = 1 \text{ A}, \quad i_2 = \frac{\Delta_2}{\Delta} = 1 \text{ A} \quad \checkmark$$

as before.

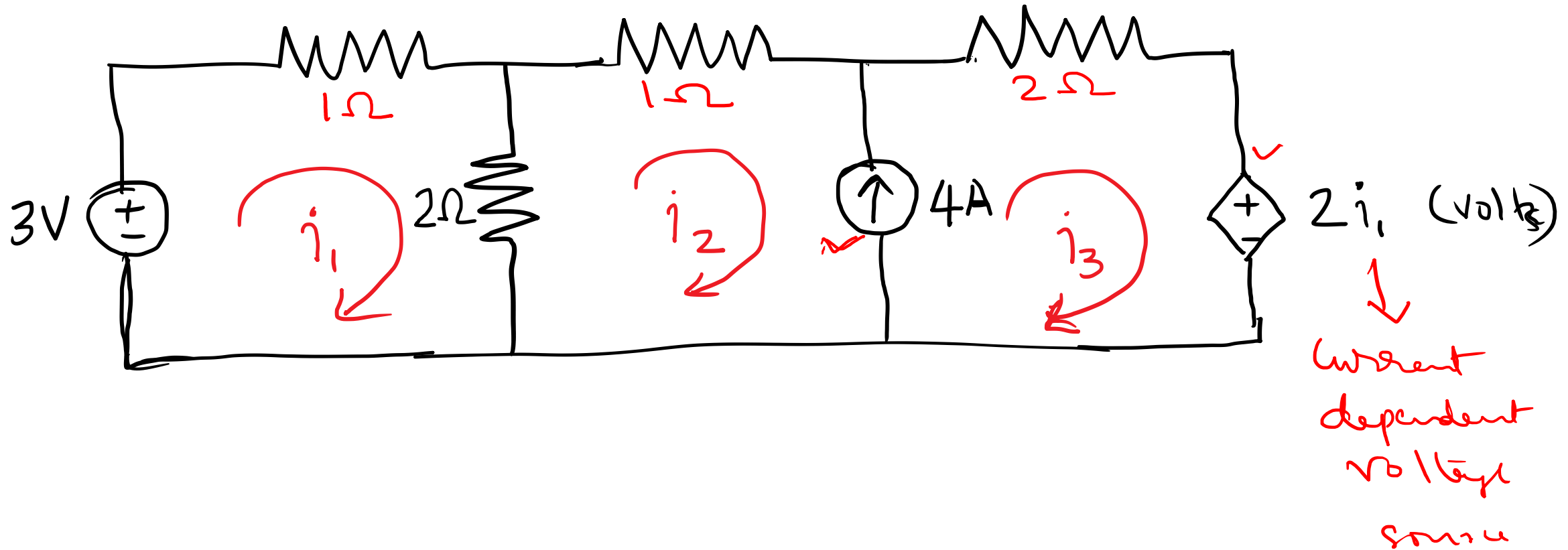Find the loop currents i_1 , i_2 and i_3 in the network (use mesh analysis)



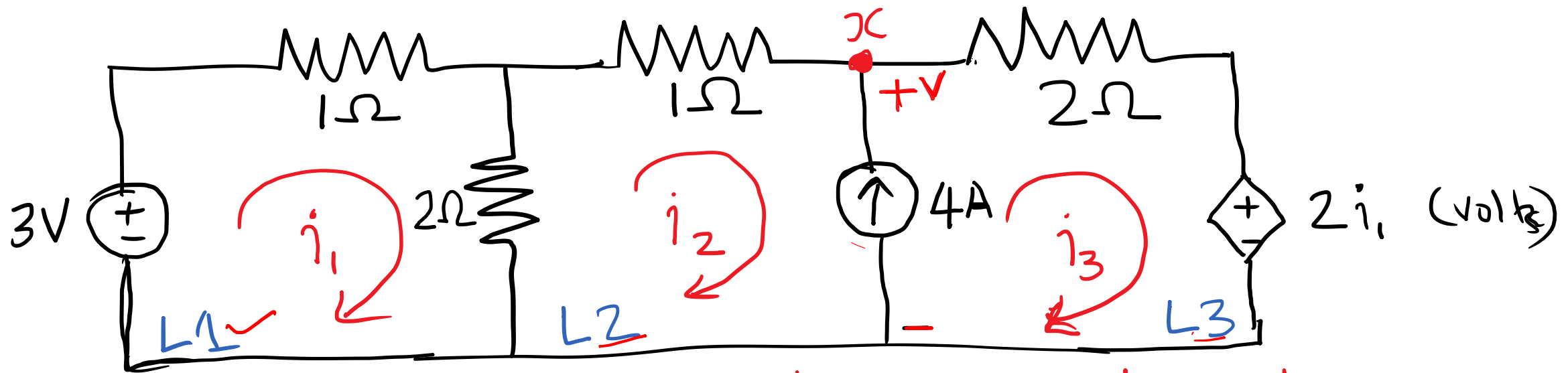

v is the assumed voltage at node x .

KVL in $L1$

$$i_1 \times 1 + (i_1 - i_2) \times 2 - 3 = 0$$

$$3i_1 - 2i_2 = 3 \rightarrow \textcircled{1}$$

KVL in $L2$

$$(i_2 - i_1) \times 2 + i_2 \times 1 + v = 0$$

$$3i_2 - i_1 + v = 0$$

$\rightarrow \textcircled{2}$

KVL in $L3$

$$-v + 2i_3 + 2i_1 = 0$$


$$2i_3 + 2i_1 = v$$

$\rightarrow \textcircled{3}$

Use $\textcircled{3}$ in $\textcircled{2}$ and solve $\Rightarrow i_1 = -\frac{1}{17} \text{ A} ; i_2 = -\frac{27}{17} \text{ A} ; i_3 = \frac{41}{17} \text{ A}$

Mesh Analysis with Current Sources

Nodal Analysis with Voltage Sources

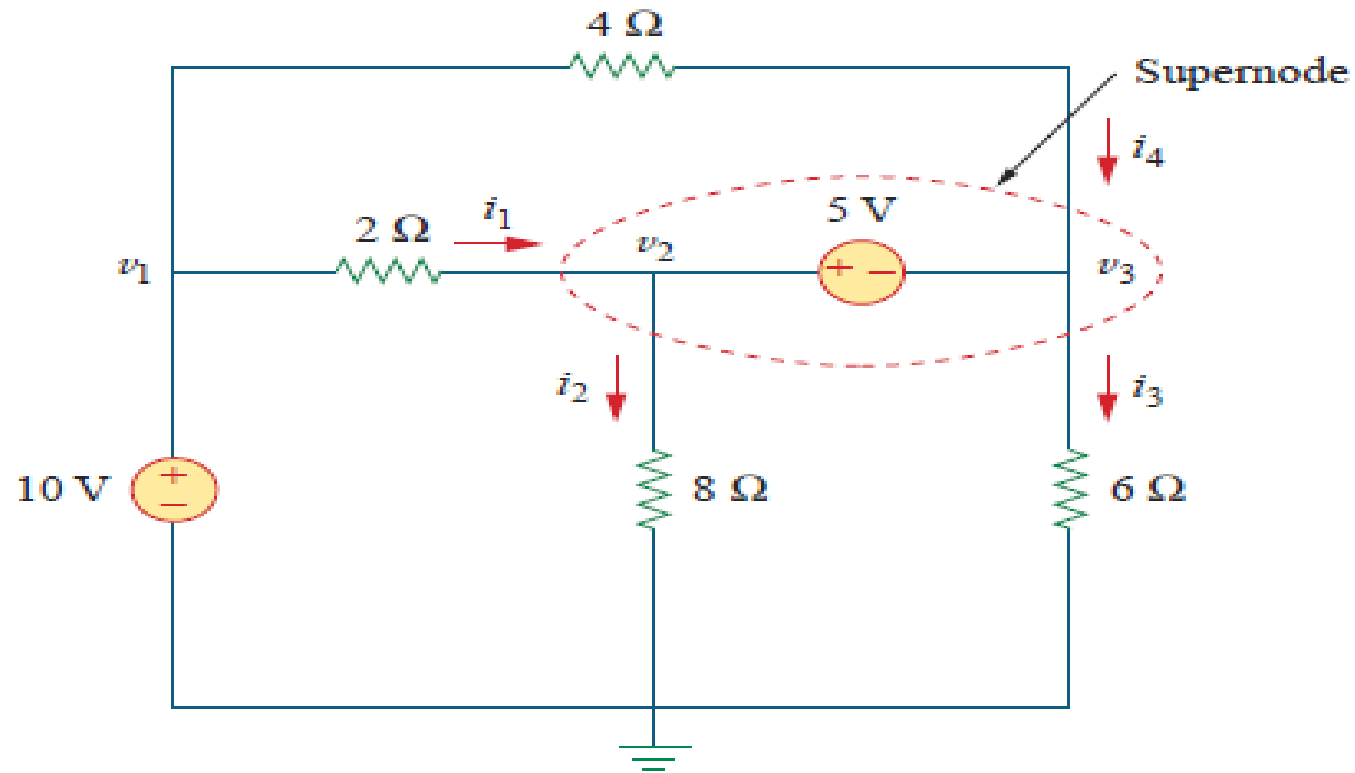

DA 1
Q 1

A **supernode** is formed by enclosing a (dependent or independent) voltage source connected between two nonreference nodes and any elements connected in parallel with it.