

## † Relationships Between Parameters

Given the  $z$  parameters, let us obtain the  $y$  parameters.

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{z}_{11} & \mathbf{z}_{12} \\ \mathbf{z}_{21} & \mathbf{z}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = [\mathbf{z}] \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix}$$

$$\begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{y}_{11} & \mathbf{y}_{12} \\ \mathbf{y}_{21} & \mathbf{y}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = [\mathbf{y}] \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix}$$

$$\begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = [\mathbf{z}]^{-1} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix}$$

$$[\mathbf{y}] = [\mathbf{z}]^{-1}$$

The adjoint of the  $[z]$  matrix is

$$= \begin{bmatrix} z_{22} & -z_{12} \\ -z_{21} & z_{11} \end{bmatrix}$$

and its determinant is  $(z)$

$$\Delta_z = z_{11}z_{22} - z_{12}z_{21}$$

$$[y] = [z]^{-1}$$

$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} = \frac{\begin{bmatrix} z_{22} & -z_{12} \\ -z_{21} & z_{11} \end{bmatrix}}{\Delta_z} = \begin{bmatrix} \frac{z_{22}}{\Delta_z} & -\frac{z_{12}}{\Delta_z} \\ -\frac{z_{21}}{\Delta_z} & \frac{z_{11}}{\Delta_z} \end{bmatrix}$$

$$y_{11} = \frac{z_{22}}{\Delta_z}, \quad y_{12} = -\frac{z_{12}}{\Delta_z}, \quad y_{21} = -\frac{z_{21}}{\Delta_z}, \quad y_{22} = \frac{z_{11}}{\Delta_z}$$

let us determine the h parameters from the z parameters.

$$\mathbf{V}_1 = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2 \quad \checkmark$$

$$\mathbf{V}_2 = \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}\mathbf{I}_2 \quad \checkmark$$

$$\mathbf{V}_1 = \frac{\mathbf{z}_{11}\mathbf{z}_{22} - \mathbf{z}_{12}\mathbf{z}_{21}}{\mathbf{z}_{22}}\mathbf{I}_1 + \frac{\mathbf{z}_{12}}{\mathbf{z}_{22}}\mathbf{V}_2$$

$$\mathbf{I}_2 = -\frac{\mathbf{z}_{21}}{\mathbf{z}_{22}}\mathbf{I}_1 + \frac{1}{\mathbf{z}_{22}}\mathbf{V}_2$$

$$\mathbf{h}_{11} = \frac{\Delta_z}{\mathbf{z}_{22}},$$

$$\mathbf{h}_{12} = \frac{\mathbf{z}_{12}}{\mathbf{z}_{22}},$$

$$\mathbf{h}_{21} = -\frac{\mathbf{z}_{21}}{\mathbf{z}_{22}},$$

$$\mathbf{h}_{22} = \frac{1}{\mathbf{z}_{22}}$$

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} \frac{\Delta_z}{\mathbf{z}_{22}} & \frac{\mathbf{z}_{12}}{\mathbf{z}_{22}} \\ -\frac{\mathbf{z}_{21}}{\mathbf{z}_{22}} & \frac{1}{\mathbf{z}_{22}} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{V}_2 \end{bmatrix}$$

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{h}_{11} & \mathbf{h}_{12} \\ \mathbf{h}_{21} & \mathbf{h}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{V}_2 \end{bmatrix}$$

	<b>z</b>	<b>y</b>	<b>h</b>
<b>z</b>	$\begin{array}{cc} z_{11} & z_{12} \\ z_{21} & z_{22} \end{array}$	$\begin{array}{cc} \frac{y_{22}}{\Delta_y} & -\frac{y_{12}}{\Delta_y} \\ \frac{y_{21}}{\Delta_y} & -\frac{y_{11}}{\Delta_y} \end{array}$	$\begin{array}{cc} \frac{\Delta_h}{h_{22}} & -\frac{h_{12}}{h_{22}} \\ \frac{h_{21}}{h_{22}} & \frac{1}{h_{22}} \end{array}$
<b>y</b>	$\begin{array}{cc} \frac{z_{22}}{\Delta_z} & -\frac{z_{12}}{\Delta_z} \\ \frac{z_{21}}{\Delta_z} & -\frac{z_{11}}{\Delta_z} \end{array}$	$\begin{array}{cc} y_{11} & y_{12} \\ y_{21} & y_{22} \end{array}$	$\begin{array}{cc} \frac{1}{h_{11}} & -\frac{h_{12}}{h_{11}} \\ \frac{h_{21}}{h_{11}} & \frac{\Delta_h}{h_{11}} \end{array}$
<b>h</b>	$\begin{array}{cc} \frac{\Delta_z}{z_{22}} & \frac{z_{12}}{z_{22}} \\ \frac{z_{21}}{z_{22}} & \frac{1}{z_{22}} \end{array}$	$\begin{array}{cc} \frac{1}{y_{11}} & -\frac{y_{12}}{y_{11}} \\ \frac{y_{21}}{y_{11}} & -\frac{\Delta_y}{y_{11}} \end{array}$	$\begin{array}{cc} h_{11} & h_{12} \\ h_{21} & h_{22} \end{array}$
<b>g</b>	$\begin{array}{cc} \frac{1}{z_{11}} & -\frac{z_{12}}{z_{11}} \\ \frac{z_{21}}{z_{11}} & \frac{\Delta_z}{z_{11}} \\ \frac{z_{11}}{z_{11}} & \frac{z_{11}}{z_{11}} \end{array}$	$\begin{array}{cc} \frac{\Delta_y}{y_{22}} & -\frac{y_{12}}{y_{22}} \\ \frac{y_{21}}{y_{22}} & \frac{1}{y_{22}} \\ \frac{y_{22}}{y_{22}} & \frac{y_{22}}{y_{22}} \end{array}$	$\begin{array}{cc} \frac{h_{22}}{\Delta_h} & -\frac{h_{12}}{\Delta_h} \\ \frac{h_{21}}{\Delta_h} & \frac{h_{11}}{\Delta_h} \\ \frac{\Delta_h}{\Delta_h} & \frac{\Delta_h}{\Delta_h} \end{array}$

$$\Delta_z = z_{11}z_{22} - z_{12}z_{21},$$

$$\Delta_y = y_{11}y_{22} - y_{12}y_{21},$$


$$\Delta_h = h_{11}h_{22} - h_{12}h_{21},$$

$$\Delta_g = g_{11}g_{22} - g_{12}g_{21},$$


# Interconnection of Networks

- A large, complex network may be divided into subnetworks for the purposes of analysis and design.
- The subnet works are modeled as two port networks, interconnected to form the original network.
- The two-port networks are building blocks a complex network.
- The interconnection can be in series, in parallel, or in cascade.
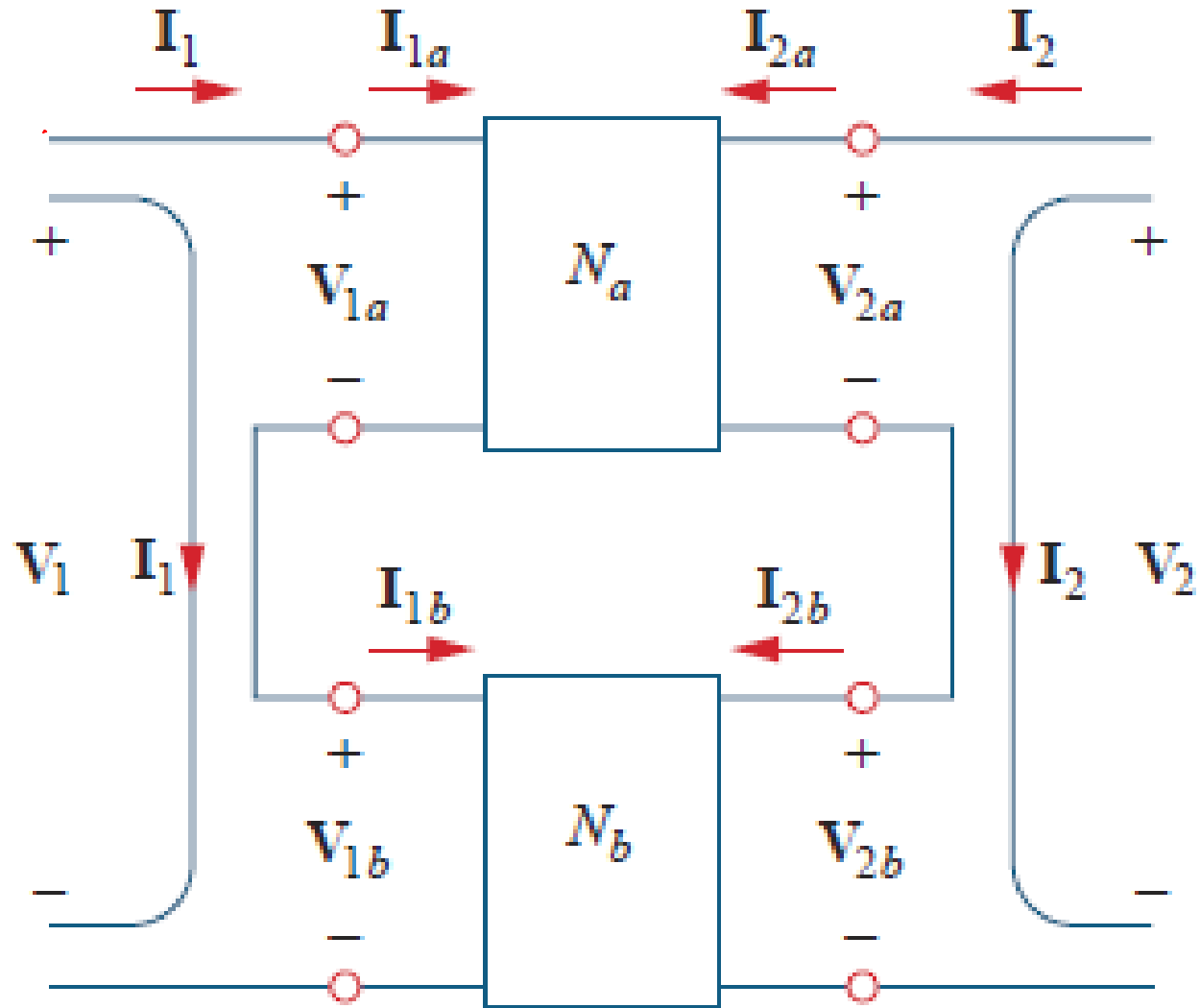
## Series connection of two two-port networks



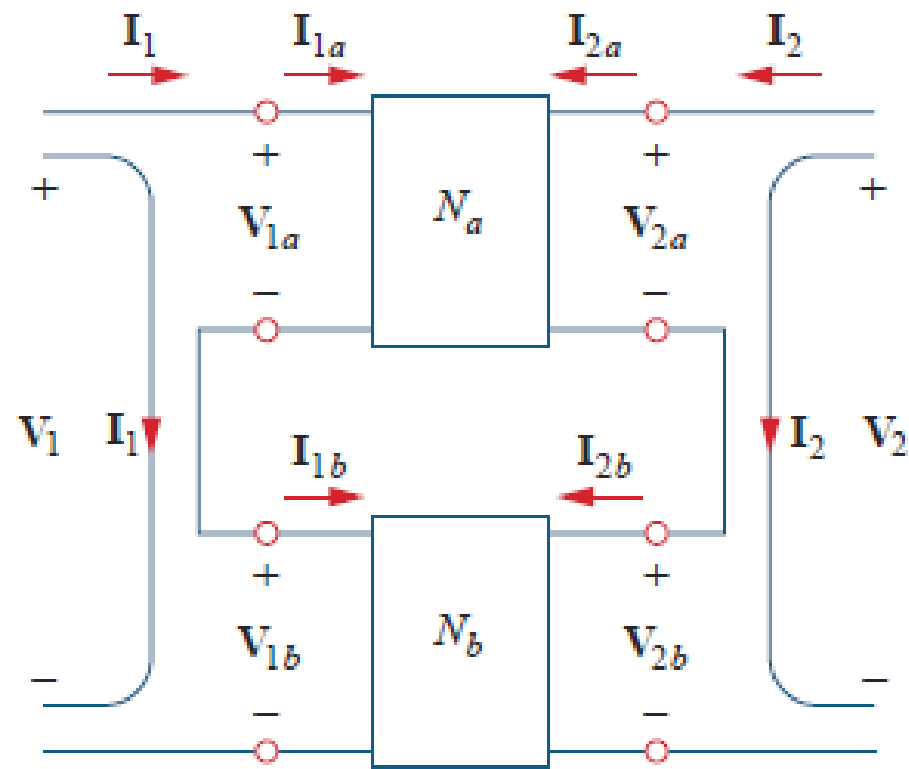- The networks are regarded as being in series because their input currents are the same and their voltages add.
- In addition, each network has a common reference, and when the circuits are placed in series, the common reference points of each circuit are connected together.



$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$

For network  $N_a$ ,

$$V_{1a} = z_{11a}I_{1a} + z_{12a}I_{2a}$$

$$V_{2a} = z_{21a}I_{1a} + z_{22a}I_{2a}$$

for network  $N_b$ ,

$$V_{1b} = z_{11b}I_{1b} + z_{12b}I_{2b}$$

$$V_{2b} = z_{21b}I_{1b} + z_{22b}I_{2b}$$

$$I_1 = I_{1a} = I_{1b}, \quad I_2 = I_{2a} = I_{2b}$$

$$V_1 = V_{1a} + V_{1b} = (z_{11a} + z_{11b})I_1 + (z_{12a} + z_{12b})I_2 \checkmark$$

$$V_2 = V_{2a} + V_{2b} = (z_{21a} + z_{21b})I_1 + (z_{22a} + z_{22b})I_2 \checkmark$$

$$\mathbf{V}_1 = \mathbf{V}_{1a} + \mathbf{V}_{1b} = (\mathbf{z}_{11a} + \mathbf{z}_{11b})\mathbf{I}_1 + (\mathbf{z}_{12a} + \mathbf{z}_{12b})\mathbf{I}_2$$

$$\mathbf{V}_2 = \mathbf{V}_{2a} + \mathbf{V}_{2b} = (\mathbf{z}_{21a} + \mathbf{z}_{21b})\mathbf{I}_1 + (\mathbf{z}_{22a} + \mathbf{z}_{22b})\mathbf{I}_2$$

Thus, the  $z$  parameters for the overall network are

$$\begin{bmatrix} \mathbf{z}_{11} & \mathbf{z}_{12} \\ \mathbf{z}_{21} & \mathbf{z}_{22} \end{bmatrix} = \begin{bmatrix} \mathbf{z}_{11a} + \mathbf{z}_{11b} & \mathbf{z}_{12a} + \mathbf{z}_{12b} \\ \mathbf{z}_{21a} + \mathbf{z}_{21b} & \mathbf{z}_{22a} + \mathbf{z}_{22b} \end{bmatrix} \checkmark$$

or


$$[\mathbf{z}] = [\mathbf{z}_a] + [\mathbf{z}_b]$$




- The  $z$  parameters for the overall network are the sum of the  $z$  parameters for the individual networks.
- This can be extended to  $n$  networks in series.
- If two two-port networks in the  $h$  model, for example, are connected in series, we use Table given before to convert the  $[h]$  to  $[z]$  and then apply above equation. Finally convert the results back to  $[h]$  using the table
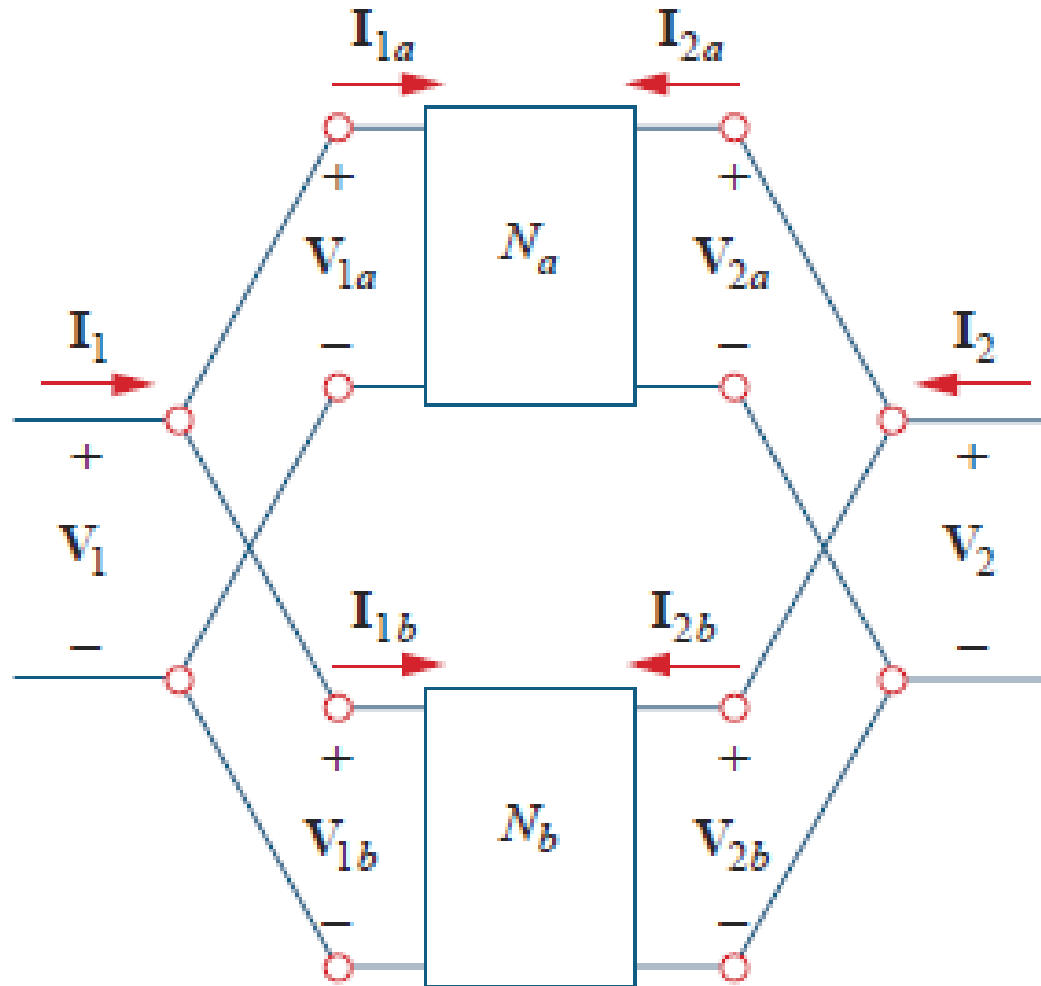
## Two-port networks in parallel.

- Two two-port networks are in parallel when their port voltages are equal
- The port currents of the larger network are the sums of the individual port currents.



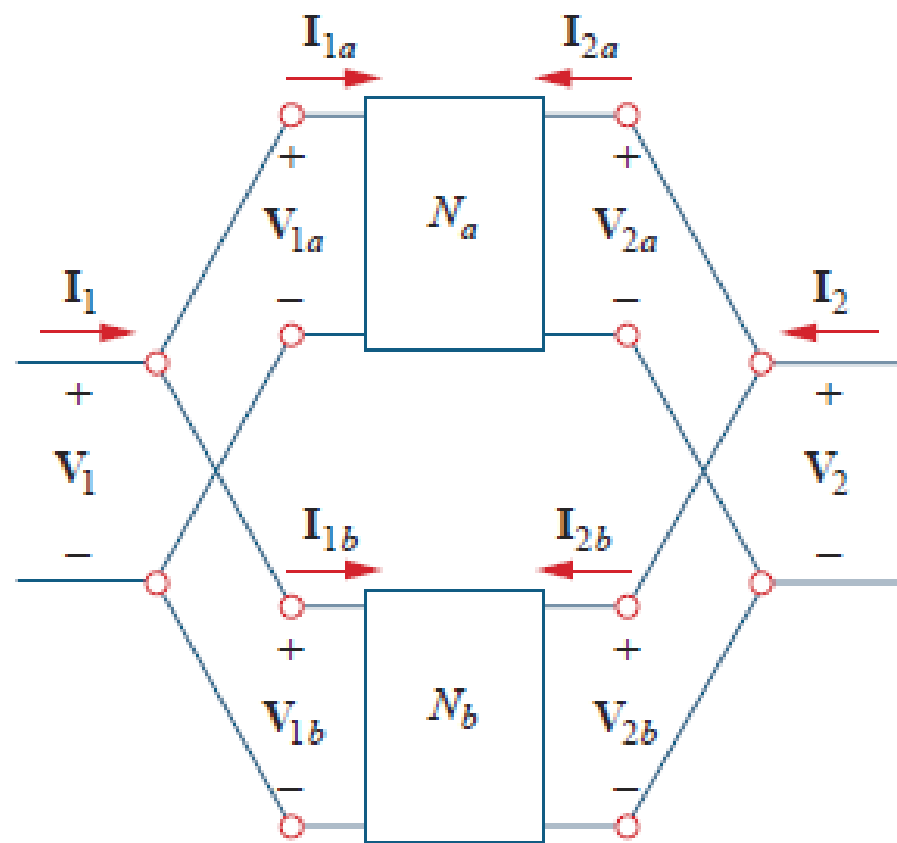

$$\mathbf{I}_1 = y_{11}\mathbf{V}_1 + y_{12}\mathbf{V}_2$$

$$\mathbf{I}_2 = y_{21}\mathbf{V}_1 + y_{22}\mathbf{V}_2$$

$$\mathbf{I}_{1a} = y_{11a}\mathbf{V}_{1a} + y_{12a}\mathbf{V}_{2a}$$

$$\mathbf{I}_{2a} = y_{21a}\mathbf{V}_{1a} + y_{22a}\mathbf{V}_{2a}$$

$$\mathbf{I}_{1b} = y_{11b}\mathbf{V}_{1b} + y_{12b}\mathbf{V}_{2b}$$

$$\mathbf{I}_{2a} = y_{21b}\mathbf{V}_{1b} + y_{22b}\mathbf{V}_{2b}$$

$$\mathbf{V}_1 = \mathbf{V}_{1a} = \mathbf{V}_{1b},$$

$$\mathbf{V}_2 = \mathbf{V}_{2a} = \mathbf{V}_{2b}$$

$$\mathbf{I}_1 = \mathbf{I}_{1a} + \mathbf{I}_{1b},$$

$$\mathbf{I}_2 = \mathbf{I}_{2a} + \mathbf{I}_{2b}$$

$$\mathbf{I}_1 = (y_{11a} + y_{11b})\mathbf{V}_1 + (y_{12a} + y_{12b})\mathbf{V}_2$$

$$\mathbf{I}_2 = (y_{21a} + y_{21b})\mathbf{V}_1 + (y_{22a} + y_{22b})\mathbf{V}_2$$


Thus, the  $y$  parameters for the overall network are

$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} = \begin{bmatrix} y_{11a} + y_{11b} & y_{12a} + y_{12b} \\ y_{21a} + y_{21b} & y_{22a} + y_{22b} \end{bmatrix}$$

$$[\mathbf{y}] = [\mathbf{y}_a] + [\mathbf{y}_b]$$
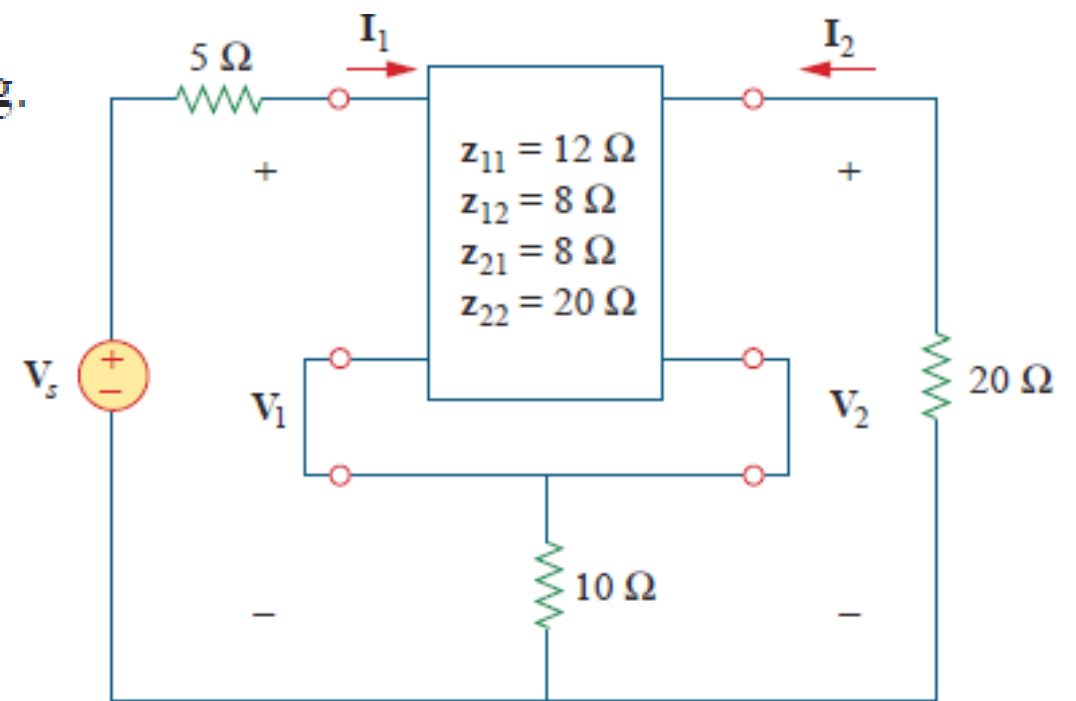
## Example

Evaluate  $V_2/V_s$  in the circuit in Fig.



$$V_1 = z_{11}I_1 + z_{12}I_2 = 22I_1 + 18I_2 \rightarrow \textcircled{1}$$


$$V_2 = z_{21}I_1 + z_{22}I_2 = 18I_1 + 30I_2 \rightarrow \textcircled{2}$$

This may be regarded as two two-ports in series. For  $N_b$ ,

$$z_{12b} = z_{21b} = 10 = z_{11b} = z_{22b}$$

Thus,
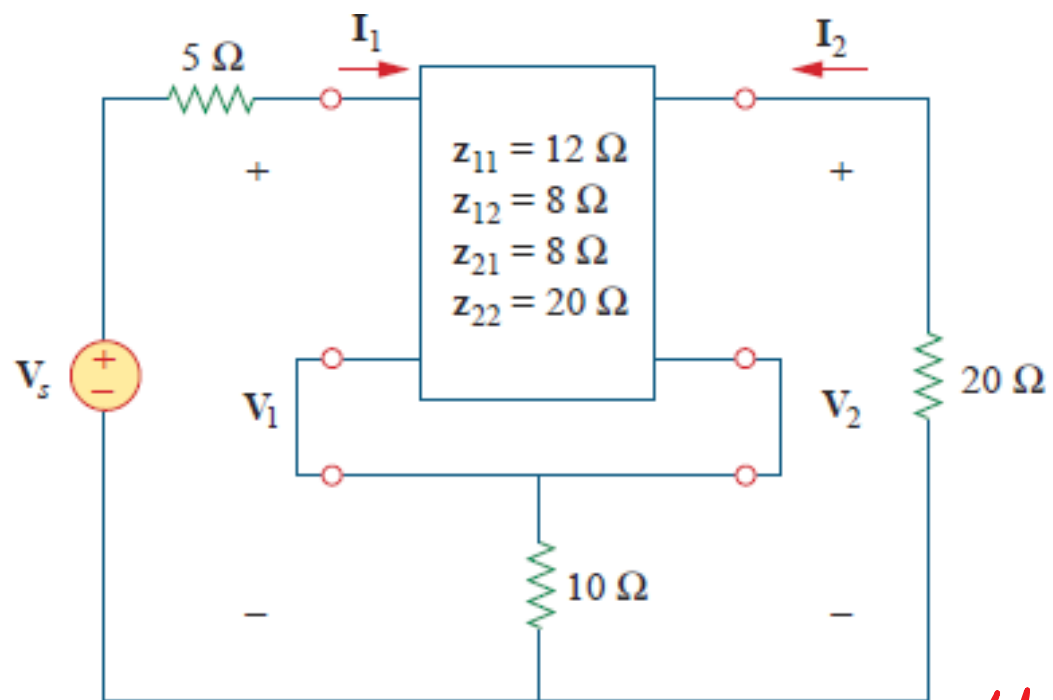
$$[z] = [z_a] + [z_b] = \begin{bmatrix} 12 & 8 \\ 8 & 20 \end{bmatrix} + \begin{bmatrix} 10 & 10 \\ 10 & 10 \end{bmatrix} = \begin{bmatrix} 22 & 18 \\ 18 & 30 \end{bmatrix}$$



Also, at the input port

$$V_1 = V_s - 5I_1 \longrightarrow \textcircled{3}$$

and at the output port

$$V_2 = -20I_2 \Rightarrow I_2 = -\frac{V_2}{20} \longrightarrow \textcircled{4}$$

Using  $\textcircled{3}$  &  $\textcircled{4}$  in  $\textcircled{1}$

$$V_s - 5I_1 = 22I_1 - \frac{18}{20}V_2 \Rightarrow V_s = 27I_1 - 0.9V_2 \longrightarrow \textcircled{5}$$


Using  $\textcircled{4}$  in  $\textcircled{2}$

$$V_2 = 18I_1 - \frac{30}{20}V_2 \Rightarrow I_1 = \frac{2.5}{18}V_2 \longrightarrow \textcircled{6}$$

Using (6) in (5)


$$V_s = 27 \times \frac{2.5}{18} V_2 - 0.9 V_2 = 2.85 V_2$$

And so,

$$\frac{V_2}{V_s} = \frac{1}{2.85} = 0.3509$$


## Practice Problem 19.12

Find  $V_2/V_s$  in the circuit in Fig. 19.43.

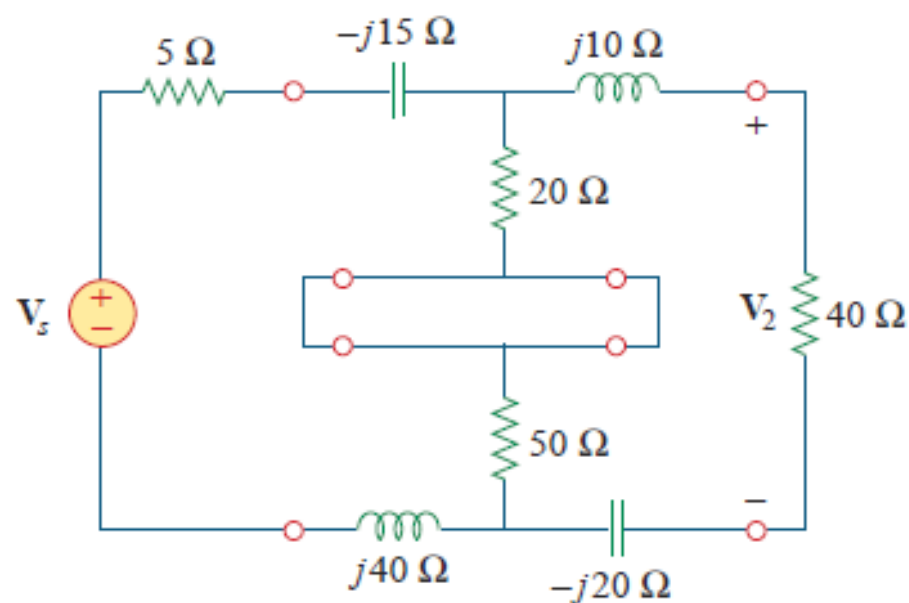


**Figure 19.43**  
For Practice Prob. 19.12.

**Answer:**  $0.6799 \angle -29.05^\circ$ .



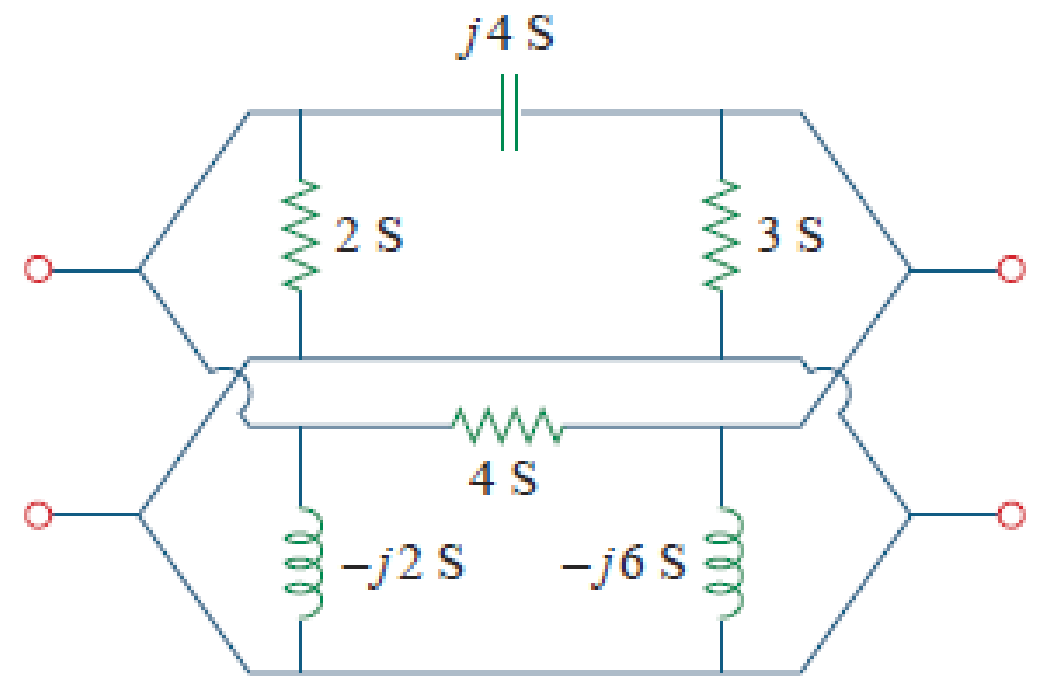
### Example

Find the  $y$  parameters of the two-port in Fig.




$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

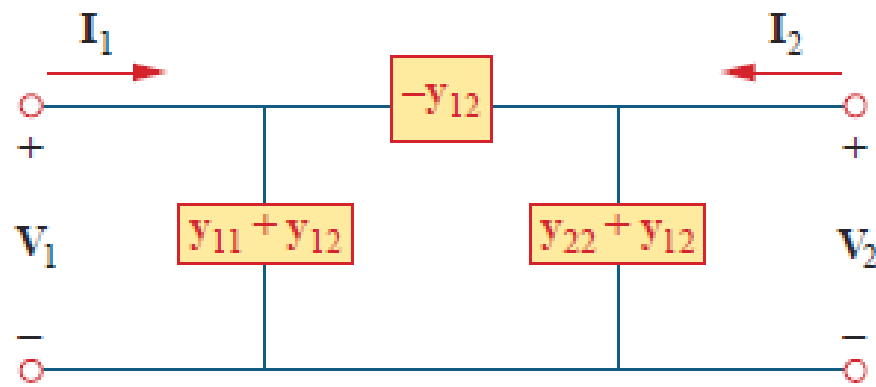


(a)

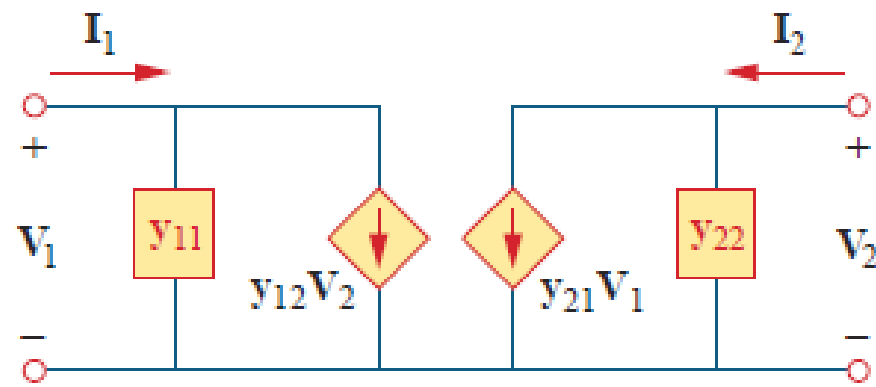


(b)

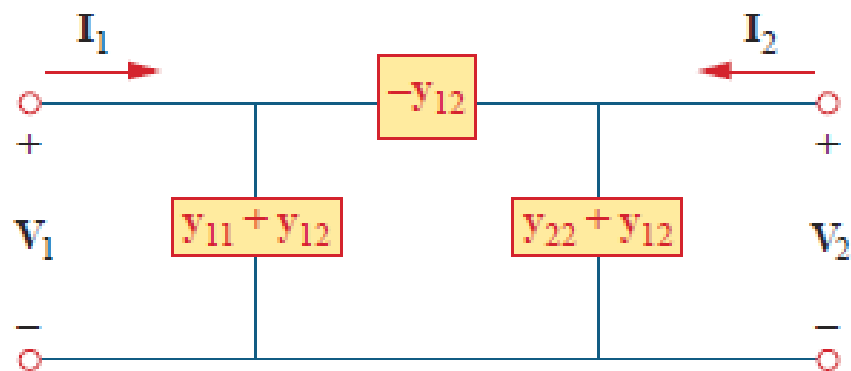(a)  $\Pi$ -equivalent circuit (for reciprocal case only), (b) general equivalent circuit.



$$y_{12a} = -j4 = y_{21a}, \quad y_{11a} = 2 + j4, \quad y_{22a} = 3 + j4$$
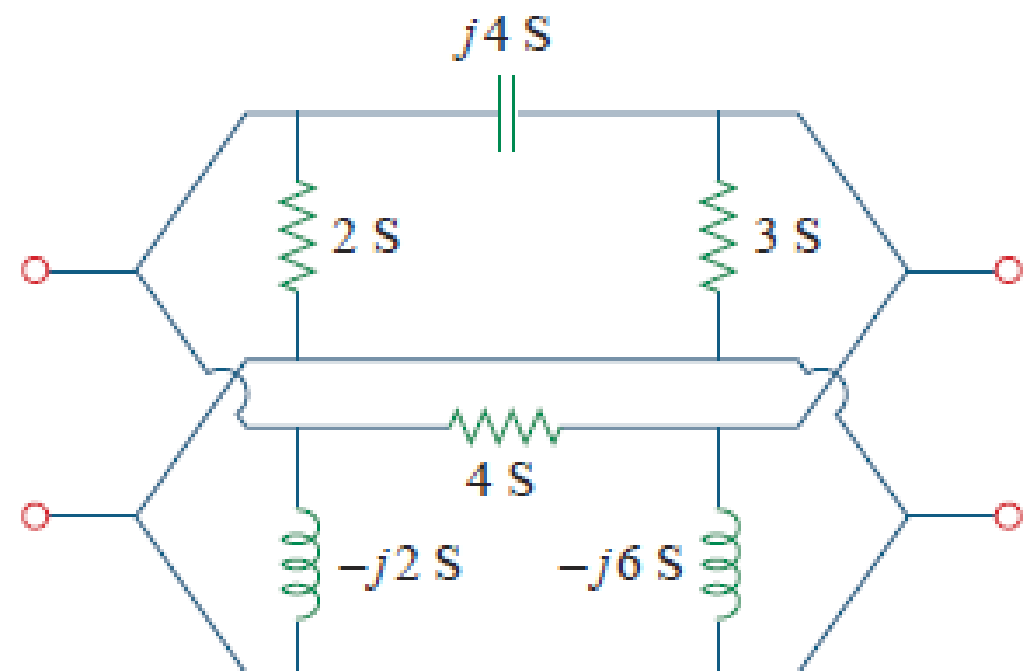
$$[y_a] = \begin{bmatrix} 2 + j4 & -j4 \\ -j4 & 3 + j4 \end{bmatrix} \text{ S}$$



$$y_{12b} = -4 = y_{21b}, \quad y_{11b} = 4 - j2, \quad y_{22b} = 4 - j6$$


$$[y_b] = \begin{bmatrix} 4 - j2 & -4 \\ -4 & 4 - j6 \end{bmatrix} \text{ S}$$

The overall  $y$  parameters are

$$[y] = [y_a] + [y_b] = \begin{bmatrix} 6 + j2 & -4 - j4 \\ -4 - j4 & 7 - j2 \end{bmatrix} S$$
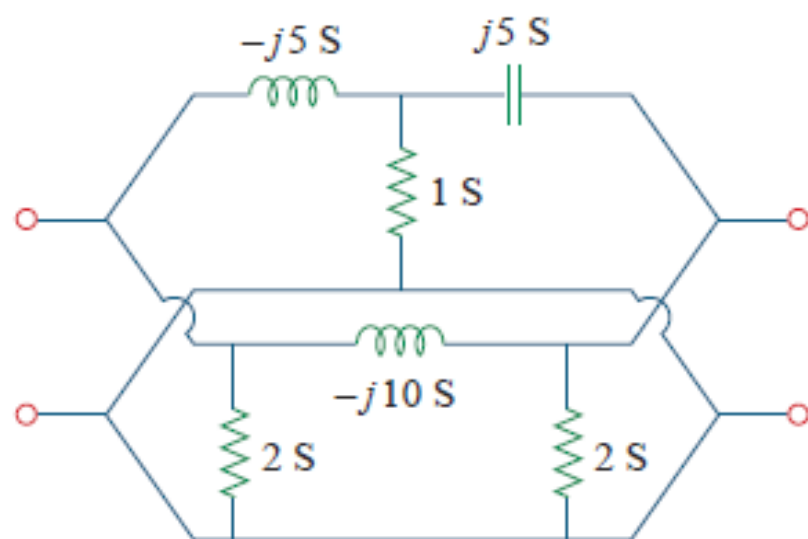
### Practice Problem 19.13

Obtain the  $y$  parameters for the network in Fig. 19.45.



**Answer:**  $\begin{bmatrix} 27 - j15 & -25 + j10 \\ -25 + j10 & 27 - j5 \end{bmatrix} \text{ S.}$