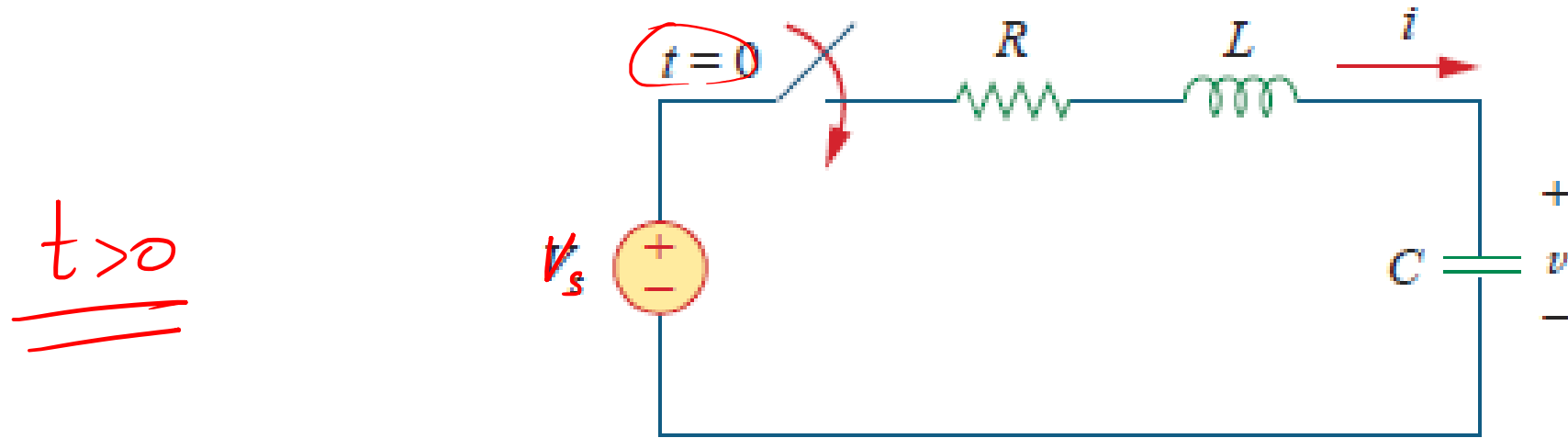


Step Response of a Series RLC Circuit



Applying KVL around the loop for $t > 0$,

$$L \frac{di}{dt} + Ri + v = V_s$$

$$i = C \frac{dv}{dt}$$

Substituting for i in Eq.

V_s

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{v}{LC} = \frac{V_s}{LC}$$

$$v(t) = \underline{v_t(t)} + \underline{v_{ss}(t)}$$

$$v_t(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{Overdamped})$$

$$v_t(t) = (A_1 + A_2 t) e^{-\alpha t} \quad (\text{Critically damped})$$

$$v_t(t) = (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t} \quad (\text{Underdamped})$$

The steady-state response is the final value of $v(t)$.

the final value of the capacitor voltage is the same as the source voltage V_s . Hence,

$$v_{ss}(t) = v(\infty) = \underline{V_s}$$

$\underline{V_t} + \underline{V_{ss}}$

Thus, the complete solutions for the overdamped, underdamped, and critically damped cases are:

$$v(t) = V_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{Overdamped}) \quad \checkmark$$

$$v(t) = V_s + (A_1 + A_2 t) e^{-\alpha t} \quad (\text{Critically damped}) \quad \checkmark$$

$$v(t) = V_s + (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t} \quad (\text{Underdamped}) \quad \checkmark$$

The values of the constants A_1 and A_2 are obtained from the initial conditions: $v(0)$ and $dv(0)/dt$. Keep in mind that v and i are, respectively, the voltage across the capacitor and the current through the inductor.

Ex - 8.5
Ex - 8.7

Ex - 8.3

Ex - 8.4

Work out all the carry

DA-2

Wednesday
