
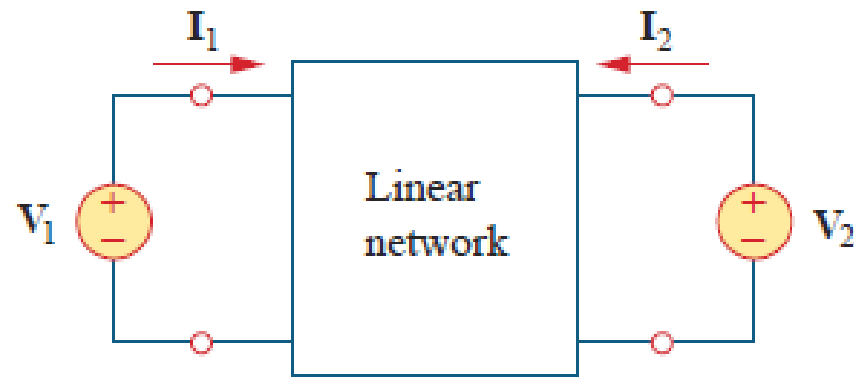

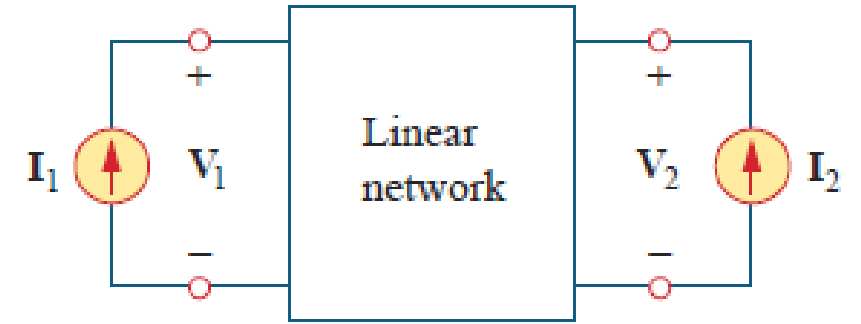
## Impedance Parameters

$$\begin{aligned}V_1 &= z_{11}I_1 + z_{12}I_2 \\V_2 &= z_{21}I_1 + z_{22}I_2\end{aligned}$$



(a)




(b)

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = [z] \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

A two-port network may be voltage-driven as in Fig. (a) or current-driven Fig (b)


$$\begin{aligned}z_{11} &= \left. \frac{V_1}{I_1} \right|_{I_2=0}, & z_{12} &= \left. \frac{V_1}{I_2} \right|_{I_1=0} \\ z_{21} &= \left. \frac{V_2}{I_1} \right|_{I_2=0}, & z_{22} &= \left. \frac{V_2}{I_2} \right|_{I_1=0}\end{aligned}$$

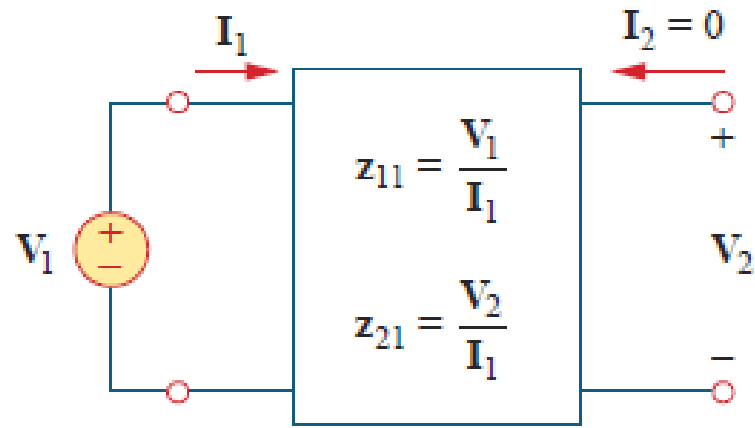

(a)

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}, \quad z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}, \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

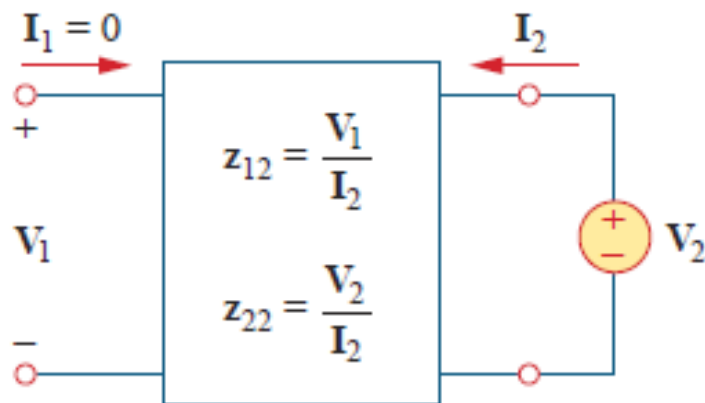

$z_{11}$  = Open-circuit input impedance


$z_{12}$  = Open-circuit transfer impedance from port 1 to port 2

$z_{21}$  = Open-circuit transfer impedance from port 2 to port 1


$z_{22}$  = Open-circuit output impedance

Determine the  $z$  parameters for the circuit in Fig.
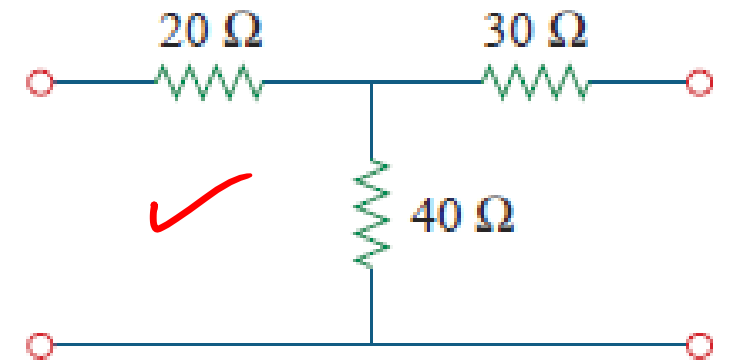
$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}$$



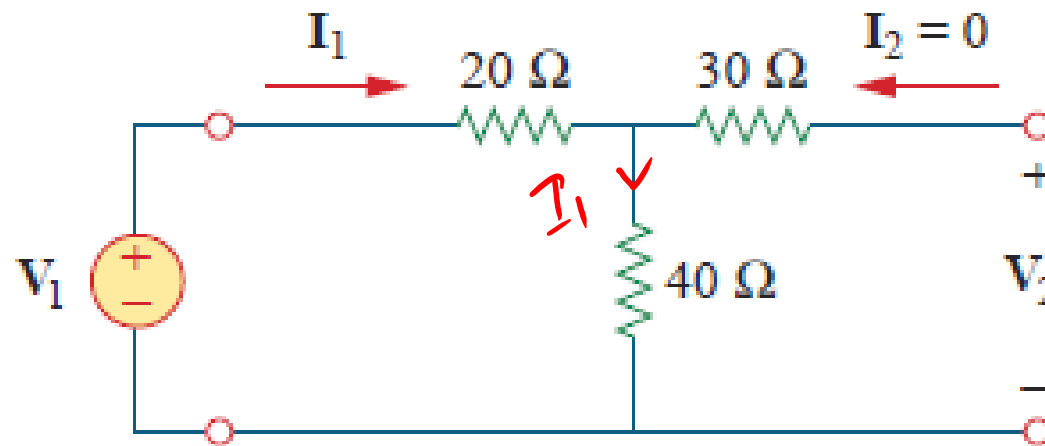■ **METHOD 1** To determine  $\underline{z_{11}}$  and  $\underline{z_{21}}$ , we apply a voltage source  $V_1$  to the input port and leave the output port open as in Fig.




*Open circuit voltmeter*

$$z_{11} = \frac{V_1}{I_1} = \frac{(20 + 40)I_1}{I_1} = \underline{60 \Omega}$$

$$z_{21} = \frac{V_2}{I_1} = \frac{40I_1}{I_1} = \underline{40 \Omega}$$

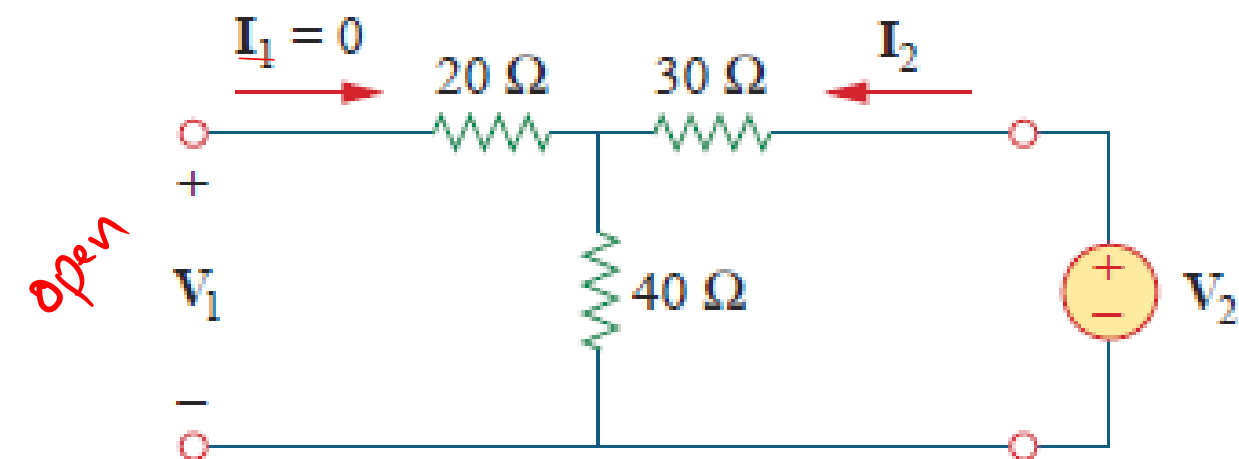To find  $z_{12}$  and  $z_{22}$ , we apply a voltage source  $V_2$  to the output port and leave the input port open as in Fig.




$$z_{12} = \frac{V_1}{I_2} = \frac{40I_2}{I_2} = 40\ \Omega,$$

$$z_{22} = \frac{V_2}{I_2} = \frac{(30 + 40)I_2}{I_2} = 70\ \Omega$$

$$[z] = \begin{bmatrix} 60\ \Omega & 40\ \Omega \\ 40\ \Omega & 70\ \Omega \end{bmatrix} \checkmark$$

$$\begin{aligned} \mathbf{V}_1 &= \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2 \\ \mathbf{V}_2 &= \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}\mathbf{I}_2 \end{aligned}$$

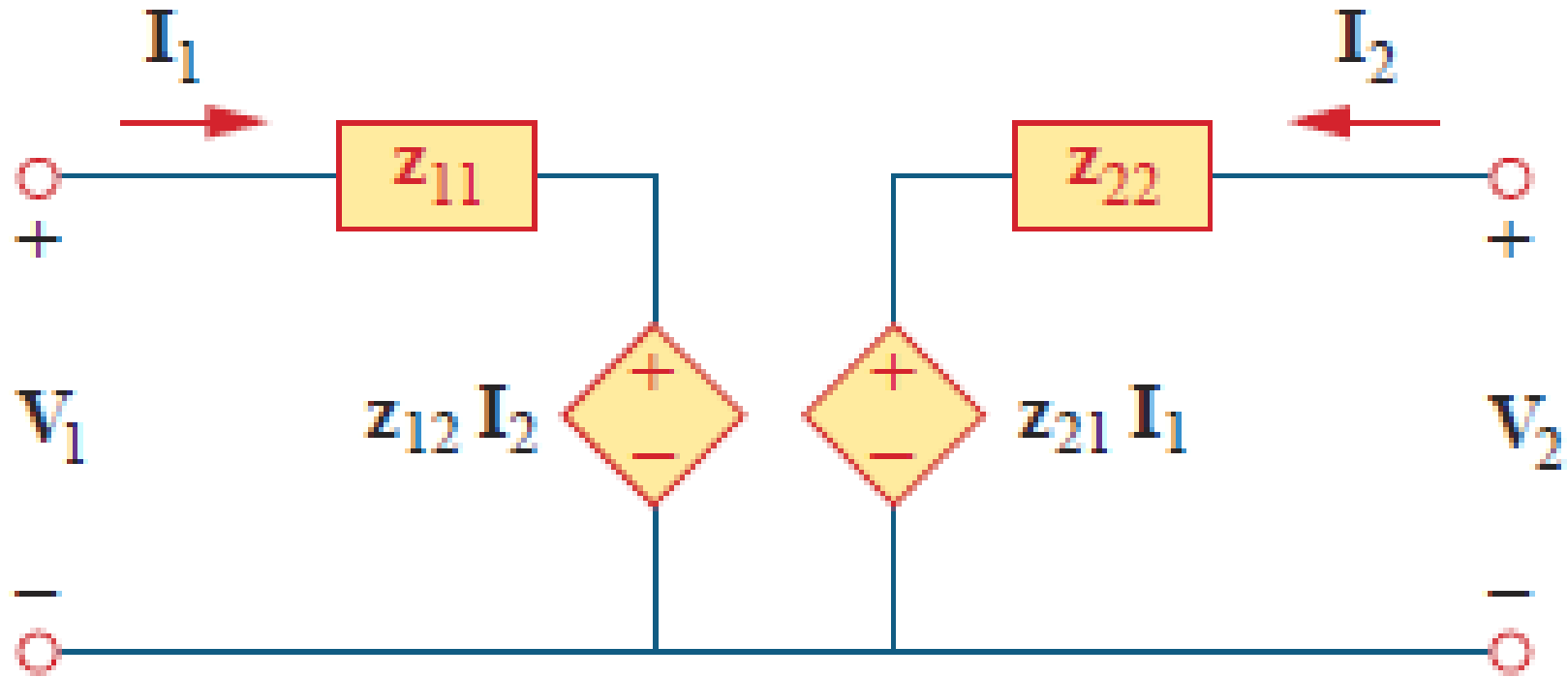
$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{z}_{11} & \mathbf{z}_{12} \\ \mathbf{z}_{21} & \mathbf{z}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix}$$



general equivalent network equivalent diagram


When  $z_{11} = z_{22}$ , the two-port network is said to be *symmetrical*. This implies that the network has mirrorlike symmetry about some center line; that is, a line can be found that divides the network into two similar halves.

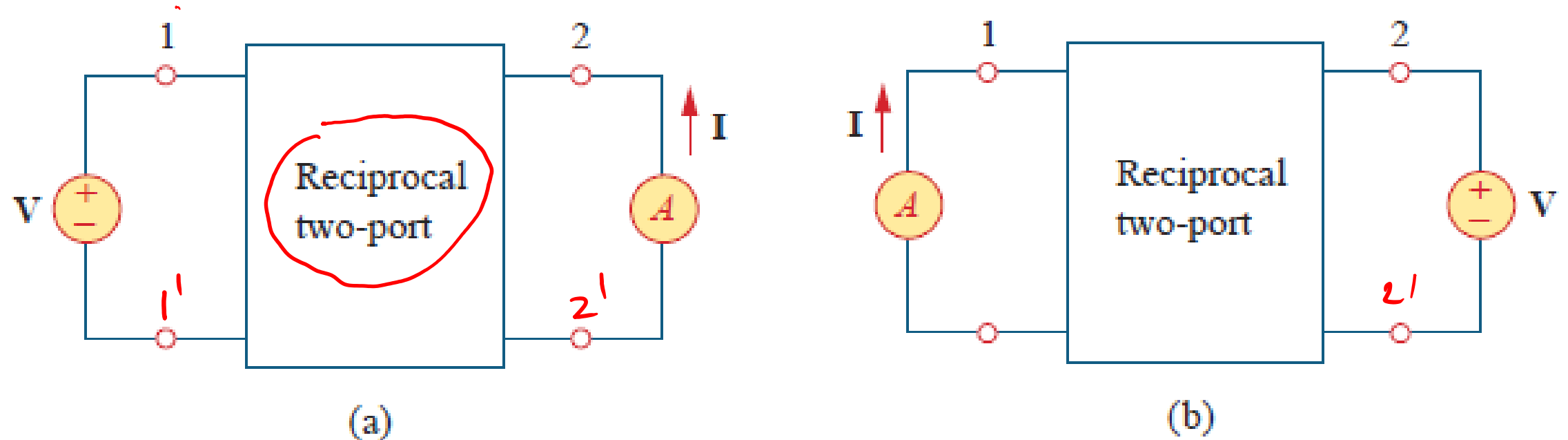When the two-port network is linear and has no dependent sources, the transfer impedances are equal ( $z_{12} = z_{21}$ ), and the two-port is said to be *reciprocal*. This means that if the points of excitation and response are interchanged, the transfer impedances remain the same.




**Interchanging a voltage source at one port with an ideal ammeter at the other port produces the same reading in a reciprocal two-port.**

if  $Z_{12} = Z_{21}$

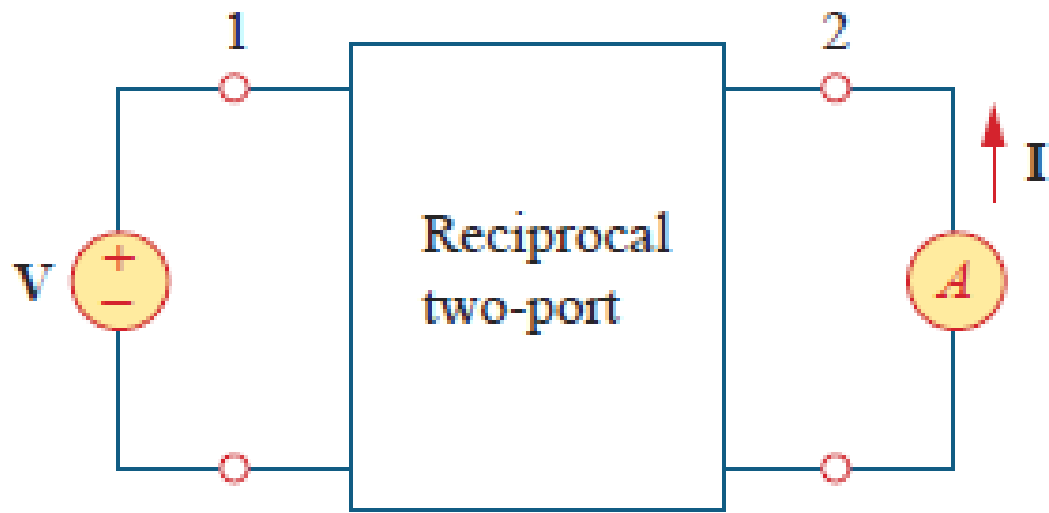

(a)

$$V = Z_{12}I$$

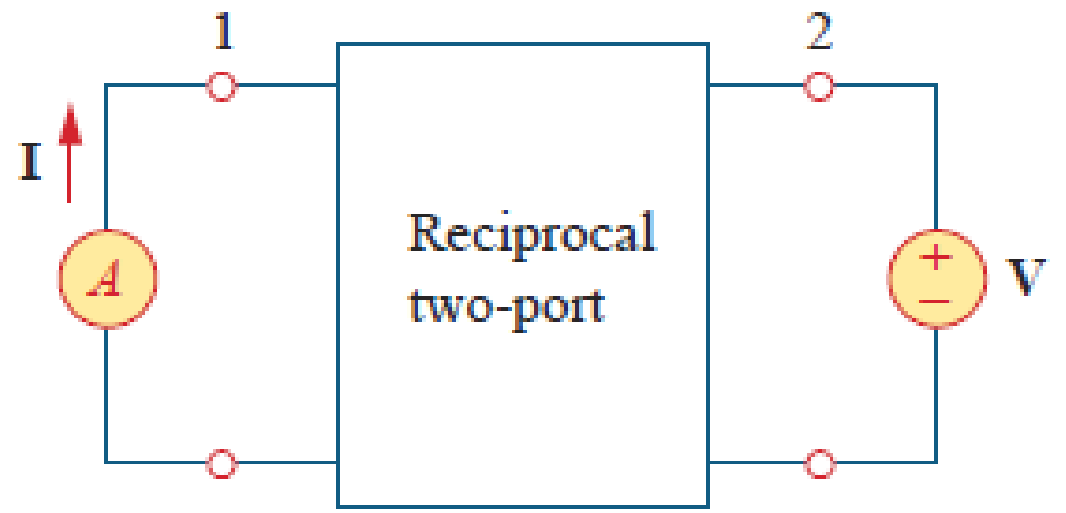

(b)

$$V = Z_{21}I$$

This means that if the points of excitation and response are interchanged, the transfer impedances remain the same




$$\left. \begin{aligned} \checkmark V_1 &= z_{11}I_1 + z_{12}I_2 \\ \checkmark V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned} \right\}$$

→ ①

From the diagram

$$\begin{aligned} V_1 &= (z_{11} - z_{12})I_1 + z_{12}(I_1 + I_2) \\ &= z_{11}I_1 - z_{12}I_1 + z_{12}I_1 + z_{12}I_2 \end{aligned}$$
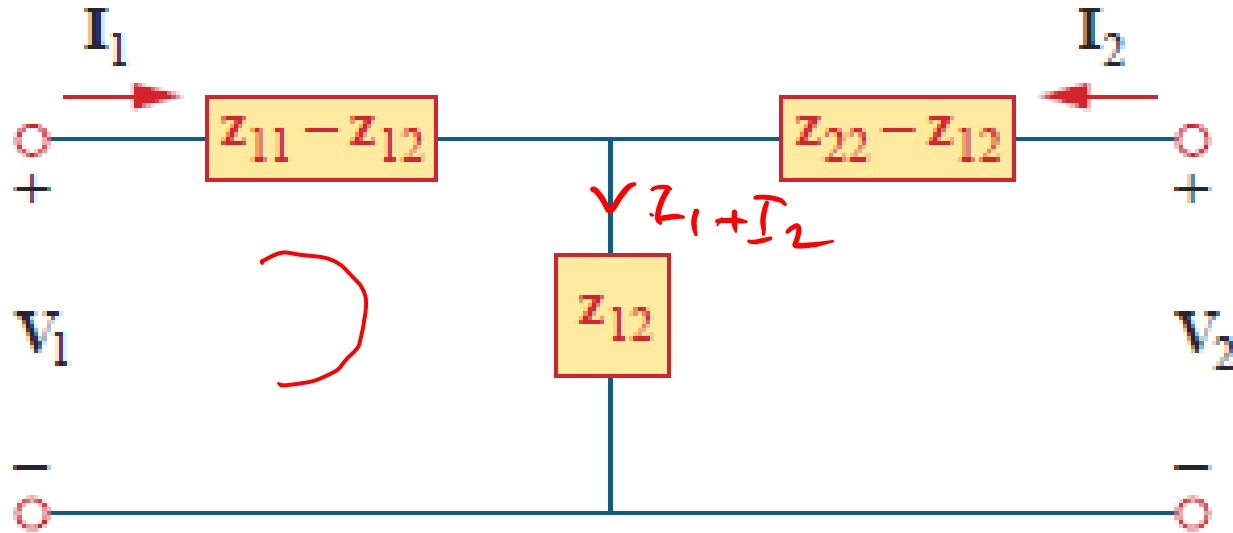
$$\boxed{V_1 = z_{11}I_1 + z_{12}I_2} \quad \text{Eqn 1 holds good}$$



$$\begin{aligned} V_2 &= (z_{22} - z_{12})I_2 + z_{12}(I_1 + I_2) \\ &= z_{22}I_2 - z_{12}I_2 + z_{12}I_1 + z_{12}I_2 \end{aligned}$$

$$V_2 = \underline{z_{12}}I_1 + z_{22}I_2$$

For reciprocal circuits


$$z_{12} = z_{21}$$

A reciprocal network can be replaced by the T-equivalent circuit

$$\text{Eqn 1 holds good} \rightarrow \therefore \boxed{V_2 = z_{21}I_1 + z_{22}I_2}$$



$$\mathbf{V}_1 = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2$$
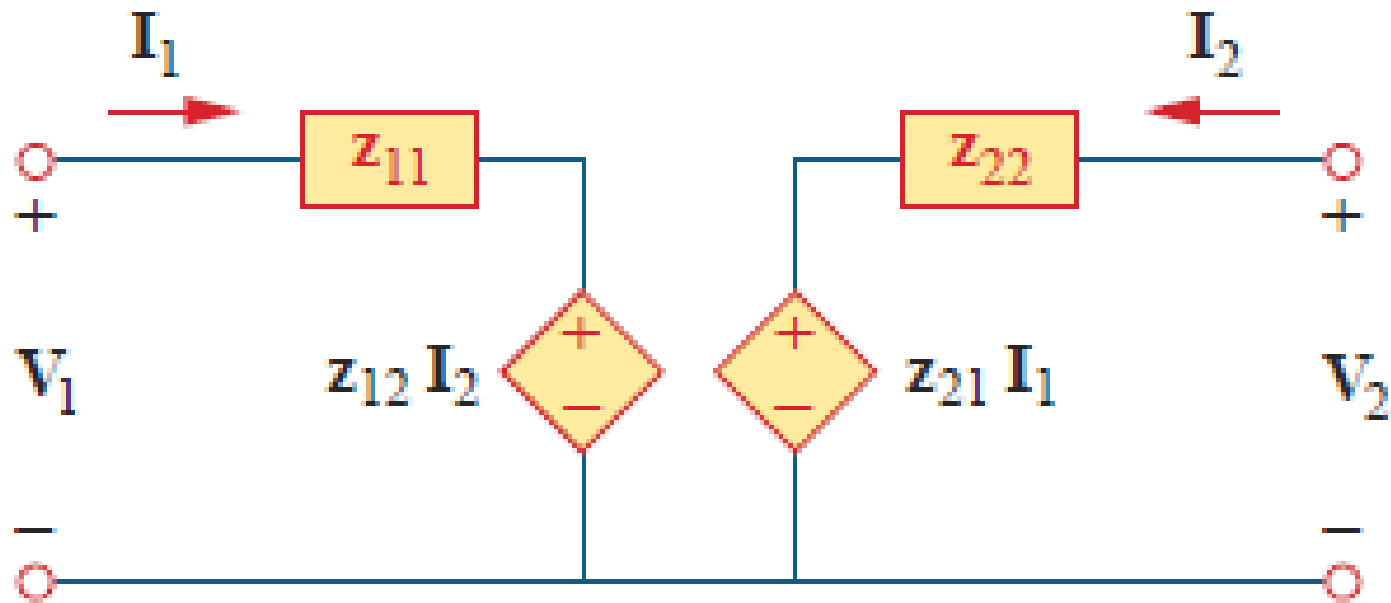
$$\mathbf{V}_2 = \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}\mathbf{I}_2$$



If the network is not reciprocal, the above general equivalent network is sufficient

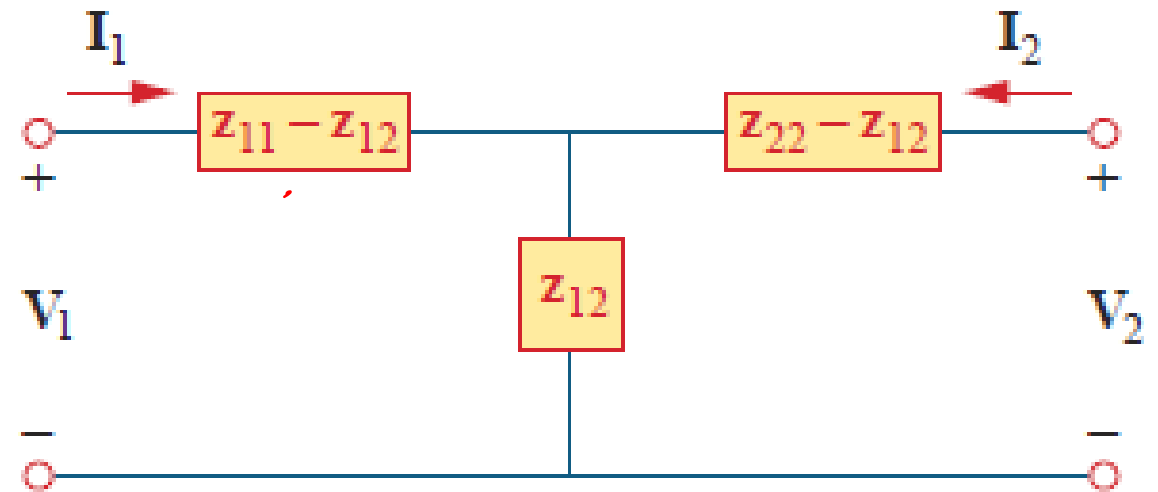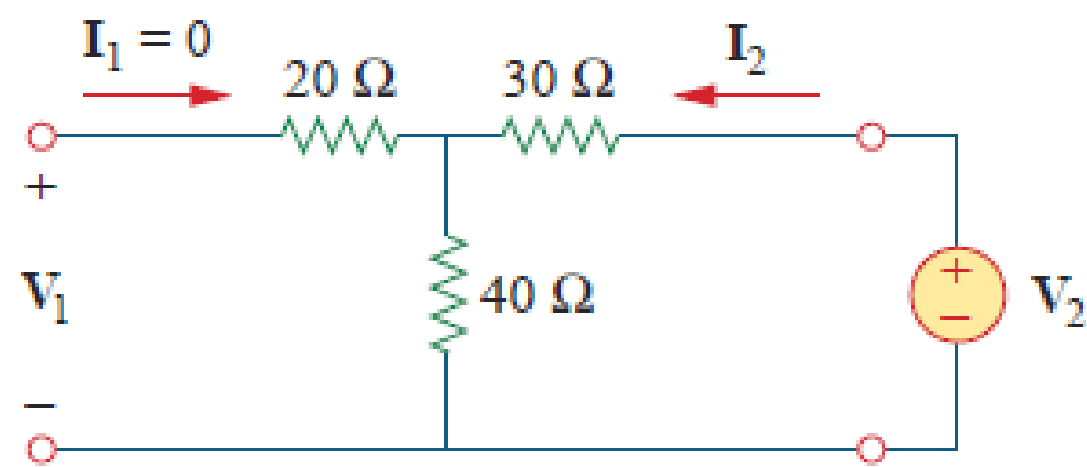■ **METHOD 2** Alternatively, since there is no dependent source in the given circuit,  $z_{12} = z_{21}$



$$z_{12} = 40 \, \Omega = z_{21}$$


$$z_{11} - z_{12} = 20 \quad \Rightarrow \quad z_{11} = 20 + z_{12} = 60 \, \Omega$$



$$z_{22} - z_{12} = 30 \quad \Rightarrow \quad z_{22} = 30 + z_{12} = 70 \, \Omega$$

Find the  $z$  parameters of the two-port network in Fig. 19.9.

**Answer:**  $z_{11} = 28 \Omega$ ,  $z_{12} = z_{21} = z_{22} = 12 \Omega$ . ✓

### Practice Problem 19.1

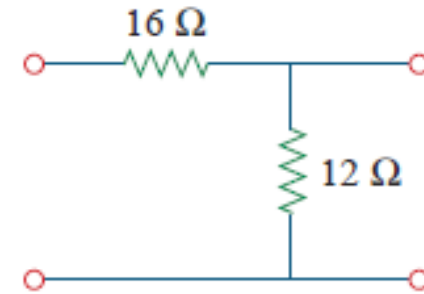

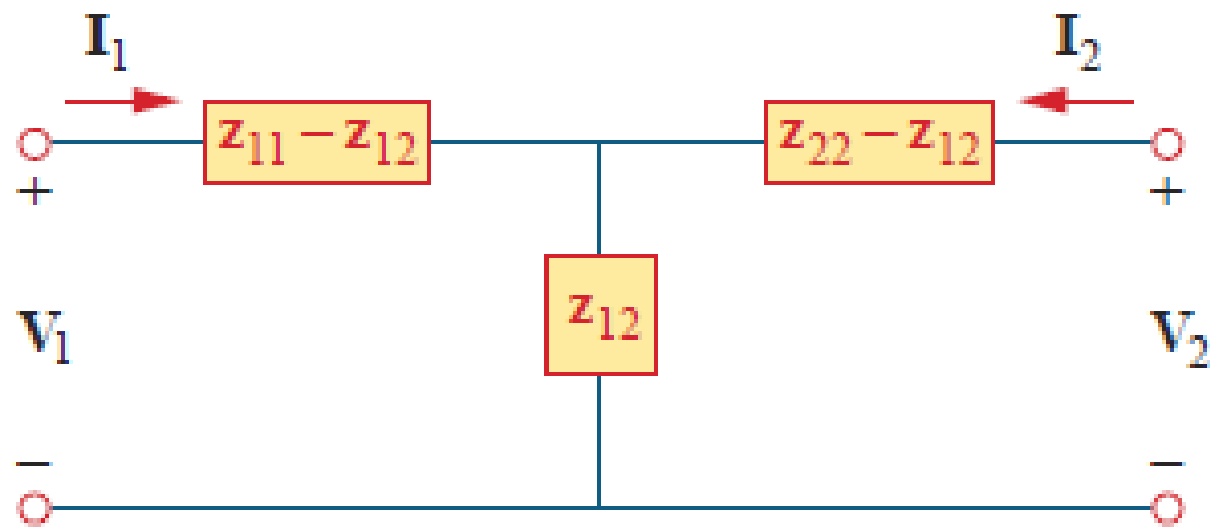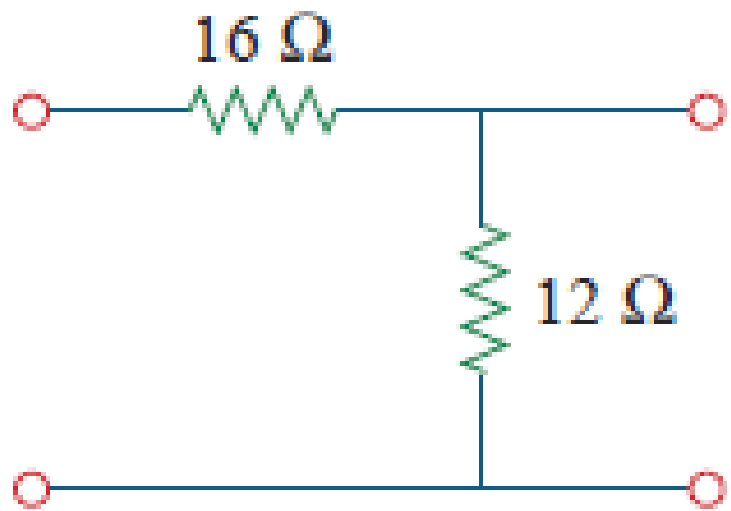


$$z_{11} - z_{12} = 16\ \Omega$$

$$z_{22} - z_{12} = 0$$


$$z_{12} = 12\ \Omega$$
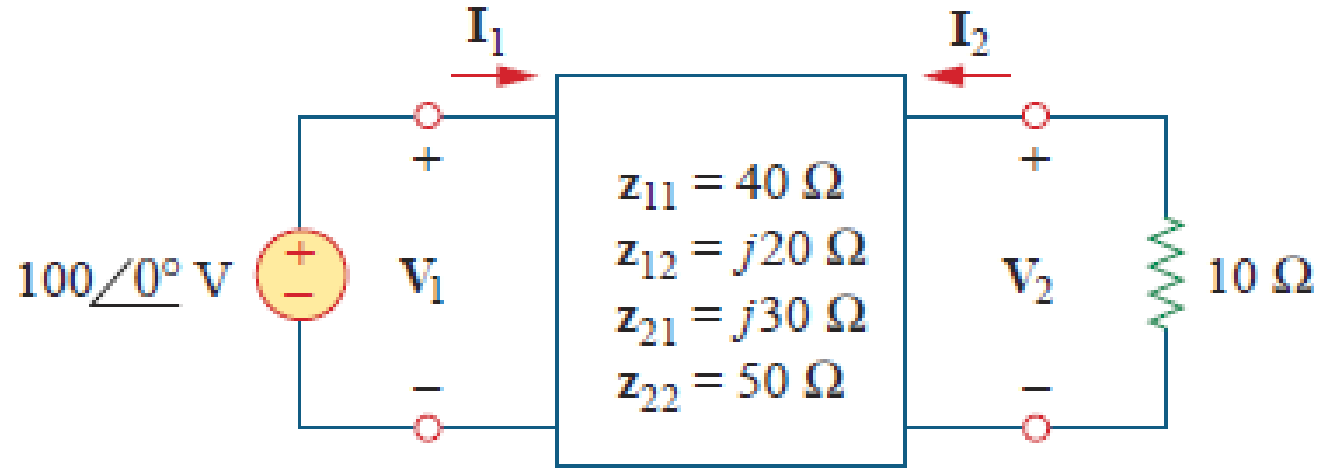
## Example 19.2

Find  $I_1$  and  $I_2$  in the circuit in Fig.



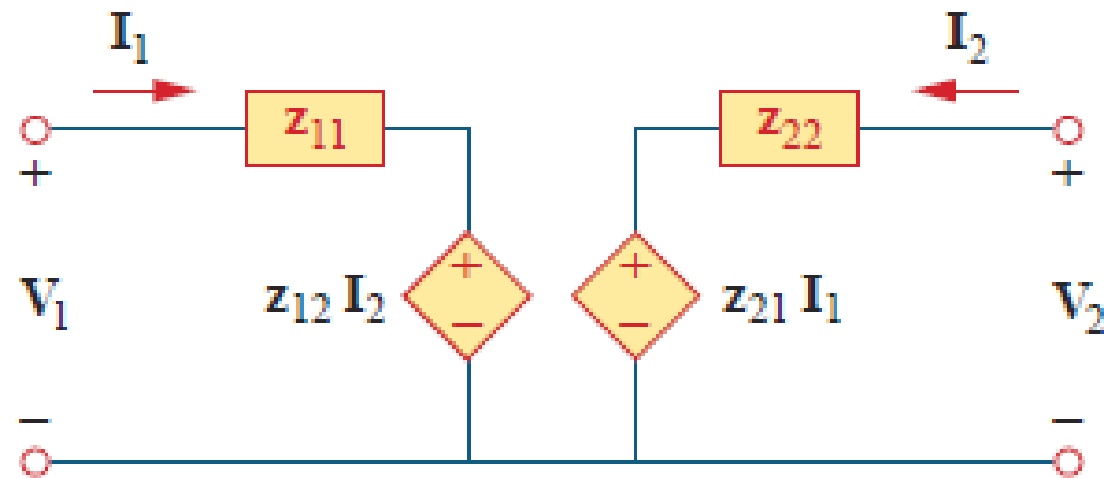This is not a reciprocal network. We may use the equivalent circuit in Fig below.



Pharos

$$\mathbf{V}_1 = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2$$

$$\mathbf{V}_2 = \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}\mathbf{I}_2$$


$$\mathbf{V}_1 = 40\mathbf{I}_1 + j20\mathbf{I}_2$$

$$\mathbf{V}_2 = j30\mathbf{I}_1 + 50\mathbf{I}_2$$

$$\mathbf{V}_1 = 100\angle 0^\circ, \quad \mathbf{V}_2 = -10\mathbf{I}_2$$

$$100 = 40\mathbf{I}_1 + j20\mathbf{I}_2$$
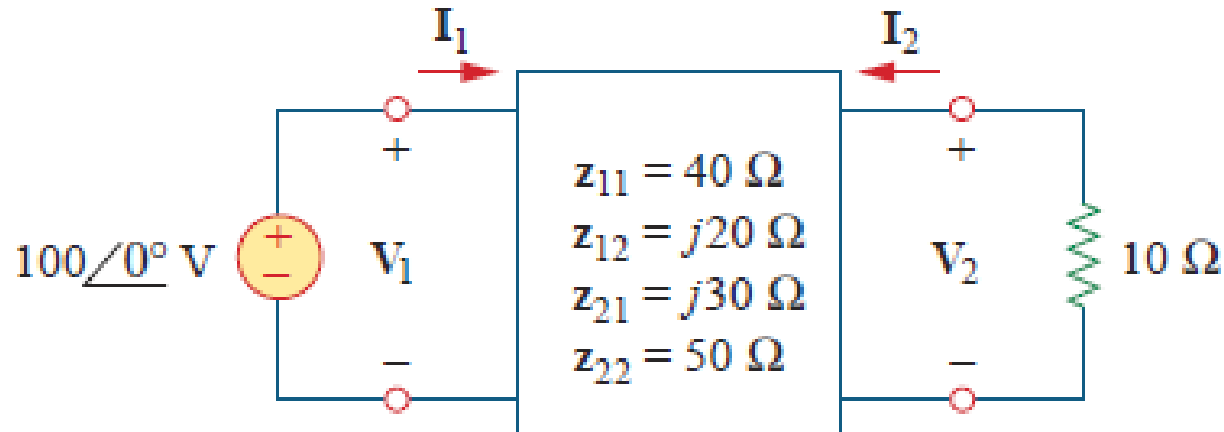
$$-10\mathbf{I}_2 = j30\mathbf{I}_1 + 50\mathbf{I}_2 \quad \Rightarrow \quad \underline{\underline{\mathbf{I}_1 = j2\mathbf{I}_2}}$$



$$100 = 40\mathbf{I}_1 + j20\mathbf{I}_2 \quad (19.2.3)$$

$$-10\mathbf{I}_2 = j30\mathbf{I}_1 + 50\mathbf{I}_2 \quad \Rightarrow \quad \mathbf{I}_1 = j2\mathbf{I}_2 \quad (19.2.4)$$

Substituting Eq. (19.2.4) into Eq. (19.2.3) gives

$$100 = j80\mathbf{I}_2 + j20\mathbf{I}_2 \quad \Rightarrow \quad \mathbf{I}_2 = \frac{100}{j100} = -j$$

From Eq. (19.2.4),  $\mathbf{I}_1 = j2(-j) = 2$ . Thus,

$$\mathbf{I}_1 = 2\angle\underline{0^\circ} \text{ A}, \quad \mathbf{I}_2 = 1\angle\underline{-90^\circ} \text{ A}$$





## Admittance Parameters

$$\mathbf{I}_1 = y_{11}\mathbf{V}_1 + y_{12}\mathbf{V}_2$$

$$\mathbf{I}_2 = y_{21}\mathbf{V}_1 + y_{22}\mathbf{V}_2$$

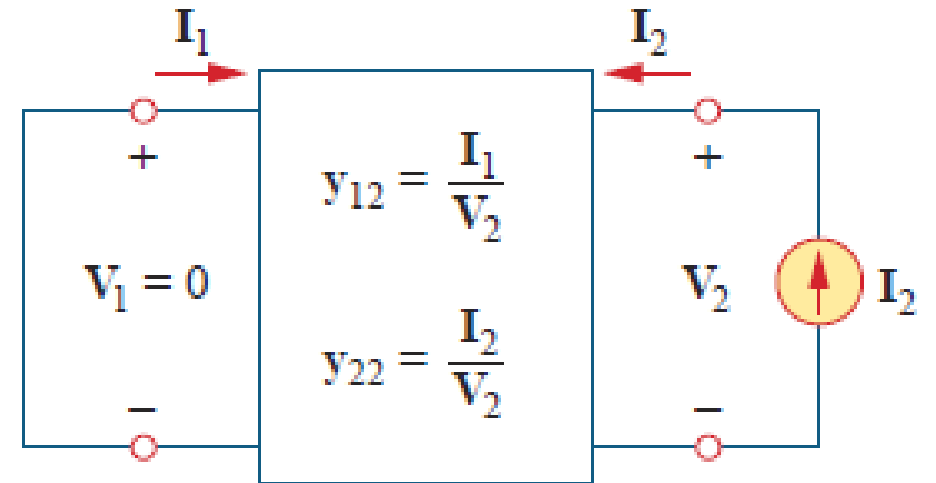
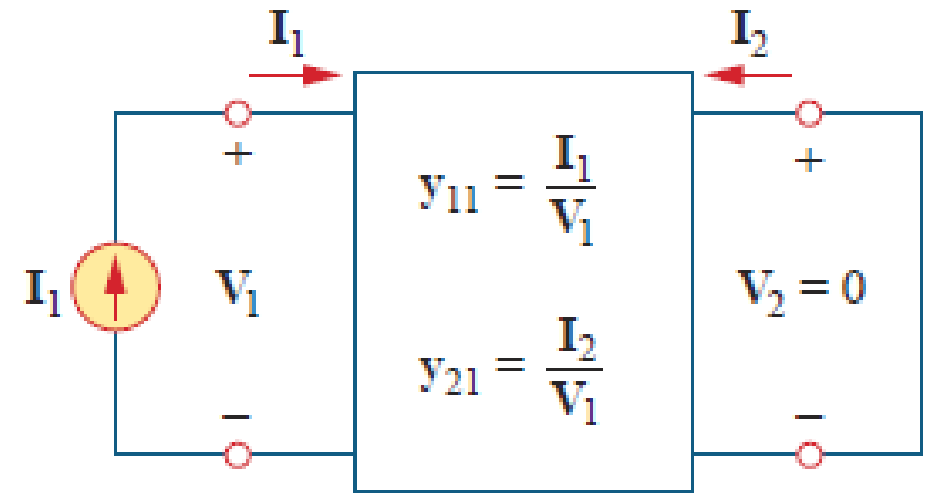
$$\begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = [\mathbf{y}] \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix}$$



$$y_{11} = \left. \frac{\mathbf{I}_1}{\mathbf{V}_1} \right|_{\mathbf{V}_2=0}, \quad y_{12} = \left. \frac{\mathbf{I}_1}{\mathbf{V}_2} \right|_{\mathbf{V}_1=0}$$

$$y_{21} = \left. \frac{\mathbf{I}_2}{\mathbf{V}_1} \right|_{\mathbf{V}_2=0}, \quad y_{22} = \left. \frac{\mathbf{I}_2}{\mathbf{V}_2} \right|_{\mathbf{V}_1=0}$$

$$\begin{aligned}
 y_{11} &= \left. \frac{I_1}{V_1} \right|_{V_2=0}, & y_{12} &= \left. \frac{I_1}{V_2} \right|_{V_1=0} \\
 y_{21} &= \left. \frac{I_2}{V_1} \right|_{V_2=0}, & y_{22} &= \left. \frac{I_2}{V_2} \right|_{V_1=0}
 \end{aligned}$$

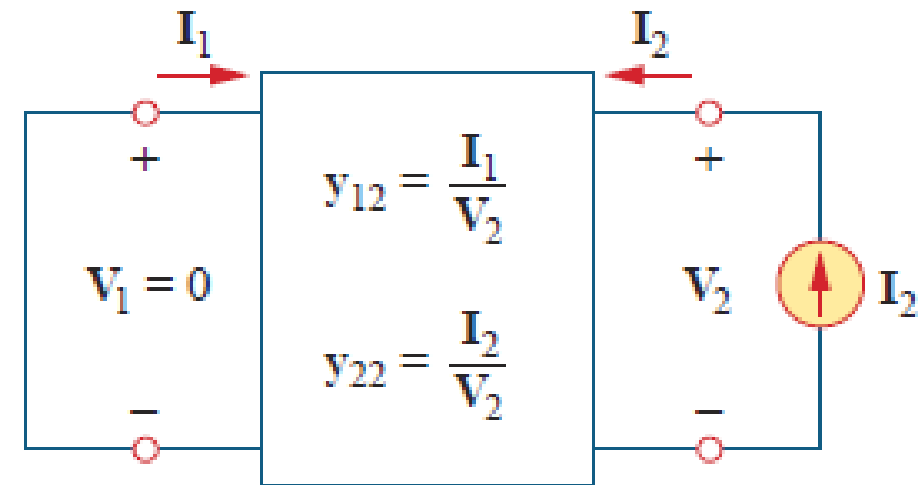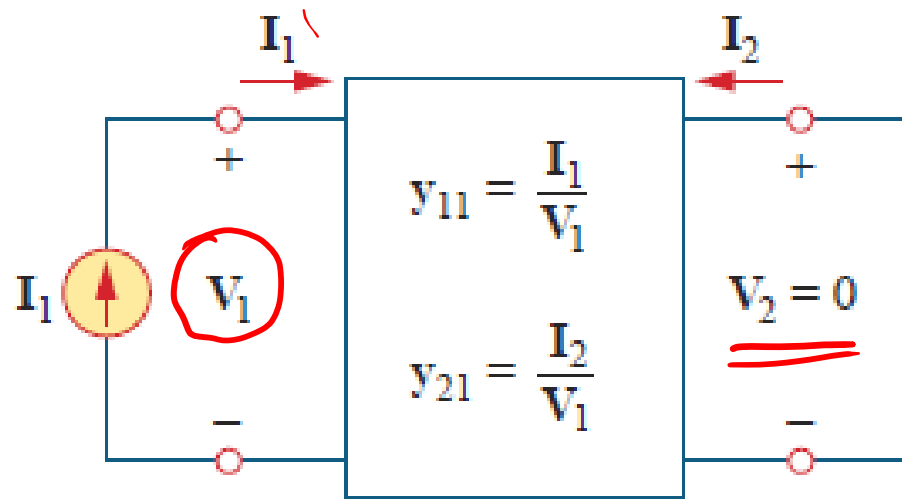

$y_{11}$  = Short-circuit input admittance

$y_{12}$  = Short-circuit transfer admittance from port 2 to port 1

$y_{21}$  = Short-circuit transfer admittance from port 1 to port 2


$y_{22}$  = Short-circuit output admittance

$$I_1 = y_{11}V_1 + y_{12}V_2$$


$$I_2 = y_{21}V_1 + y_{22}V_2$$

Reciprocal network is a linear two-port network that has no dependent sources, the transfer admittances are equal:

$$(y_{12} = y_{21})$$

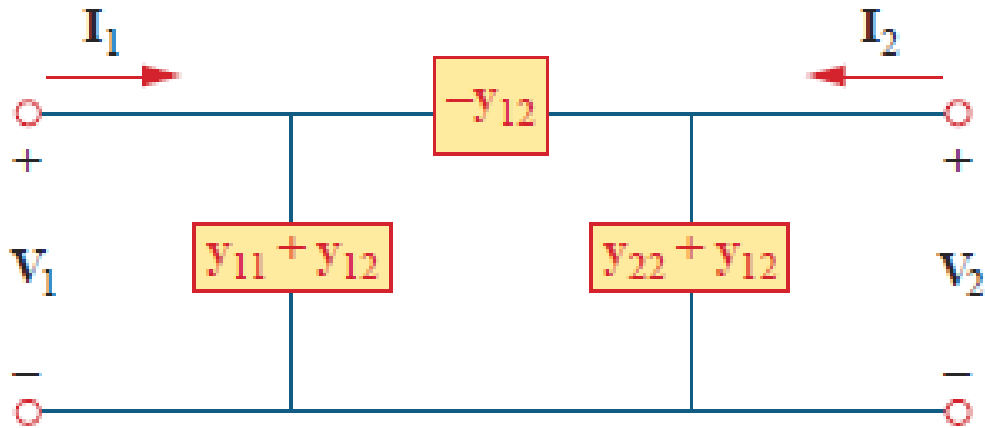

(a)

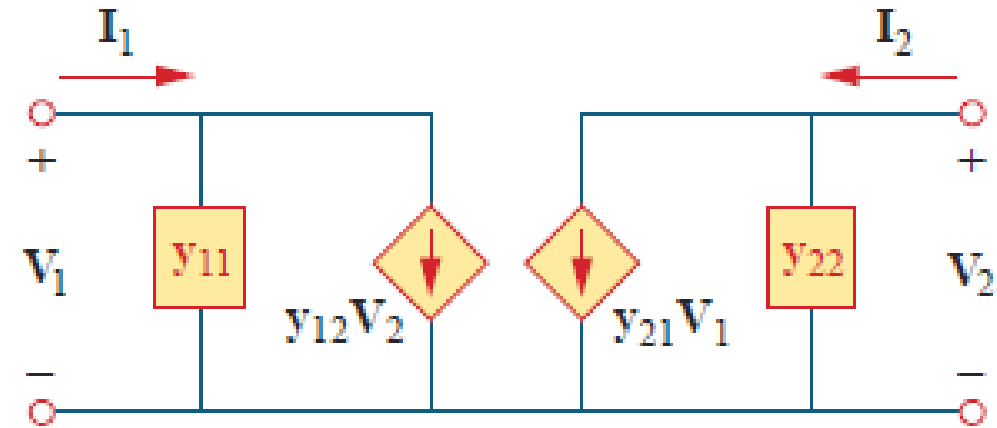



(b)

(a)  $\Pi$ -equivalent circuit (for reciprocal case only), (b) general equivalent circuit.

Obtain the  $y$  parameters for the  $\Pi$  network shown in Fig.

### METHOD 1

To find  $y_{11}$  and  $y_{21}$ ,

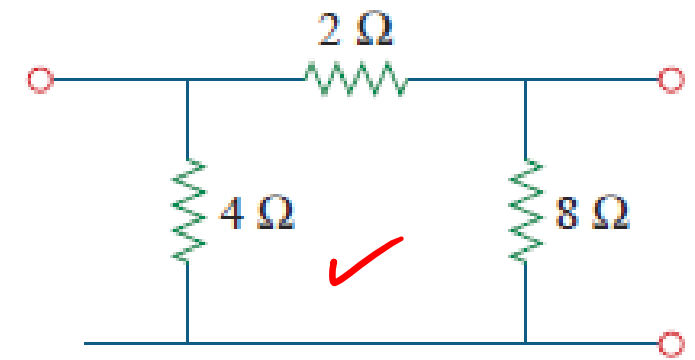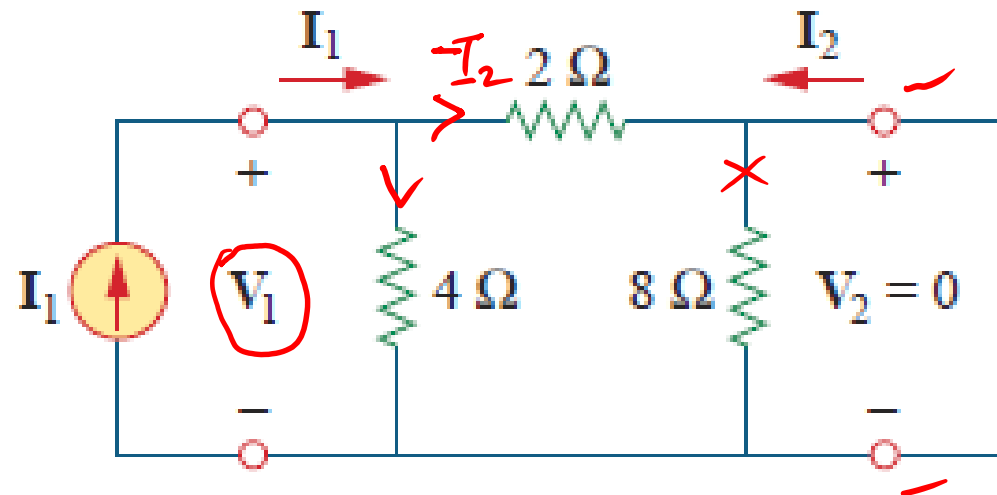

$$I_2 = \frac{4}{4+2} \times I_1$$


the  $8\text{-}\Omega$  resistor is short-circuited, the  $2\text{-}\Omega$  resistor is in parallel with the  $4\text{-}\Omega$  resistor. Hence,

$$V_1 = I_1(4 \parallel 2) = \frac{4}{3}I_1, \quad y_{11} = \frac{I_1}{V_1} = \frac{I_1}{\frac{4}{3}I_1} = 0.75\text{ S}$$

By current division,

$$-I_2 = \frac{4}{4+2}I_1 = \frac{2}{3}I_1, \quad y_{21} = \frac{I_2}{V_1} = \frac{-\frac{2}{3}I_1}{\frac{4}{3}I_1} = -0.5\text{ S}$$

To get  $y_{12}$  and  $y_{22}$

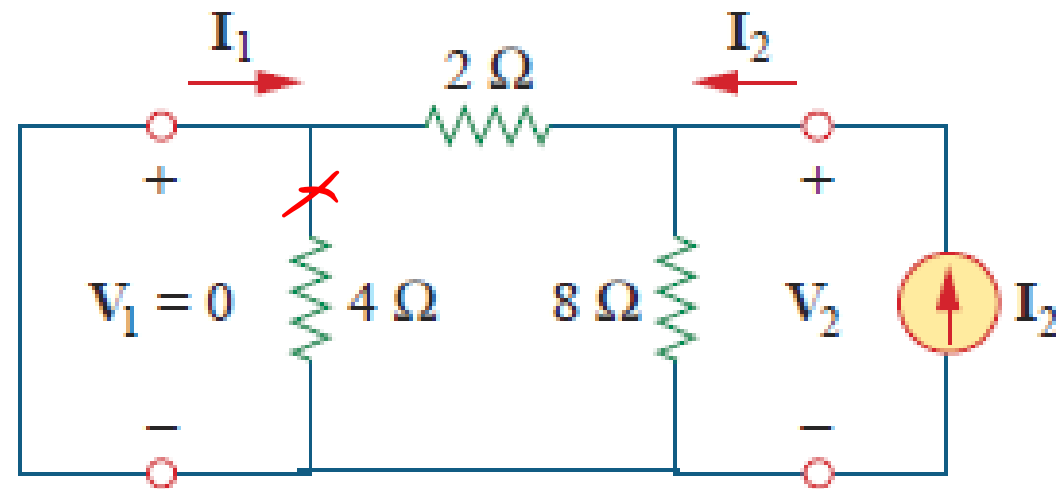

The  $4\text{-}\Omega$  resistor is short-circuited so that the  $2\text{-}\Omega$  and  $8\text{-}\Omega$  resistors are in parallel.



$$V_2 = I_2(8 \parallel 2) = \frac{8}{5}I_2, \quad y_{22} = \frac{I_2}{V_2} = \frac{I_2}{\frac{8}{5}I_2} = \frac{5}{8} = 0.625\text{ S}$$

By current division,

$$-I_1 = \frac{8}{8 + 2}I_2 = \frac{4}{5}I_2, \quad y_{12} = \frac{I_1}{V_2} = \frac{-\frac{4}{5}I_2}{\frac{8}{5}I_2} = -0.5\text{ S}$$

■ **METHOD 2** Alternatively, comparing Fig.

*There are no dependent sources*

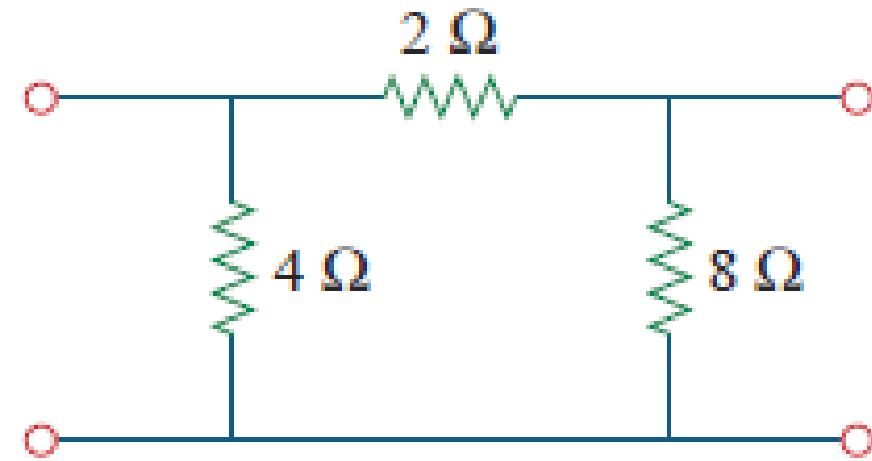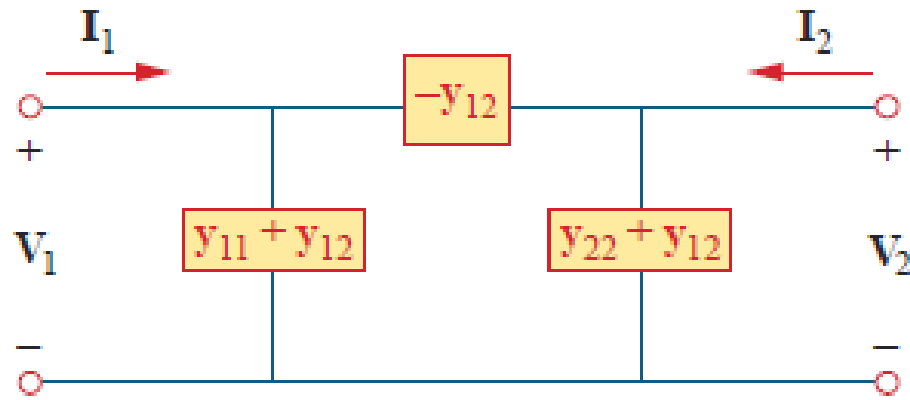

$\Pi$ -equivalent circuit (for reciprocal case only).

$$y_{12} = -\frac{1}{2}\text{ S} = y_{21}$$

$$y_{11} + y_{12} = \frac{1}{4} \quad \Rightarrow \quad y_{11} = \frac{1}{4} - y_{12} = 0.75\text{ S}$$


$$y_{22} + y_{12} = \frac{1}{8} \quad \Rightarrow \quad y_{22} = \frac{1}{8} - y_{12} = 0.625\text{ S}$$

as obtained previously.

Obtain the  $y$  parameters for the  $T$  network shown in Fig. 19.16.

**Answer:**  $y_{11} = 75.77 \text{ mS}$ ,  $y_{12} = y_{21} = -30.3 \text{ mS}$ ,  $y_{22} = 45.47 \text{ mS}$ .


### Practice Problem 19.3

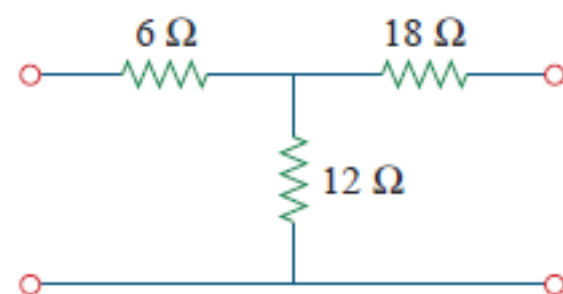

Determine the  $y$  parameters for the two-port shown in Fig.

finding  $y_{11}$  and  $y_{21}$ :


$$I_1 = \frac{V_1 - V_o}{8}$$

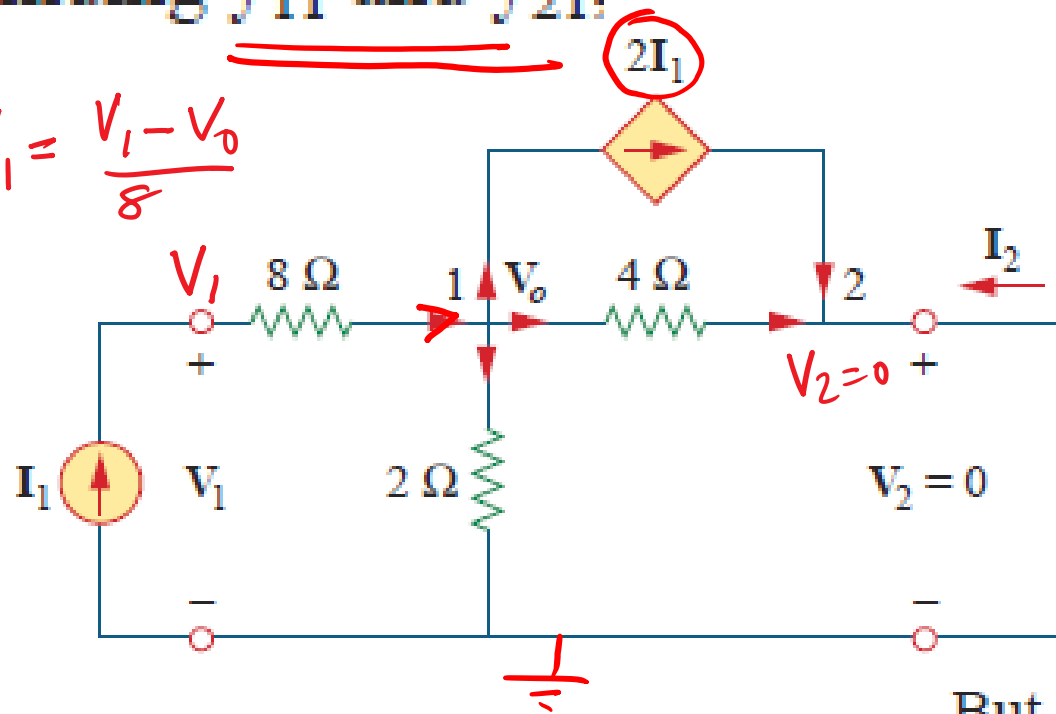

But  $I_1 = \frac{V_1 - V_o}{8}$ ; therefore,

$$0 = \frac{V_1 - V_o}{8} + \frac{3V_o}{4}$$

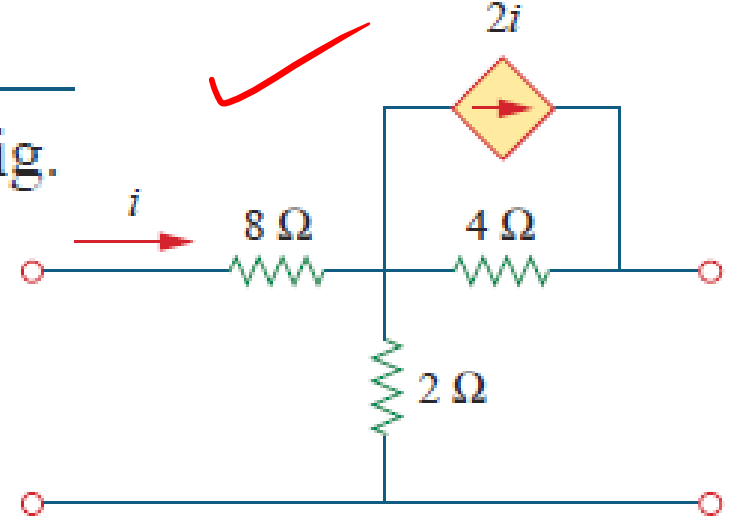
$$0 = V_1 - V_o + 6V_o \Rightarrow V_1 = -5V_o$$



KCL
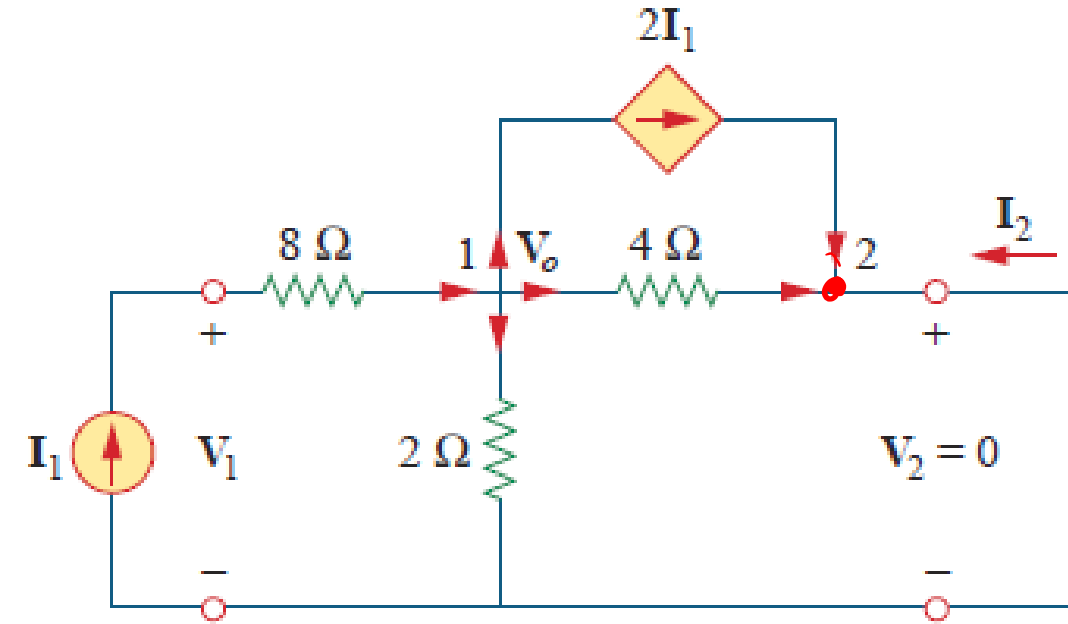
$$\frac{V_1 - V_o}{8} = 2I_1 + \frac{V_o}{2} + \frac{V_o - 0}{4}$$





Hence,

$$I_1 = \frac{-5V_o - V_o}{8} = -0.75V_o$$

and

$$y_{11} = \frac{I_1}{V_1} = \frac{-0.75V_o}{-5V_o} = 0.15 \text{ S}$$

At node 2,

$$\frac{V_o - 0}{4} + 2I_1 + I_2 = 0$$


or

$$-I_2 = 0.25V_o - 1.5V_o = -1.25V_o$$

Hence,

$$y_{21} = \frac{I_2}{V_1} = \frac{1.25V_o}{-5V_o} = -0.25 \text{ S}$$

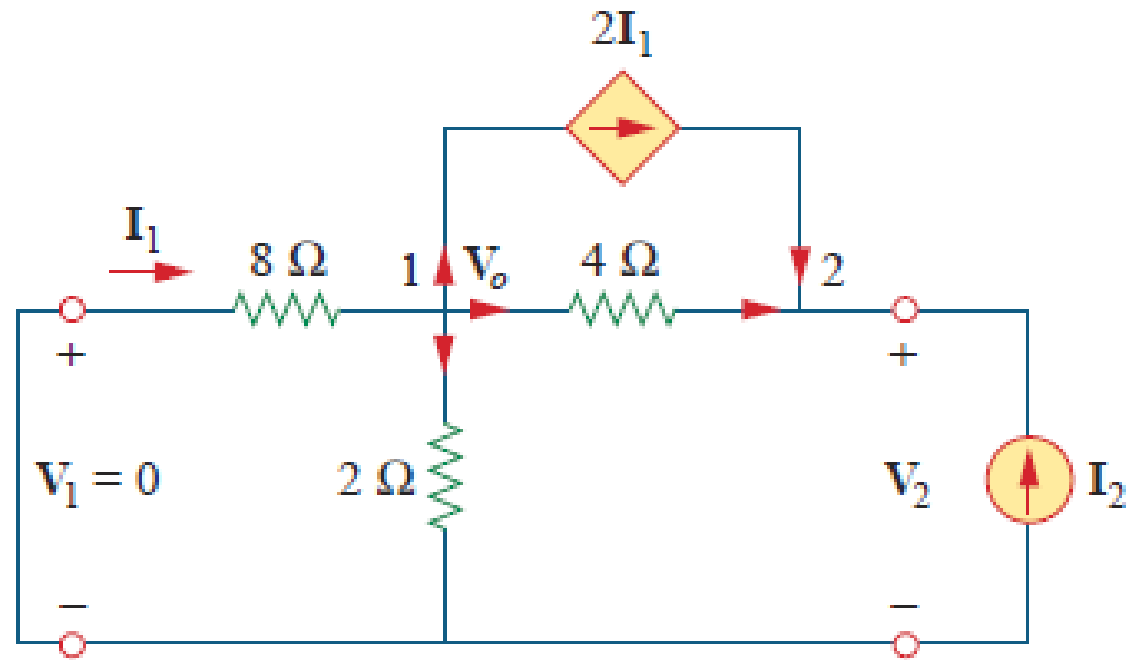Similarly, we get  $y_{12}$  and  $y_{22}$  using Fig.



At node 1,

$$\frac{0 - V_o}{8} = 2I_1 + \frac{V_o}{2} + \frac{V_o - V_2}{4}$$

But  $I_1 = \frac{0 - V_o}{8}$ ; therefore,

$$0 = -\frac{V_o}{8} + \frac{V_o}{2} + \frac{V_o - V_2}{4}$$

or

$$0 = -V_o + 4V_o + 2V_o - 2V_2 \Rightarrow V_2 = 2.5V_o$$

Hence,

$$y_{12} = \frac{I_1}{V_2} = \frac{-V_o/8}{2.5V_o} = -0.05 \text{ S}$$

At node 2,

$$\frac{V_o - V_2}{4} + 2I_1 + I_2 = 0$$


or

$$-I_2 = 0.25V_o - \frac{1}{4}(2.5V_o) - \frac{2V_o}{8} = -0.625V_o$$

Thus,


$$y_{22} = \frac{I_2}{V_2} = \frac{0.625V_o}{2.5V_o} = 0.25 \text{ S}$$

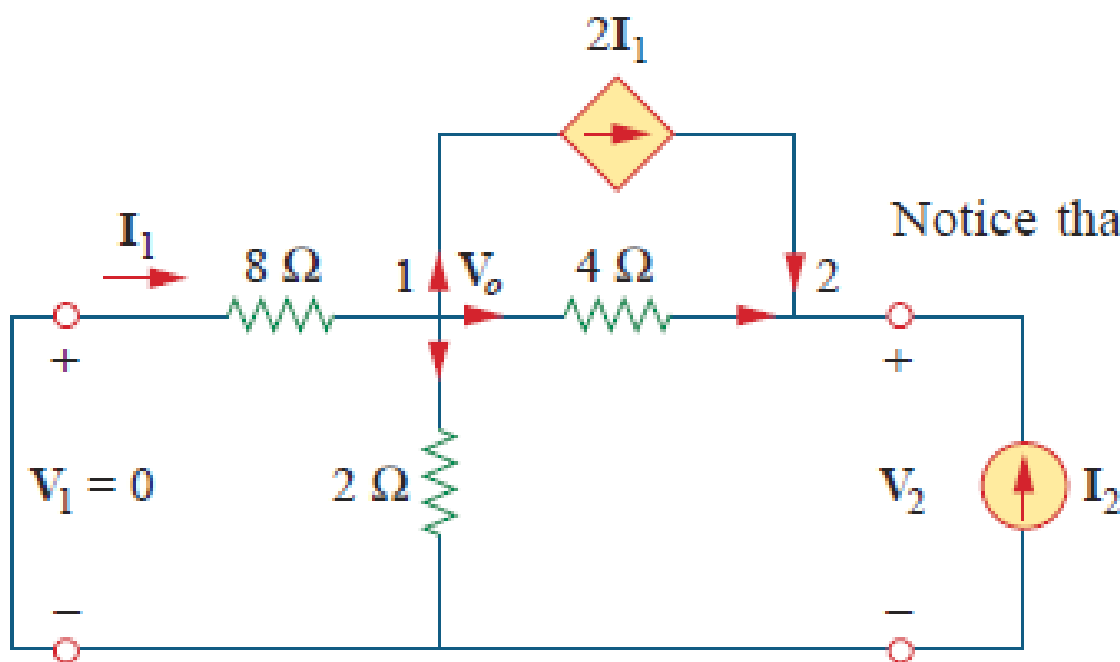Notice that  $y_{12} \neq y_{21}$  in this case, since the network is not reciprocal.


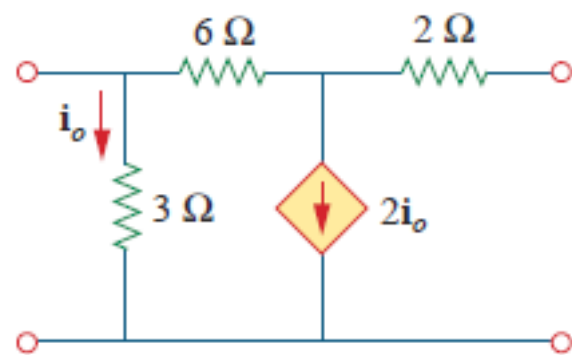
### Practice Problem 19.4

Obtain the  $y$  parameters for the circuit in Fig. 19.19.



**Answer:**  $y_{11} = 0.625 \text{ S}$ ,  $y_{12} = -0.125 \text{ S}$ ,  $y_{21} = 0.375 \text{ S}$ ,  $y_{22} = 0.125 \text{ S}$ .

# Hybrid Parameters

$$\begin{aligned}V_1 &= h_{11}I_1 + h_{12}V_2 \\I_2 &= h_{21}I_1 + h_{22}V_2\end{aligned}$$

$$\begin{aligned}h_{11} &= \left. \frac{V_1}{I_1} \right|_{V_2=0}, & h_{12} &= \left. \frac{V_1}{V_2} \right|_{I_1=0} \\h_{21} &= \left. \frac{I_2}{I_1} \right|_{V_2=0}, & h_{22} &= \left. \frac{I_2}{V_2} \right|_{I_1=0}\end{aligned}$$

For reciprocal networks

$$h_{12} = -h_{21}$$


$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = [\mathbf{h}] \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$h_{11}$  = Short-circuit input impedance

$h_{12}$  = Open-circuit reverse voltage gain

$h_{21}$  = Short-circuit forward current gain

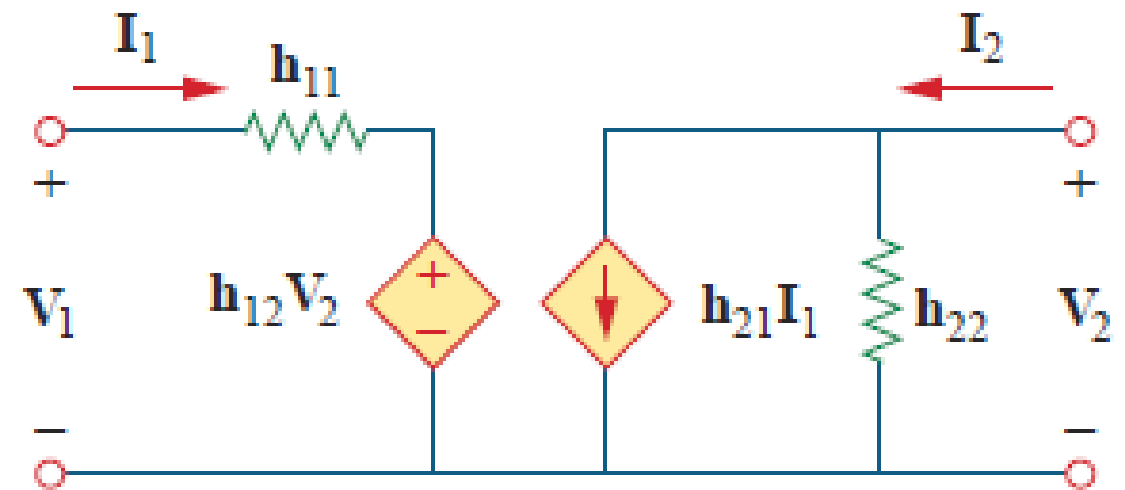$h_{22}$  = Open-circuit output admittance



A set of parameters closely related to the  $h$  parameters are the  **$g$  parameters** or **inverse hybrid parameters**. These are used to describe the terminal currents and voltages as

$$\begin{aligned} \mathbf{I}_1 &= \mathbf{g}_{11}\mathbf{V}_1 + \mathbf{g}_{12}\mathbf{I}_2 \\ \mathbf{V}_2 &= \mathbf{g}_{21}\mathbf{V}_1 + \mathbf{g}_{22}\mathbf{I}_2 \end{aligned}$$


$$\begin{bmatrix} \mathbf{I}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{g}_{11} & \mathbf{g}_{12} \\ \mathbf{g}_{21} & \mathbf{g}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_2 \end{bmatrix} = [\mathbf{g}] \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_2 \end{bmatrix}$$

$\mathbf{g}_{11}$  = Open-circuit input admittance

$\mathbf{g}_{12}$  = Short-circuit reverse current gain

$\mathbf{g}_{21}$  = Open-circuit forward voltage gain


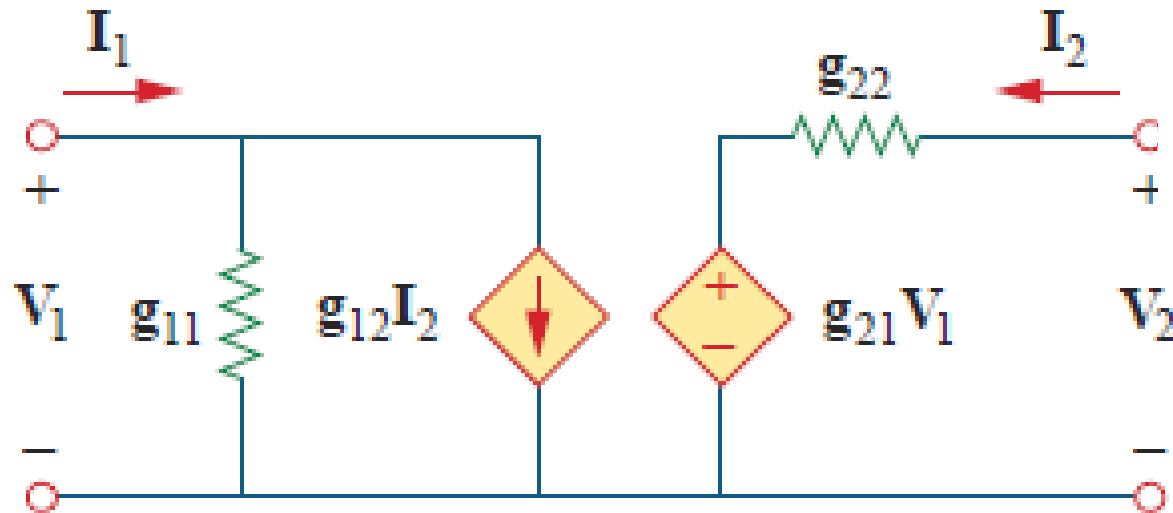
$\mathbf{g}_{22}$  = Short-circuit output impedance



$$\mathbf{g}_{11} = \left. \frac{\mathbf{I}_1}{\mathbf{V}_1} \right|_{\mathbf{I}_2=0}, \quad \mathbf{g}_{12} = \left. \frac{\mathbf{I}_1}{\mathbf{I}_2} \right|_{\mathbf{V}_1=0}$$

$$\mathbf{g}_{21} = \left. \frac{\mathbf{V}_2}{\mathbf{V}_1} \right|_{\mathbf{I}_2=0}, \quad \mathbf{g}_{22} = \left. \frac{\mathbf{V}_2}{\mathbf{I}_2} \right|_{\mathbf{V}_1=0}$$

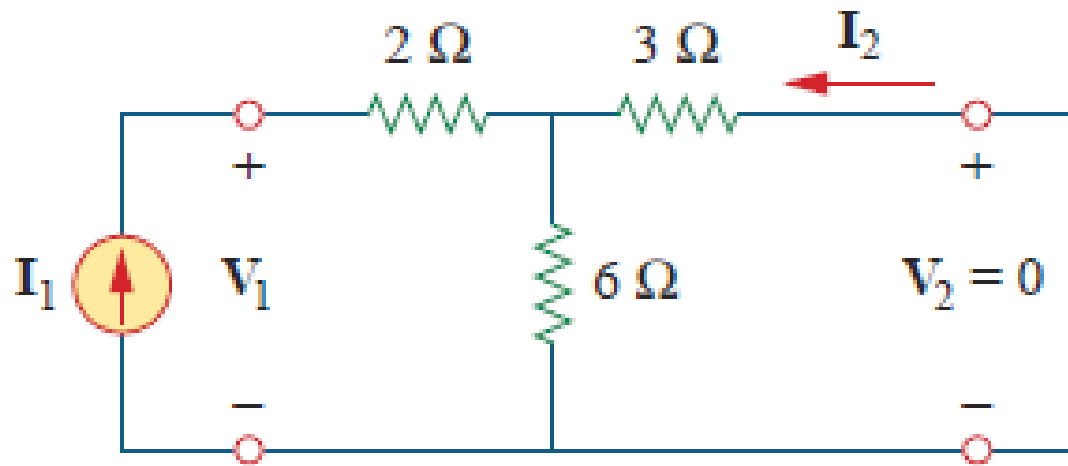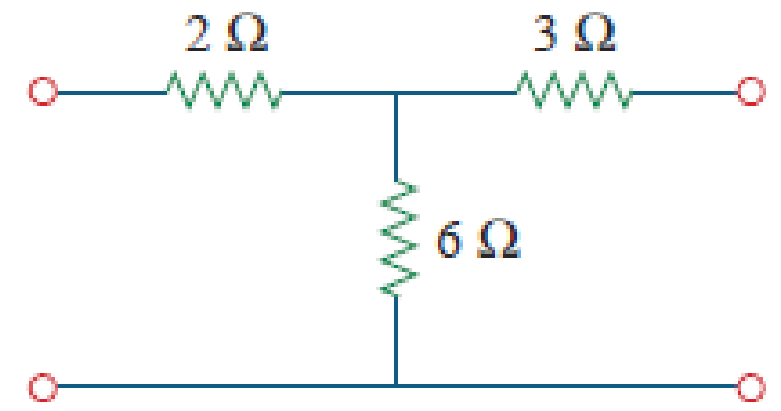
Find the hybrid parameters for the two-port network of Fig.



(a)

$$h_{11} = \frac{V_1}{I_1}$$

$$h_{21} = \frac{I_2}{I_1}$$

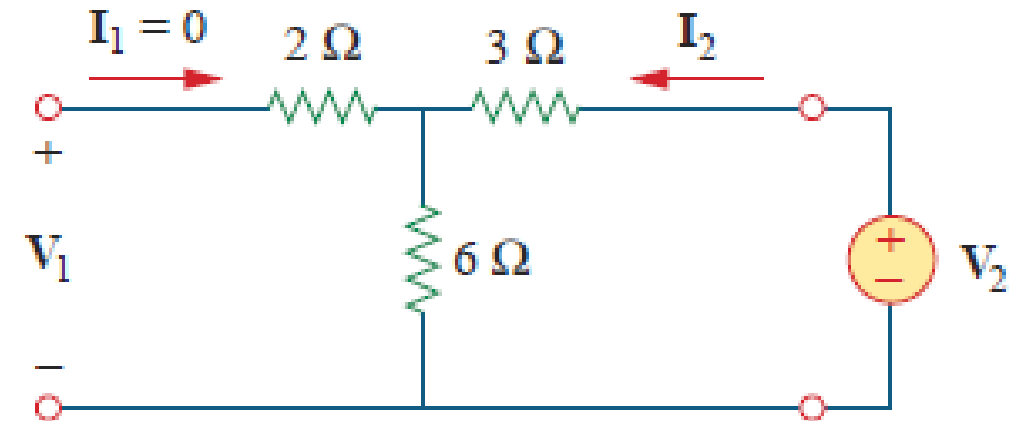


(b)

$$h_{12} = \frac{V_1}{V_2}$$

$$h_{22} = \frac{I_2}{V_2}$$

Hence,

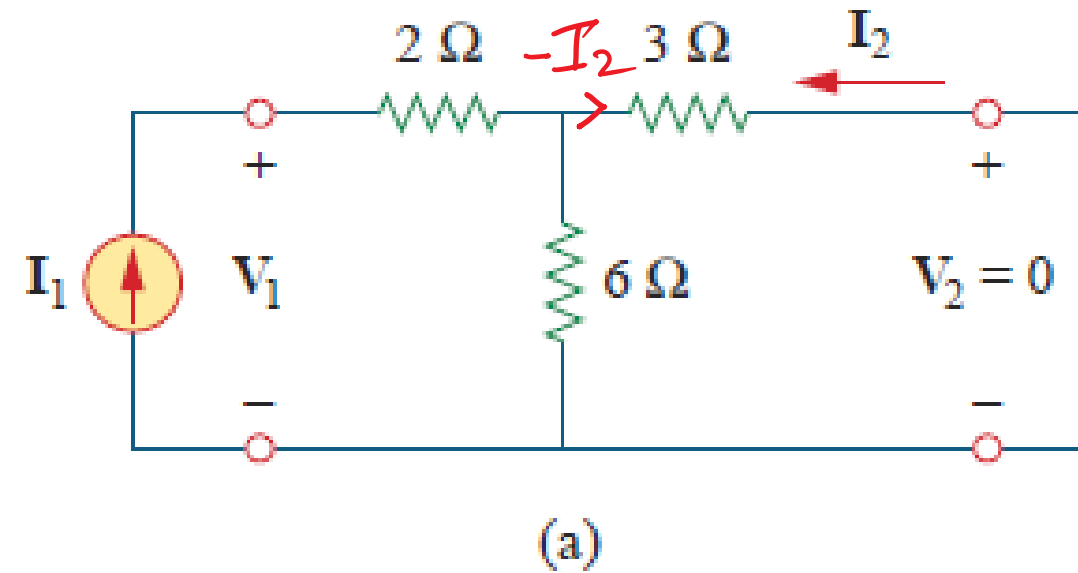

Hence,

$$V_1 = I_1(2 + \underline{\underline{3 \parallel 6}}) = 4I_1$$


$$h_{11} = \frac{V_1}{I_1} = \underline{\underline{4 \Omega}}$$

$$-I_2 = \frac{6}{6 + 3} I_1 = \frac{2}{3} I_1$$

$$h_{21} = \frac{I_2}{I_1} = -\frac{2}{3} \quad \checkmark$$



$$V_2 = 3I_2 + 6I_2 ; 9I_2 = V_2$$

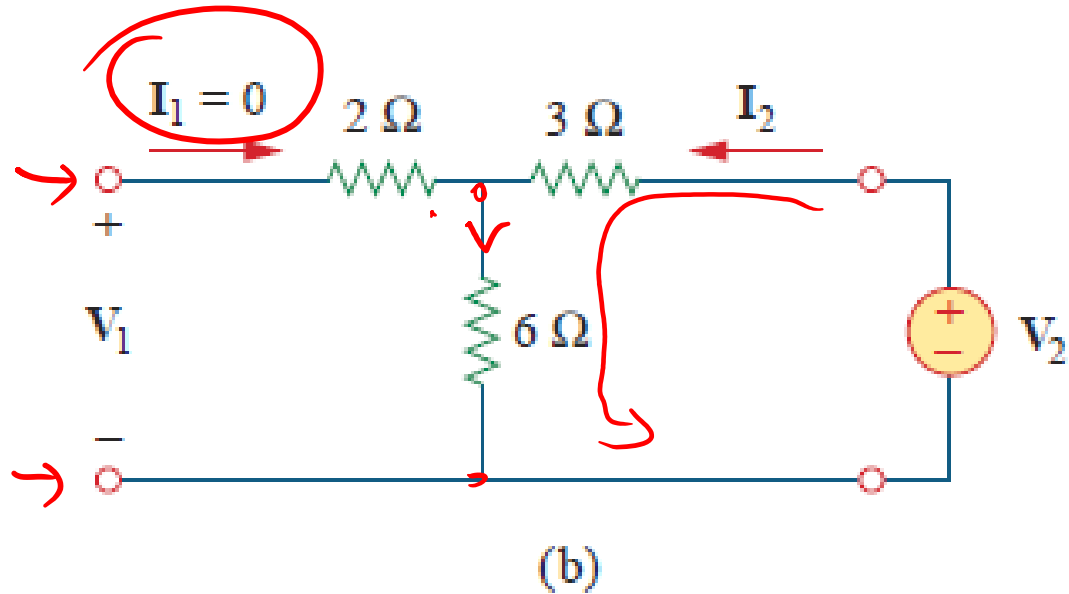

$$V_1 = \frac{6}{6+3} V_2 = \underline{\underline{\frac{2}{3} V_2}}$$

$$\checkmark h_{12} = \frac{V_1}{V_2} = \frac{2}{3}$$

$V_1 =$  Voltage across  $6\Omega$  resistance

$$I_2 = \frac{V_2}{9}$$

$$V_1 = \frac{6 V_2}{9} = \frac{2}{3} V_2$$


$$\underline{\underline{V_2 = (3+6)I_2 = 9I_2}}$$

$$\checkmark h_{22} = \frac{I_2}{V_2} = \frac{1}{9} \text{ S}$$

Determine the  $h$  parameters for the circuit in Fig. 19.24.

**Answer:**  $\mathbf{h_{11} = 2.4\ \Omega}$ ,  $\mathbf{h_{12} = 0.4}$ ,  $\mathbf{h_{21} = -0.4}$ ,  $\mathbf{h_{22} = 200\ mS}$ .

## Practice Problem 19.5

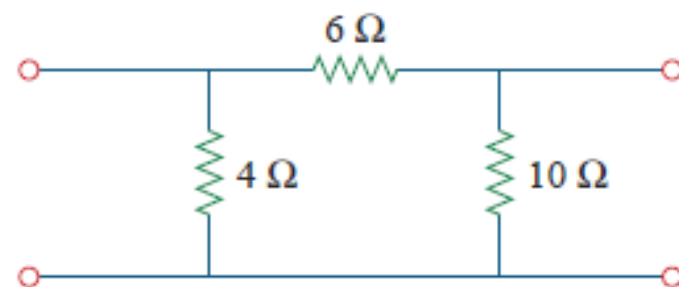


Determine the Thevenin equivalent at the output port of the circuit in

Fig.

To find  $Z_{TH}$  &  $V_{TH}$


$$V_1 = h_{11}I_1 + h_{12}V_2 \rightarrow \textcircled{1}$$
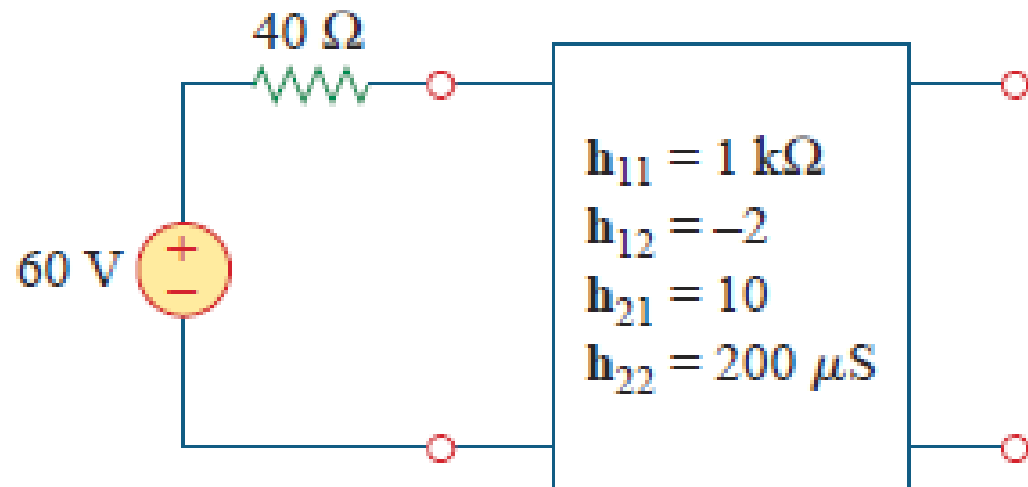
$$I_2 = h_{21}I_1 + h_{22}V_2 \rightarrow \textcircled{2}$$



$Z_{TH}$

Short the voltage source

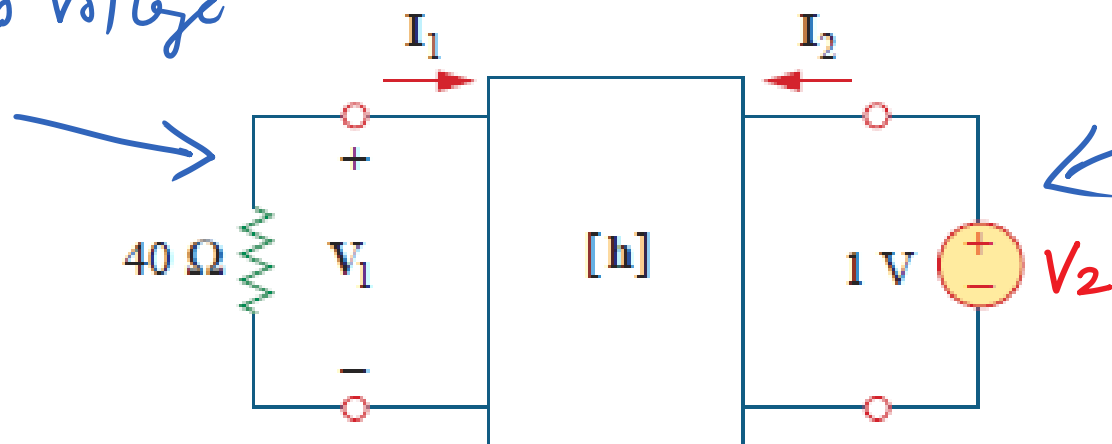

(a)

Connect test voltage source of 1V

Using  $\textcircled{2}$  in  $\textcircled{1}$

$$\rightarrow -40I_1 = h_{11}I_1 + h_{12} \checkmark$$

But  $V_2 = 1$ , and  $V_1 = -40I_1 \rightarrow \textcircled{3}$

$$I_1 = -\frac{h_{12}}{40 + h_{11}} \rightarrow \textcircled{4}$$

Since  $V_2 = 1V$  ; Eqn (2) becomes

$$I_2 = h_{21}I_1 + h_{22} \longrightarrow (5)$$


Using Eqn (4) in Eqn (5)

$$I_2 = h_{22} - \frac{h_{21}h_{12}}{h_{11} + 40} = \frac{h_{11}h_{22} - h_{21}h_{12} + h_{22}40}{h_{11} + 40} \longrightarrow (6)$$

Therefore,

$$Z_{Th} = \frac{V_2}{I_2} = \frac{1}{I_2} = \frac{h_{11} + 40}{h_{11}h_{22} - h_{21}h_{12} + h_{22}40} \longrightarrow (7)$$

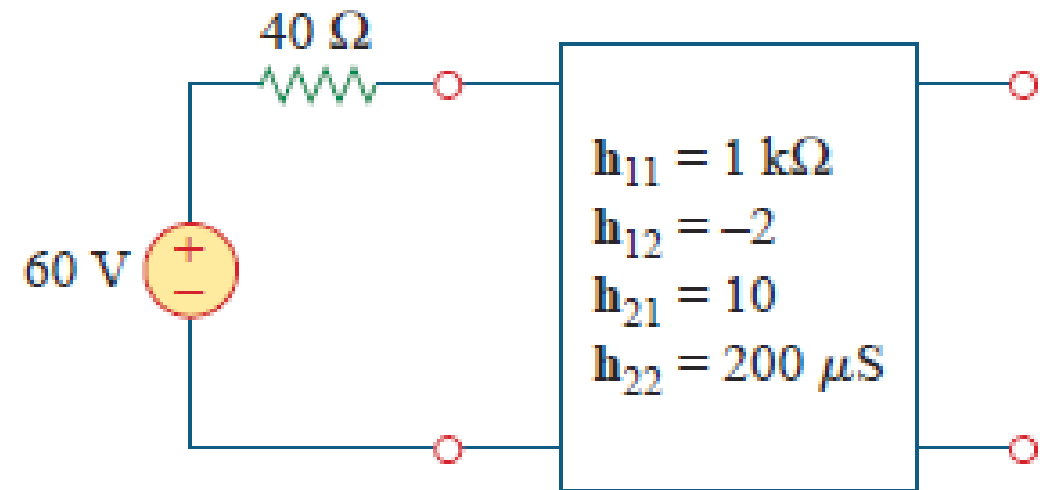
$$\mathbf{Z}_{\text{Th}} = \frac{\mathbf{V}_2}{\mathbf{I}_2} = \frac{1}{\mathbf{I}_2} = \frac{\mathbf{h}_{11} + 40}{\mathbf{h}_{11}\mathbf{h}_{22} - \mathbf{h}_{21}\mathbf{h}_{12} + \mathbf{h}_{22}40}$$



Substituting the values of the  $h$  parameters,

$$\begin{aligned} \mathbf{Z}_{\text{Th}} &= \frac{1000 + 40}{10^3 \times 200 \times 10^{-6} + 20 + 40 \times 200 \times 10^{-6}} \\ &= \frac{1040}{20.21} = \underline{\underline{51.46 \Omega}} \end{aligned}$$

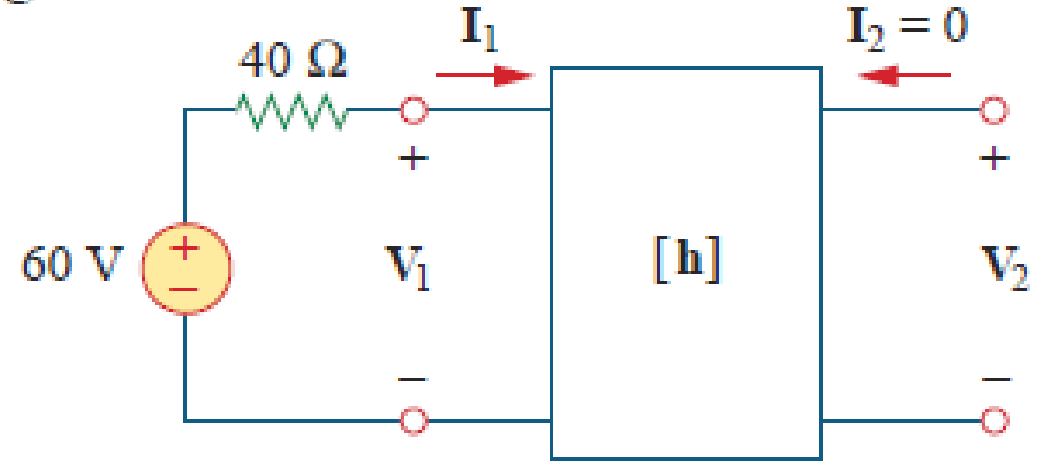To get  $V_{Th}$ , we find the open-circuit voltage  $V_2$  in Fig.



Apply KVL in the input port

$$-60 + 40I_1 + V_1 = 0$$

$\Rightarrow$

$$V_1 = 60 - 40I_1 \longrightarrow \textcircled{8}$$

At the output,

$$I_2 = 0 \longrightarrow \textcircled{9}$$

Using Eqs. (8) & (9) in  
Eqs. (1) and (2)

$$V_1 = h_{11}I_1 + h_{12}V_2 \longrightarrow (1)$$

$$I_2 = h_{21}I_1 + h_{22}V_2 \longrightarrow (2)$$

$$60 - 40I_1 = h_{11}I_1 + h_{12}V_2 \checkmark$$

$$60 = (h_{11} + 40)I_1 + h_{12}V_2 \longrightarrow (10)$$

$$0 = h_{21}I_1 + h_{22}V_2 \Rightarrow I_1 = -\frac{h_{22}}{h_{21}}V_2 \checkmark \longrightarrow (11)$$

Using Eqn (11) in Eqn (10)

$$60 = \left[ -(\mathbf{h}_{11} + 40) \frac{\mathbf{h}_{22}}{\mathbf{h}_{21}} + \mathbf{h}_{12} \right] \mathbf{V}_2$$

or

$$\mathbf{V}_{Th} = \mathbf{V}_2 = \frac{60}{-(\mathbf{h}_{11} + 40)\mathbf{h}_{22}/\mathbf{h}_{21} + \mathbf{h}_{12}} = \frac{60\mathbf{h}_{21}}{\mathbf{h}_{12}\mathbf{h}_{21} - \mathbf{h}_{11}\mathbf{h}_{22} - 40\mathbf{h}_{22}}$$

Substituting the values of the  $h$  parameters,

$$\mathbf{V}_{Th} = \frac{60 \times 10}{-20.21} = \underline{\underline{-29.69 \text{ V}}}$$

$V_{Th}$  is the open circuit voltage