

Fundamental Cut-set Matrix

- Fundamental cut set or **f-cut set** is the minimum number of branches that are removed from a graph in such a way that the original graph will become two isolated subgraphs.
- The f-cut set contains only one twig and one or more links.
- The number of f-cut sets will be equal to the number of twigs.
- Fundamental cut set matrix is represented with letter C . This matrix gives the relation between branch voltages and twig voltages.

- If there are 'n' nodes and 'b' branches are present in a directed graph, then the number of twigs present in a selected Tree of given graph will be $n-1$.
- The fundamental cut set matrix will have 'n-1' rows and 'b' columns.
- Rows and columns are corresponding to the twigs of selected tree and branches of given graph.
- The order of fundamental cut set matrix will be $(n-1) \times b$.

The elements of fundamental cut set matrix will be having one of these three values, +1, -1 and 0.


- **The value of element will be +1 for the twig of selected f-cutset.**
- The value of elements will be 0 for the remaining twigs and links, which are not part of the selected f-cut set.
- If the direction of link current of selected f-cut set is same as that of the cut set twig current, then the value of element will be +1.
- If the direction of link current of selected f-cut set is opposite to that of off-cut set twig current, then the value of element will be -1.

Procedure to find Fundamental Cut-set Matrix


- To find the fundamental cut set matrix of given directed graph.
- Select a Tree of given directed graph and represent the links with the dotted lines.
- By removing one twig and necessary links at a time, we get one f-cut set. Fill the values of elements corresponding to this f-cut set in a row of fundamental cut set matrix.
- Repeat the above step for all twigs.

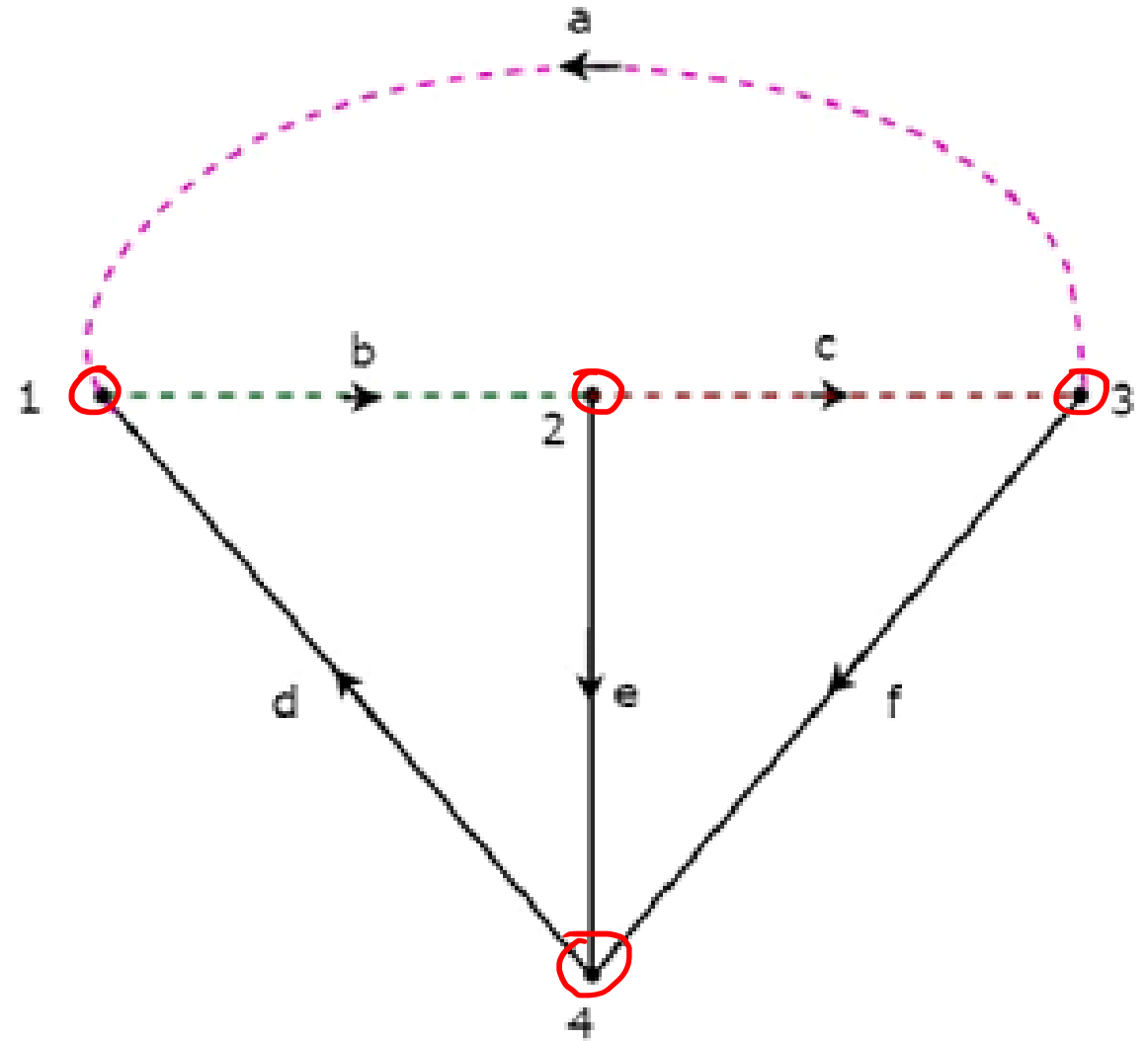
Example

- Consider the same **directed graph**
- Select the **branches d, e & f** of this directed graph as **twigs**.
- The remaining **branches a, b & c** of this directed graph will be the **links**.
- The **twigs d, e & f** are represented with solid lines
- The **links a, b & c** are represented with dotted lines in the figure.




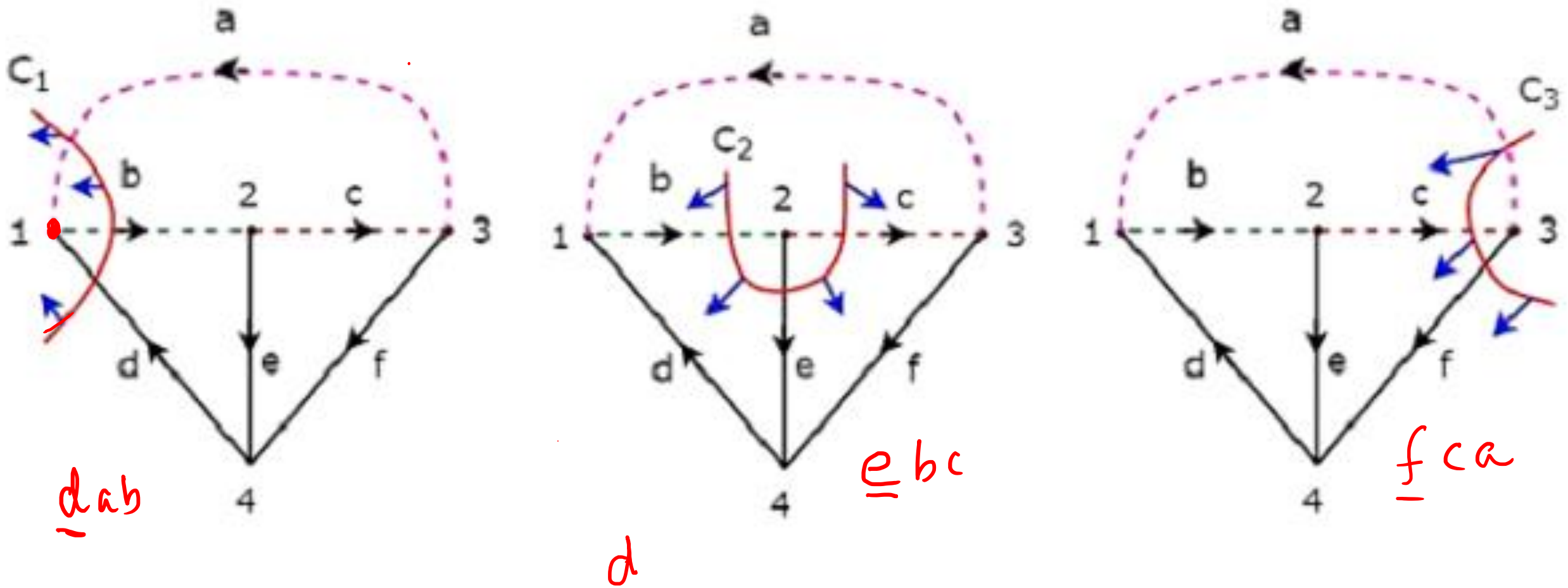- By removing one twig and necessary links at a time, we will get one f-cut set.
- So, there will be **three f-cut sets**, since there are three twigs. These three f-cut sets are shown in the following figure.




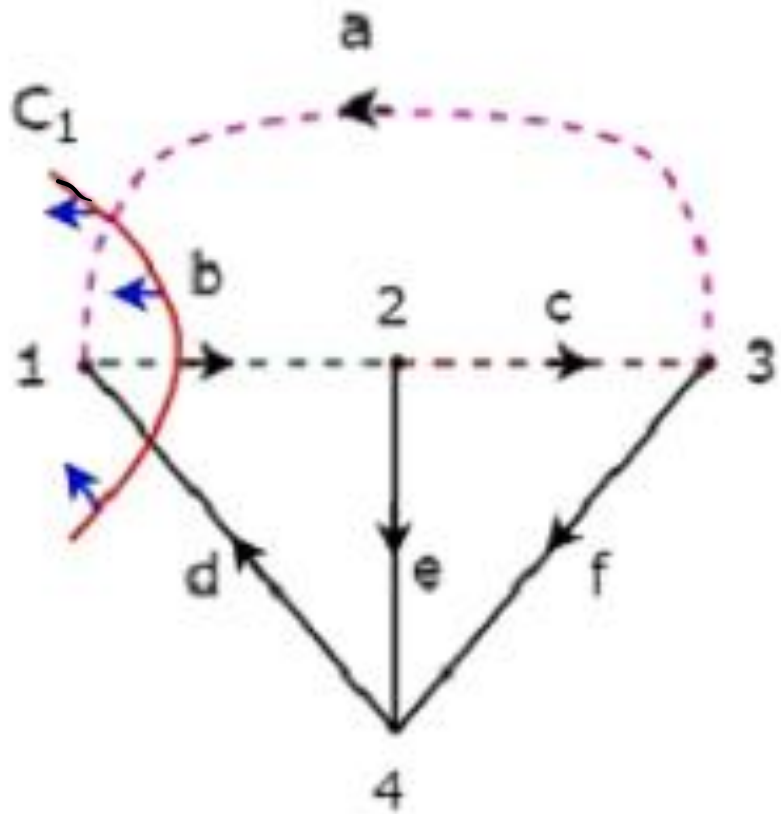

dab

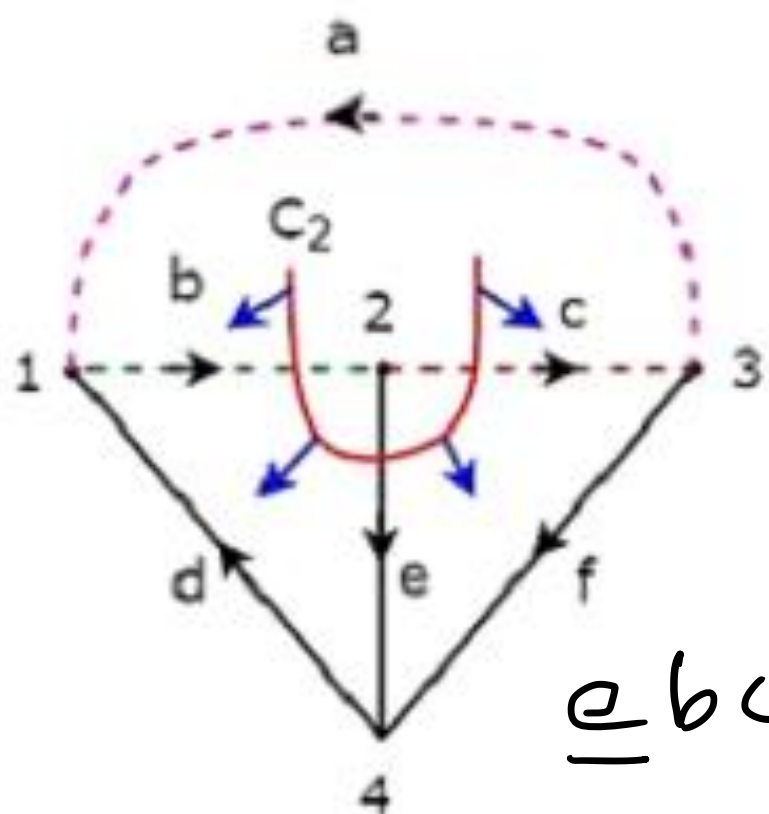

abc

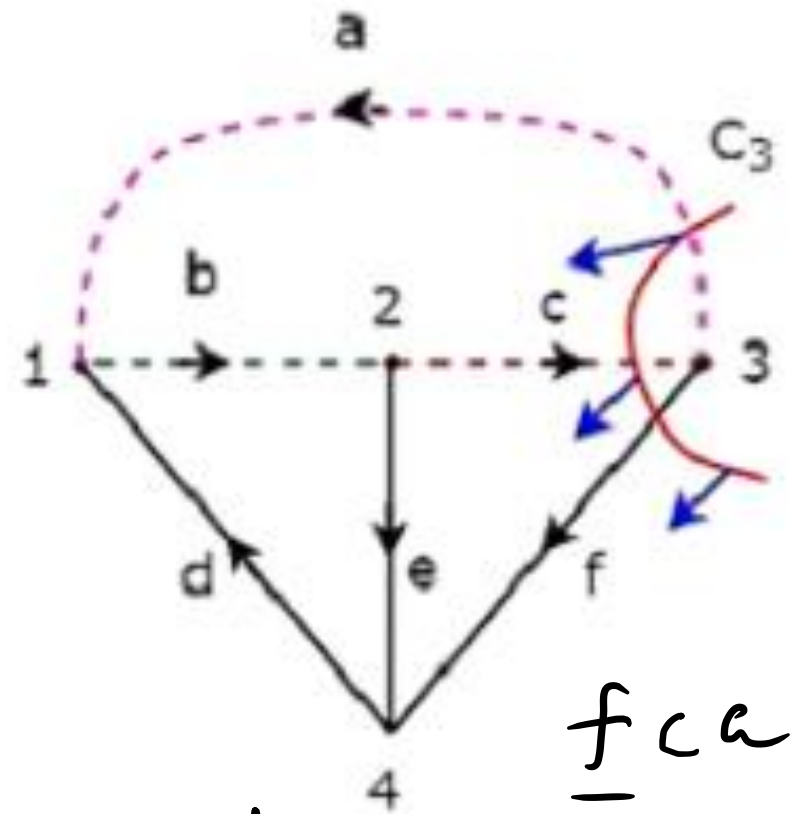






fca

$$C = \begin{matrix} & \begin{matrix} a & b & c & d & e & f \end{matrix} \\ \begin{matrix} c_1 \\ c_2 \\ c_3 \end{matrix} & \begin{bmatrix} 1 & -1 & 0 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \\ 1 & 0 & -1 & 0 & 0 & 1 \end{bmatrix} \end{matrix}$$

$$C = \begin{bmatrix} 1 & -1 & 0 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \\ 1 & 0 & -1 & 0 & 0 & 1 \end{bmatrix}$$

- The rows and columns of the above matrix represents the twigs and branches of given directed graph.
- The order of this fundamental cut set matrix is 3×6 .
- The number of Fundamental cut set matrices of a directed graph will be equal to the number of Trees of that directed graph. Because, every Tree will be having one Fundamental cut set matrix.

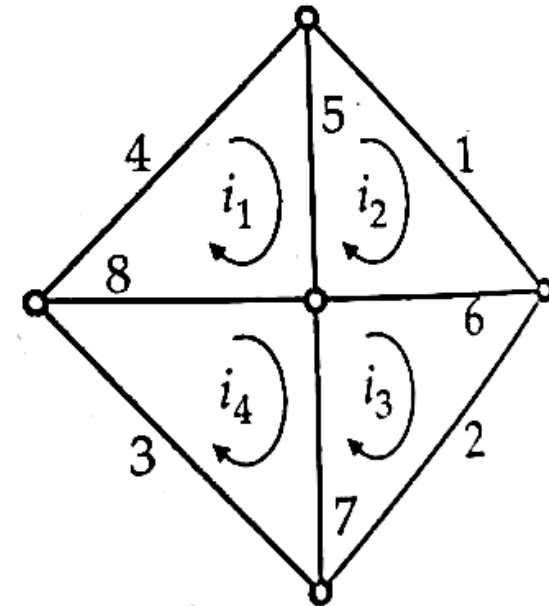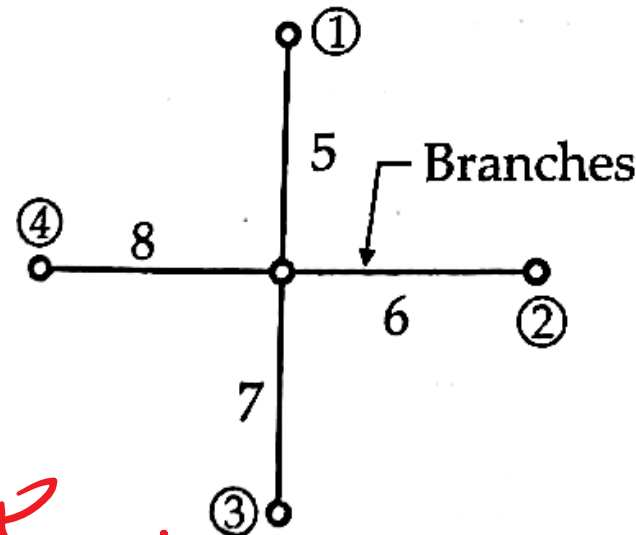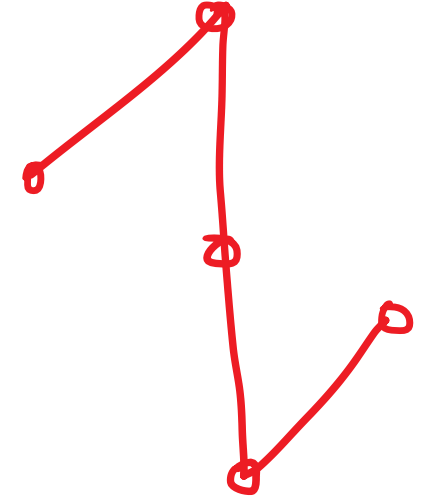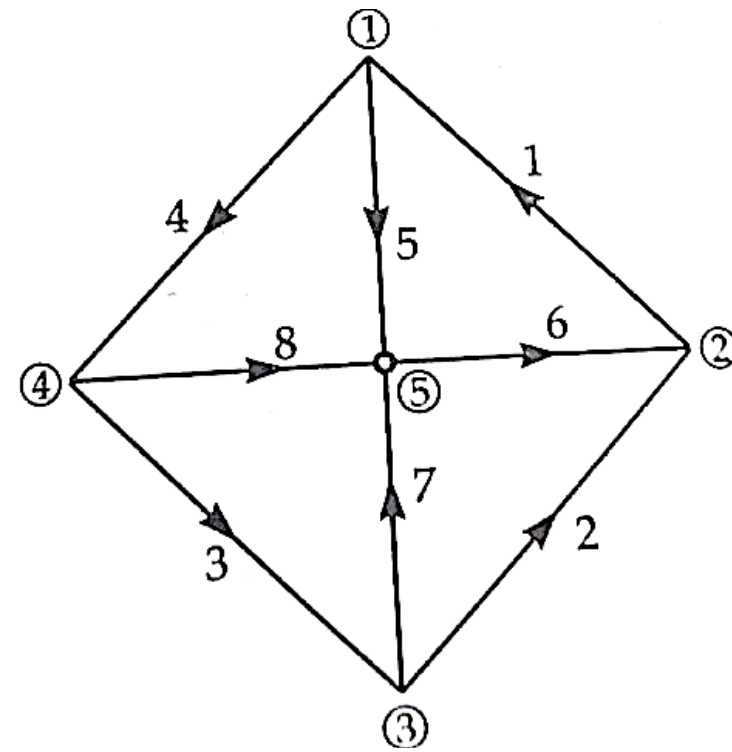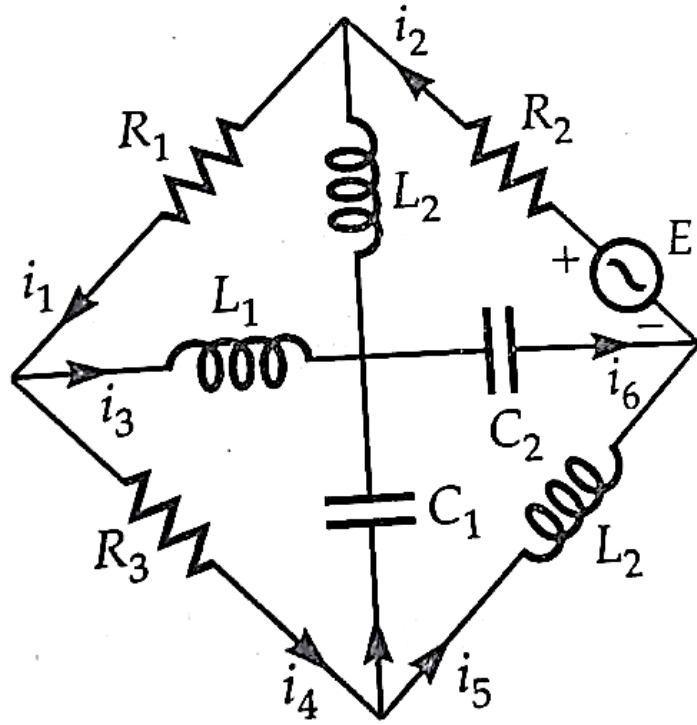
Example: Draw the directed graph of the network shown in



i_1, i_2, i_3 & i_4
are the arbitrary loop currents


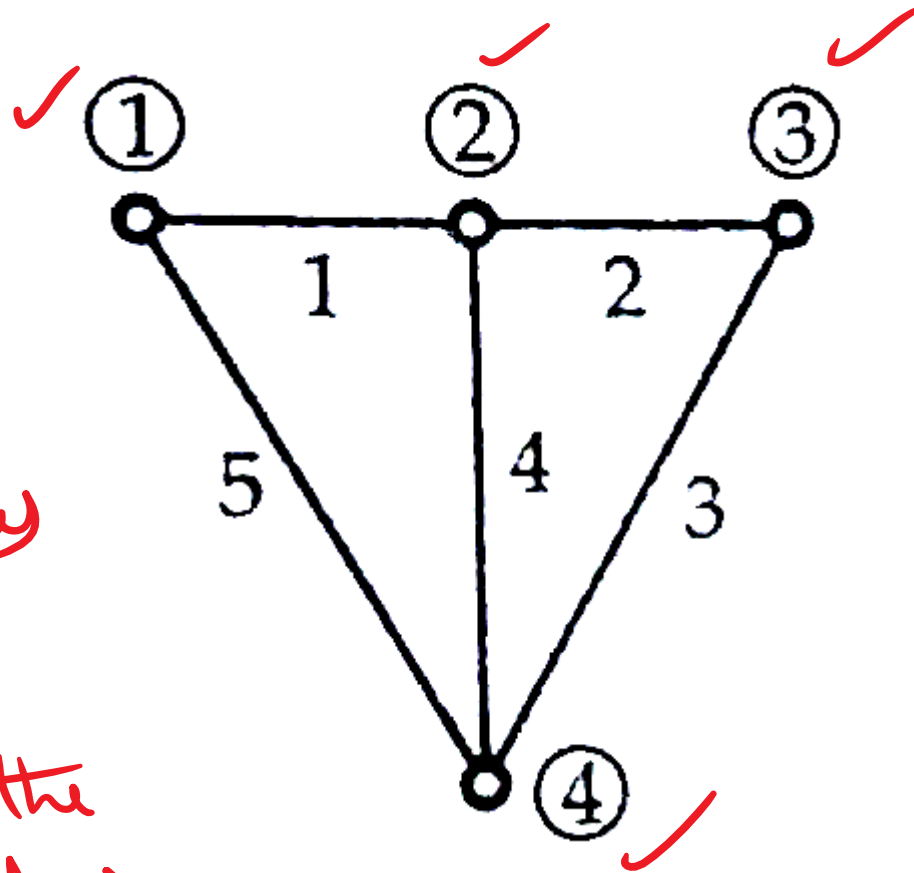
Example



Give the graph of a network. Show the possible TREES, TWIGS and LINKS



1, 2, 3, 4, 5
are the branches


① ② ③ ④ are the nodes

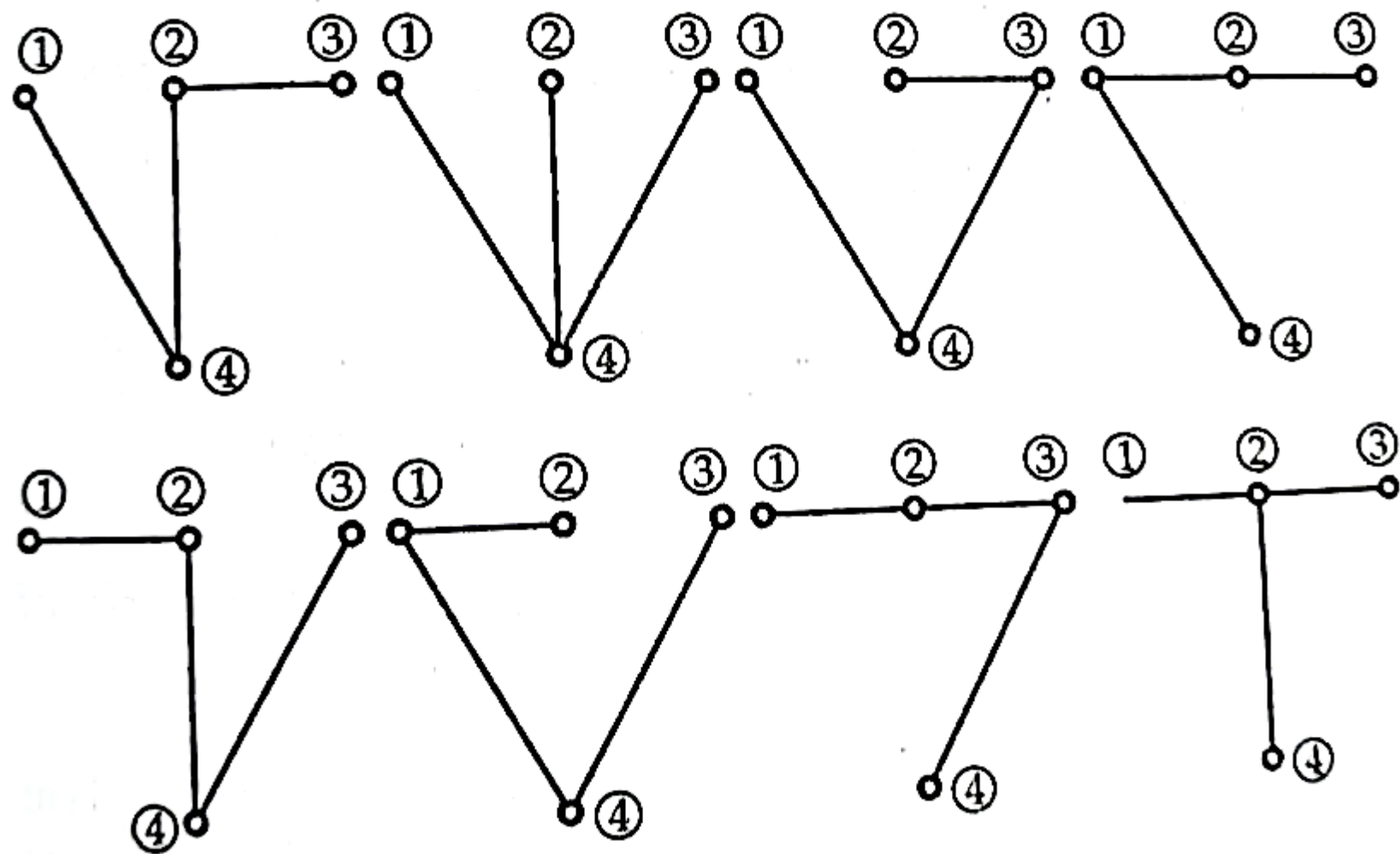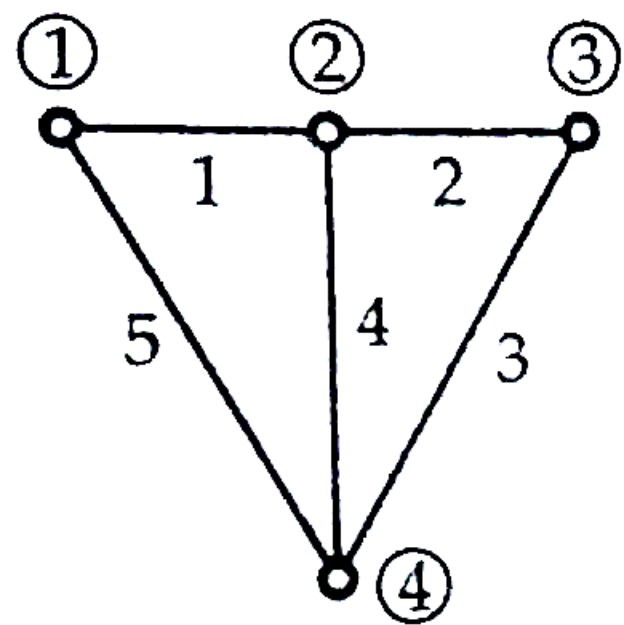


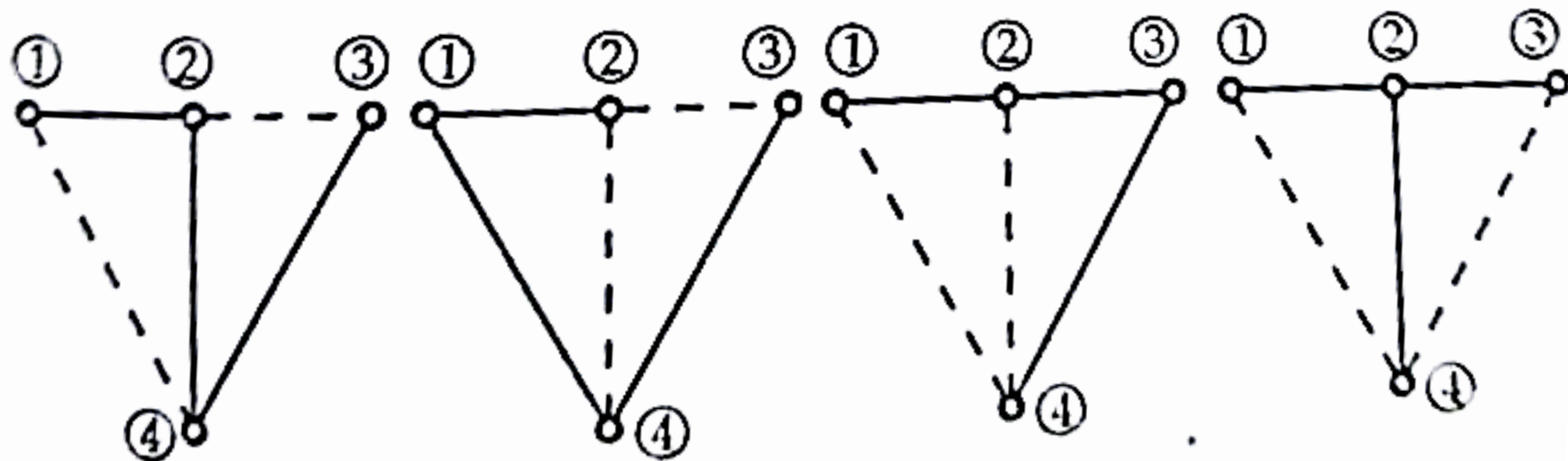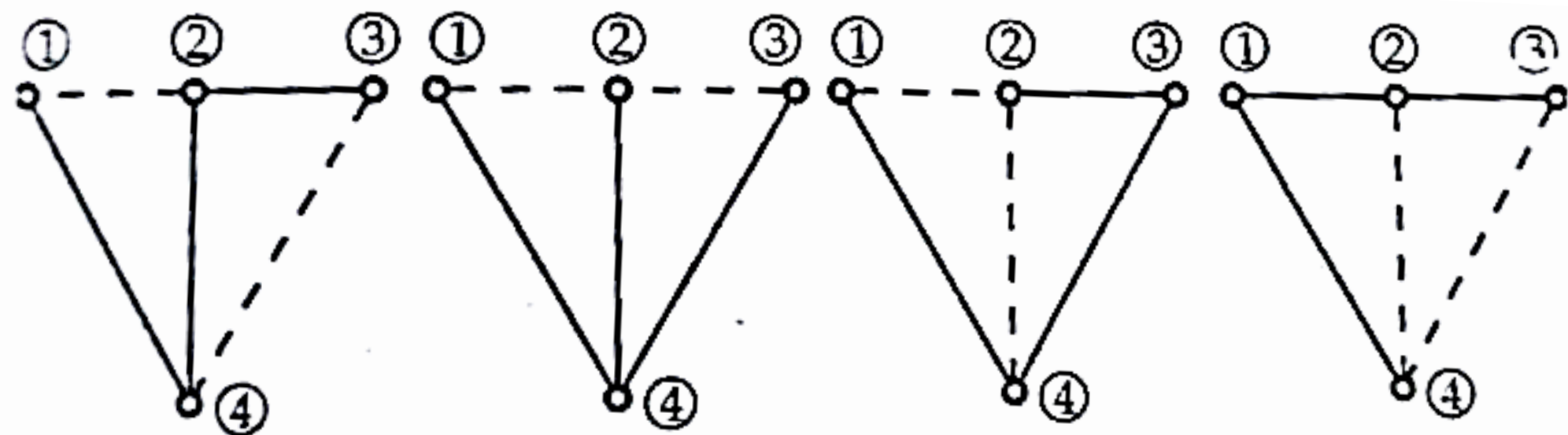

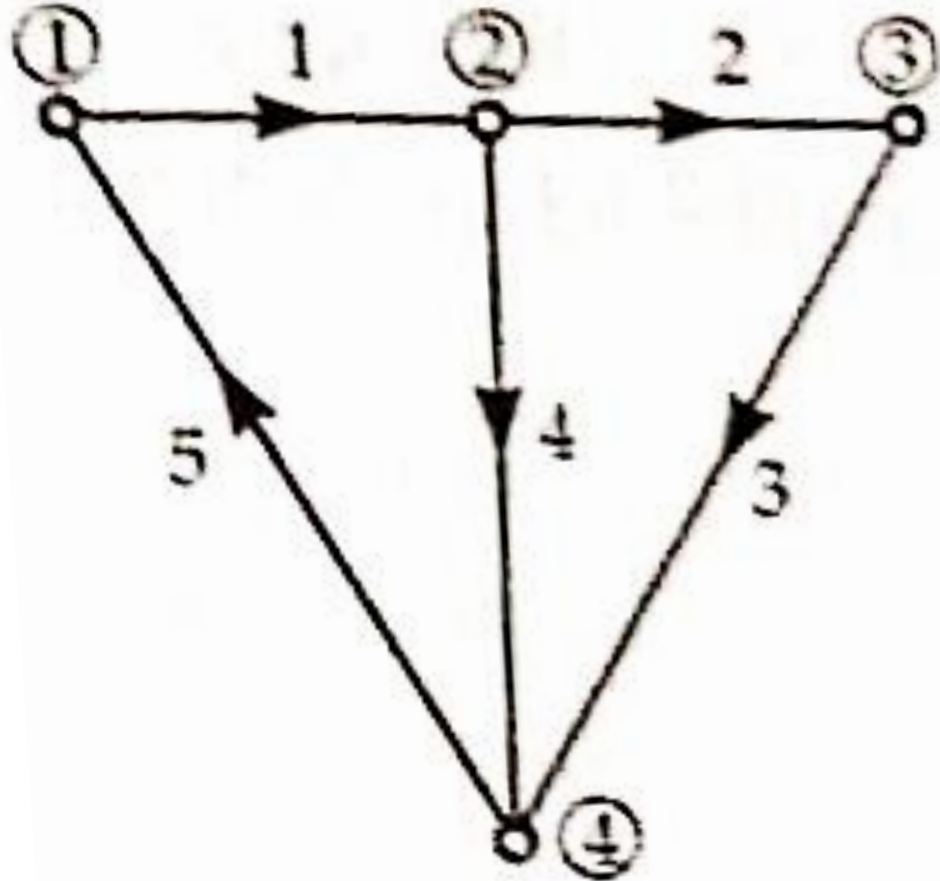
Example

Develop the fundamental TIE-SET matrix for the following directed graph



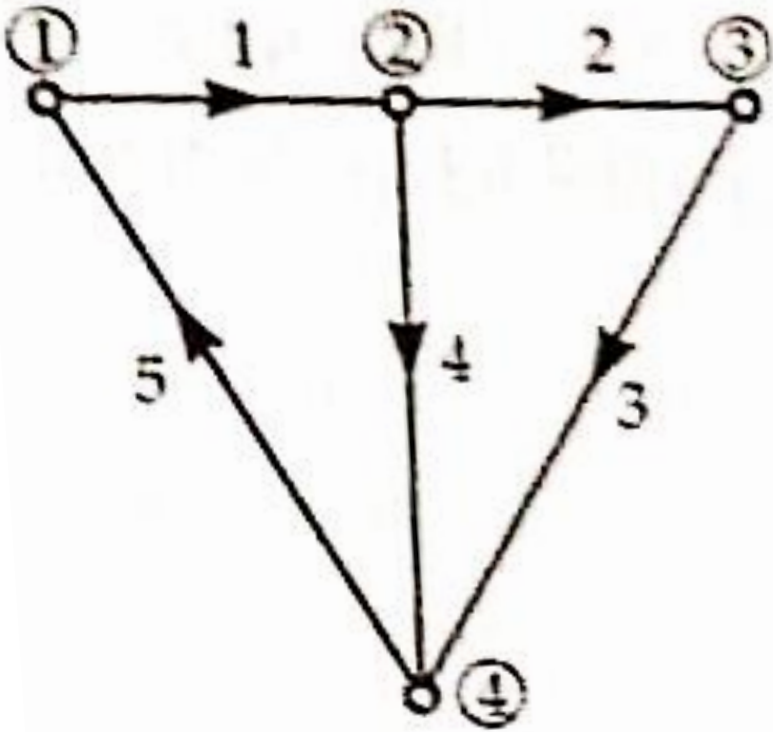


graph



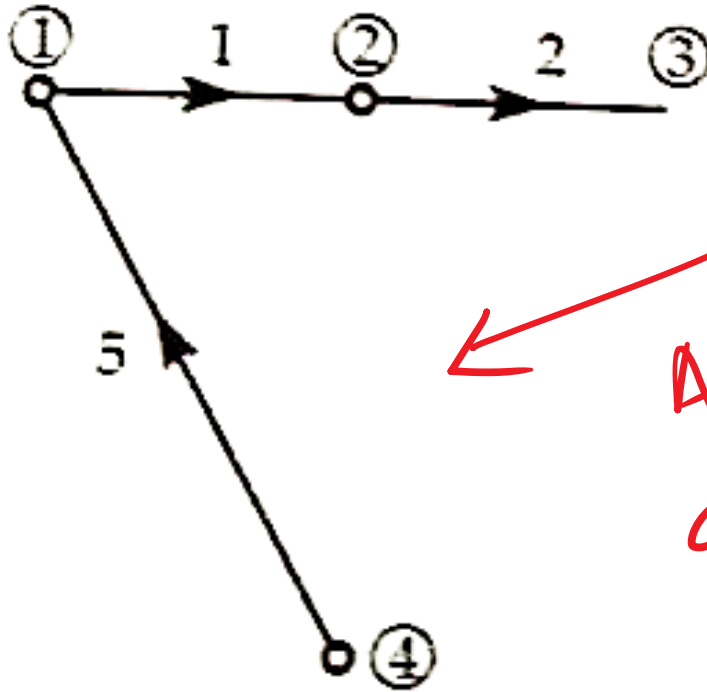


selected
Tree (3 Twigs)

← All nodes included
and open

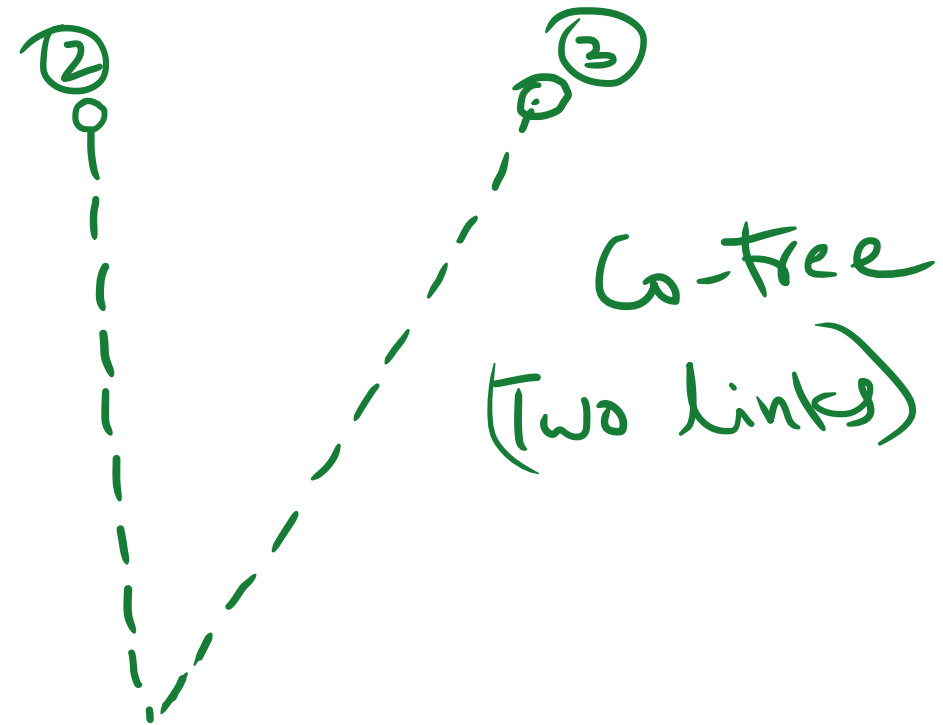


Co-tree
(Two links)

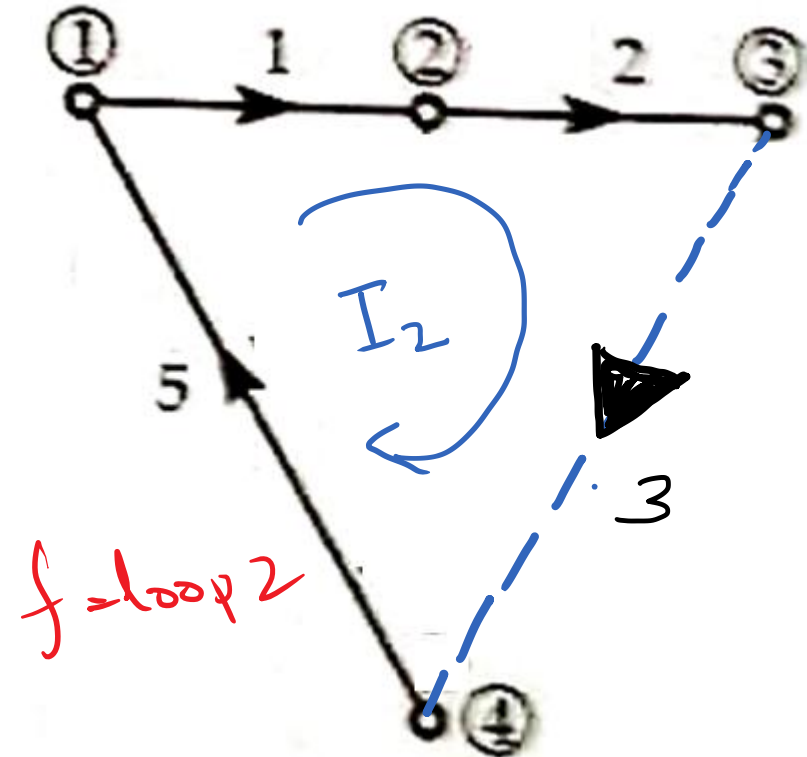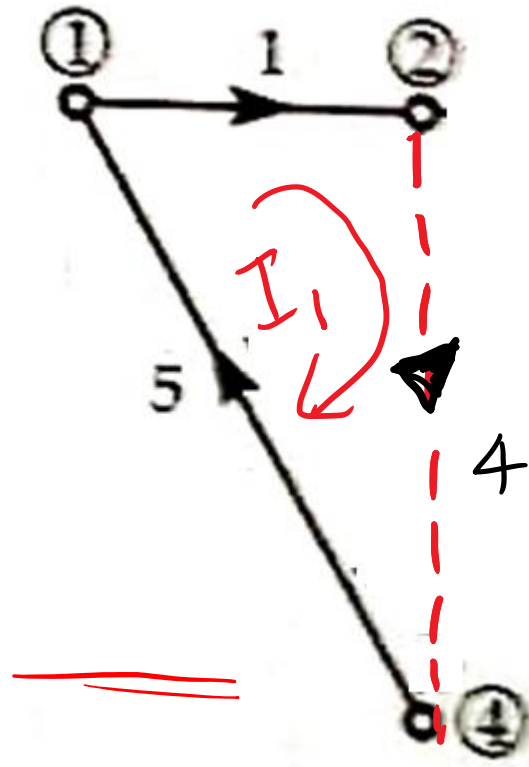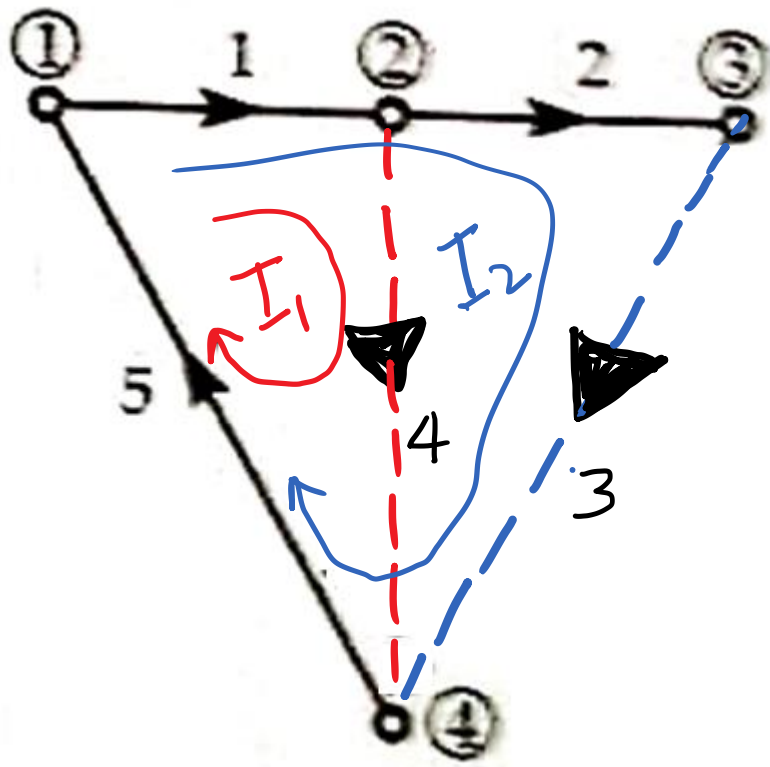

Tie-sets (or loop currents)	Branches				
	1	2	3	4	5
I_1	1	0	0	1	1
I_2	1	1	1	0	1

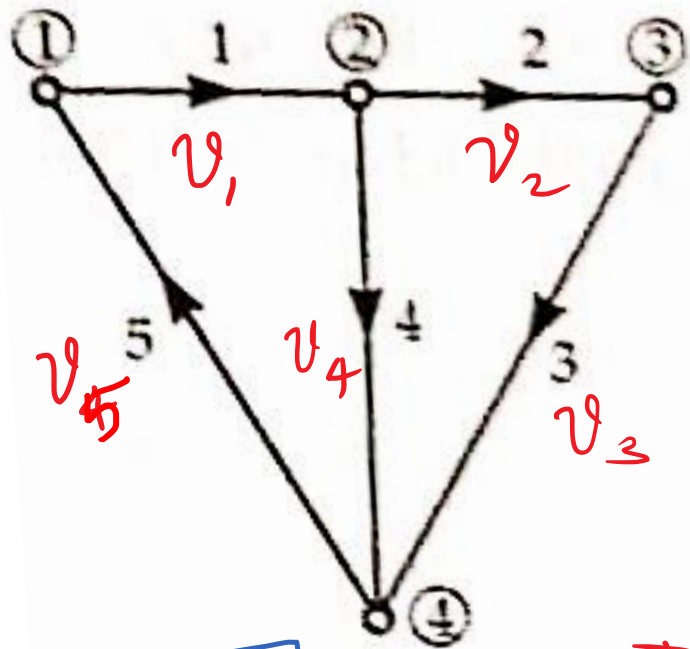Assume the direction of the link is the direction of the loop current I_1 or I_2



Tie-sets
(or loop currents)

Branches

I_1

I_2

	1	2	3	4	5
I_1	1	0	0	1	1
I_2	1	1	1	0	1

Summation
of row
voltages

If v_1, v_2, v_3, v_4 and v_5 are the branch voltages

Then $v_1 + 0 + 0 + v_4 + v_5 = 0$


$$v_1 + v_4 + v_5 = 0$$

← 1st row

Similarly,

$$v_1 + v_2 + v_3 + v_5 = 0$$

← 2nd row

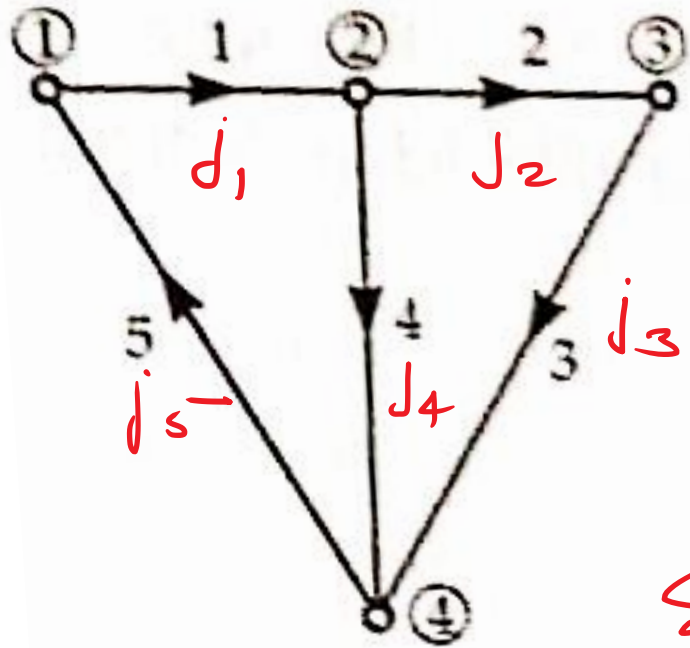

Tie-sets
(or loop currents)

Branches

I_1

I_2




	1	2	3	4	5
I_1	1	0	0	1	1
I_2	1	1	1	0	1

Similarly each branch currents (j) is given by the algebraic sum of link currents

$$\begin{array}{l} I_1 + I_2 = j_1 \\ 0 + I_2 = j_2 \\ 0 + I_2 = j_3 \end{array} \left[\begin{array}{l} I_1 + 0 = j_4 \\ I_1 + I_2 = j_5 \end{array} \right]$$

Summation
of column
currents

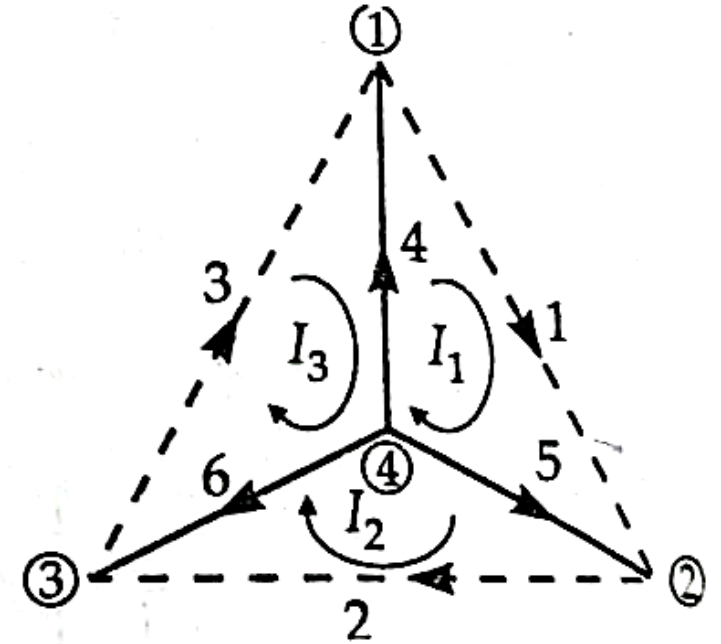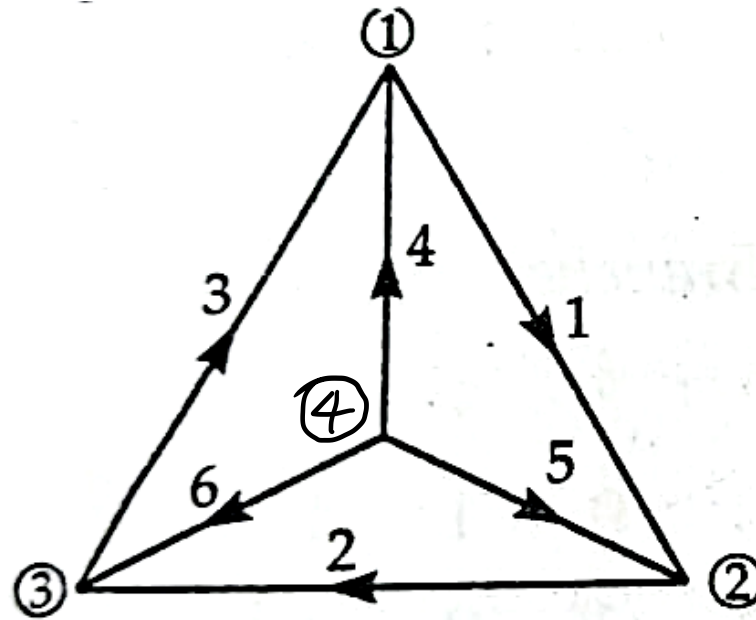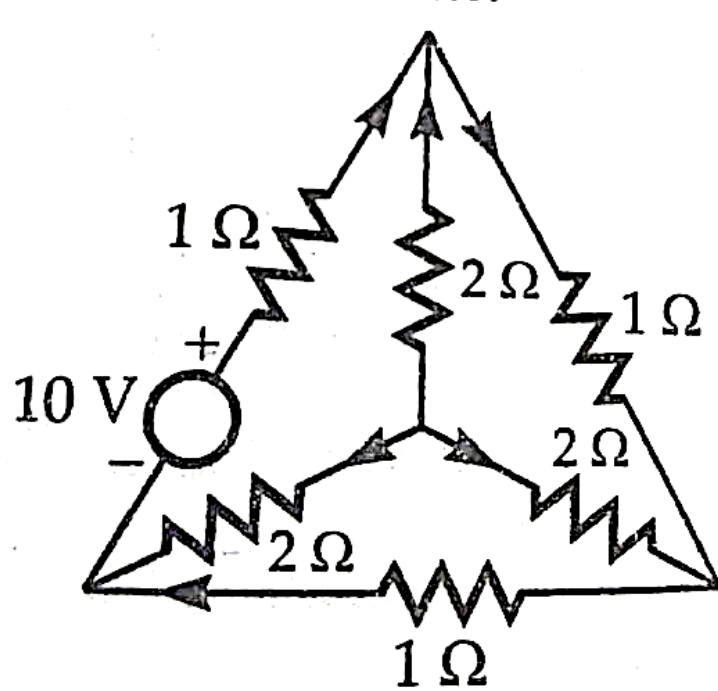Example: Draw the graph and develop the fundamental TIE-SET matrix



Branches


Tie-set (loop)




	1	2	3	4	5	6
I_1	1	0	0	1	-1	0
I_2	0	1	0	0	1	-1
I_3	0	0	1	-1	0	1

Find the branch currents?

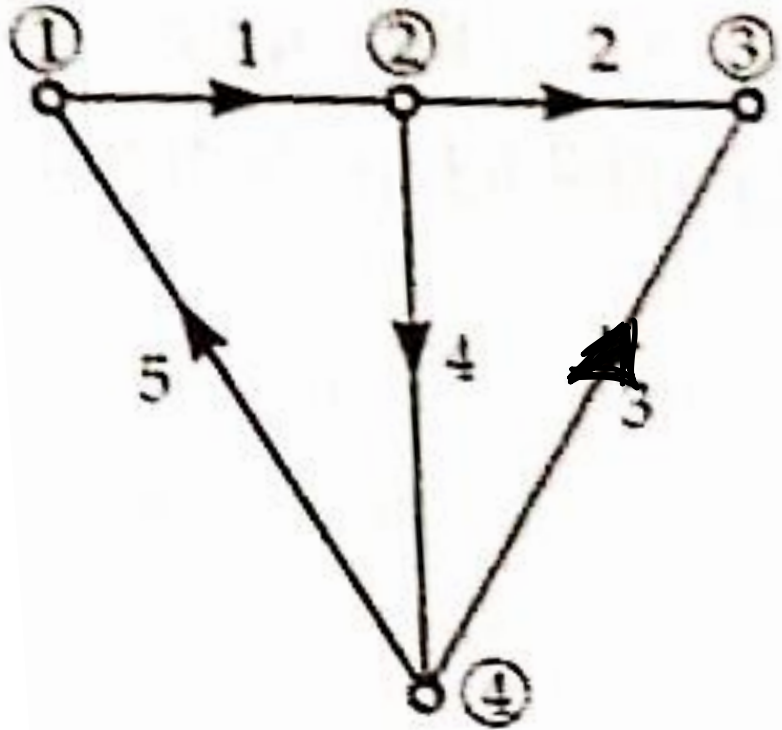
Example

Develop the fundamental CUT-SET matrix for the following directed graph



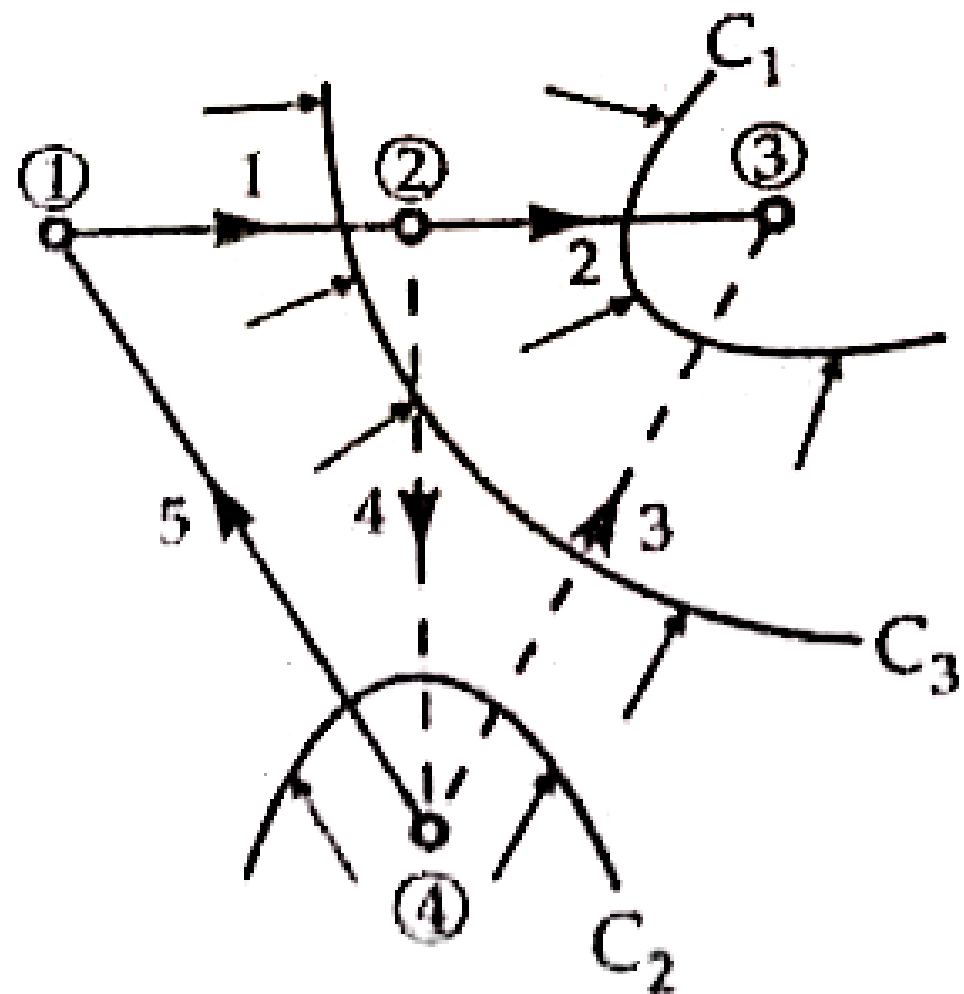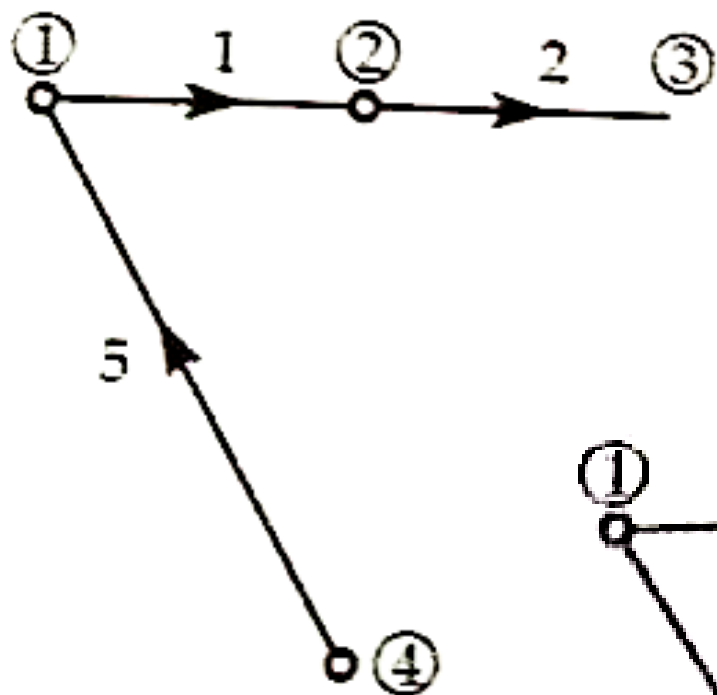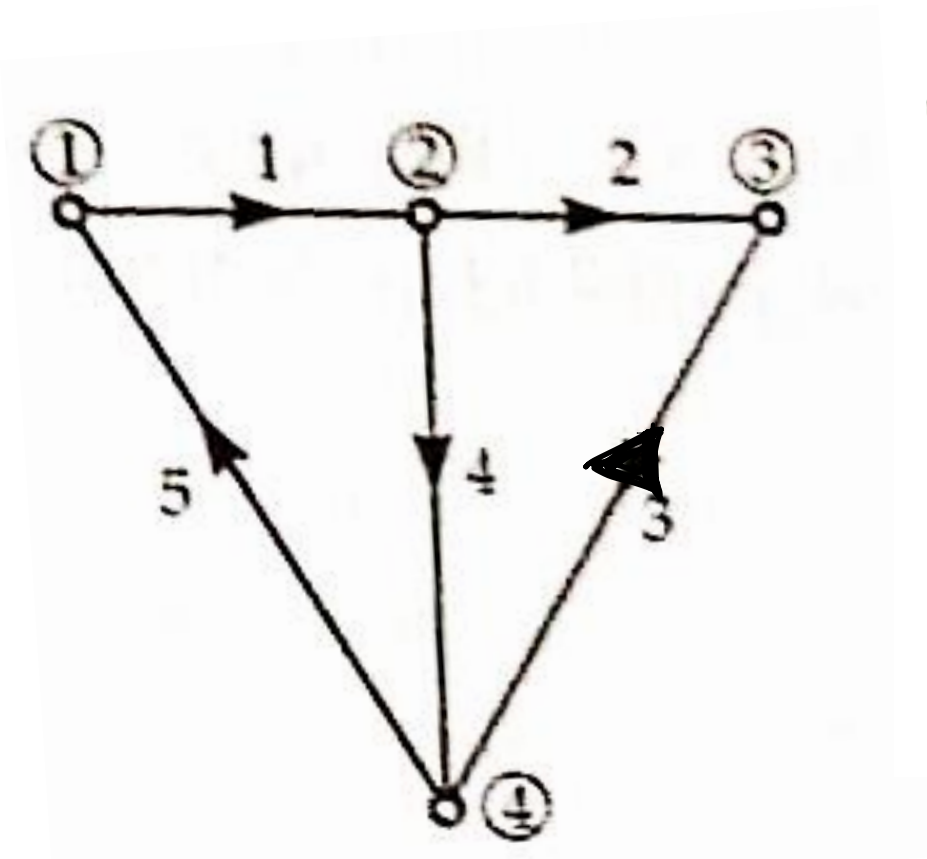

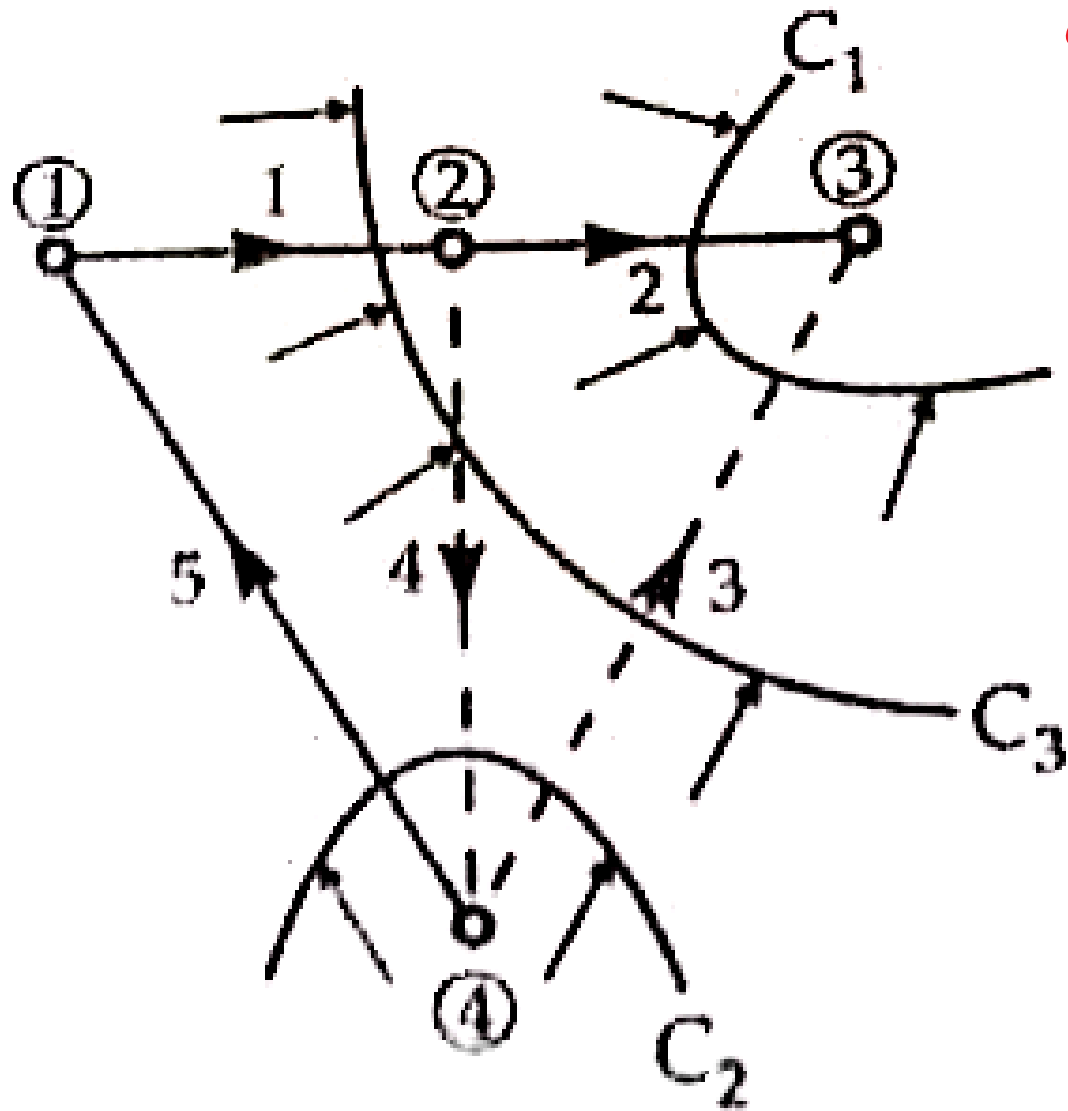The direction of the twig current is taken as reference



CUT SET C_1 : TWIG 2 & LINK 3

CUT SET C_2 : TWIG 5 & LINKS 3 & 4

CUT SET C_3 : TWIG 1 & LINKS 4 & 3

Cut-sets	Branches				
	1	2	3	4	5
C_1	0	+1	+1	0	0
C_2	0	0	+1	-1	+1
C_3	+1	0	+1	-1	0


Cut-sets	Branches				
	1	2	3	4	5
C_1	0	+1	+1	0	0
C_2	0	0	+1	-1	+1
C_3	+1	0	+1	-1	0

The current balance equations can be obtained from cut-set matrix




$$\dot{i}_2 + \dot{i}_3 = 0 \longrightarrow \textcircled{1}$$

$$\dot{i}_3 - \dot{i}_4 + \dot{i}_5 = 0 \longrightarrow \textcircled{2}$$
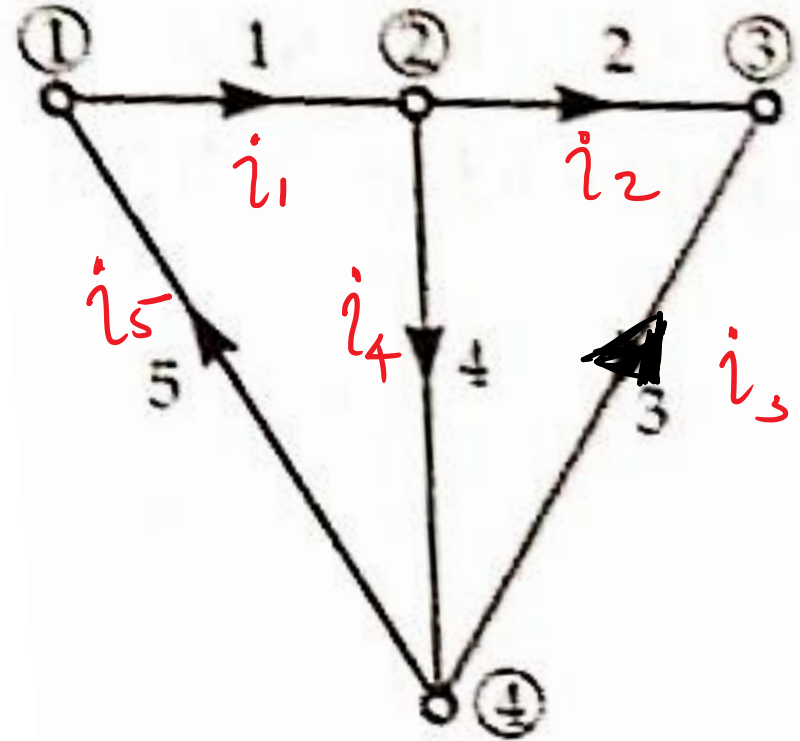
$$\dot{i}_1 + \dot{i}_3 - \dot{i}_4 = 0 \longrightarrow \textcircled{3}$$



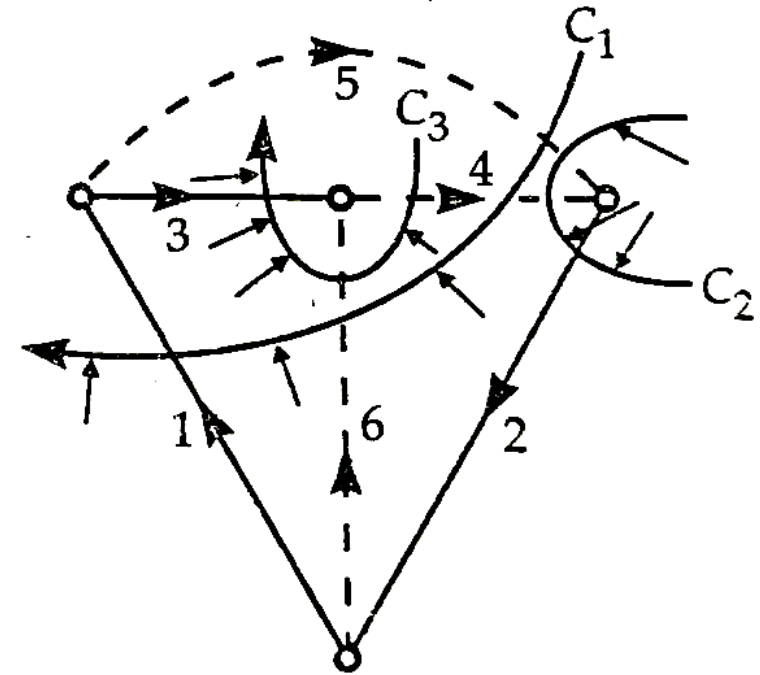
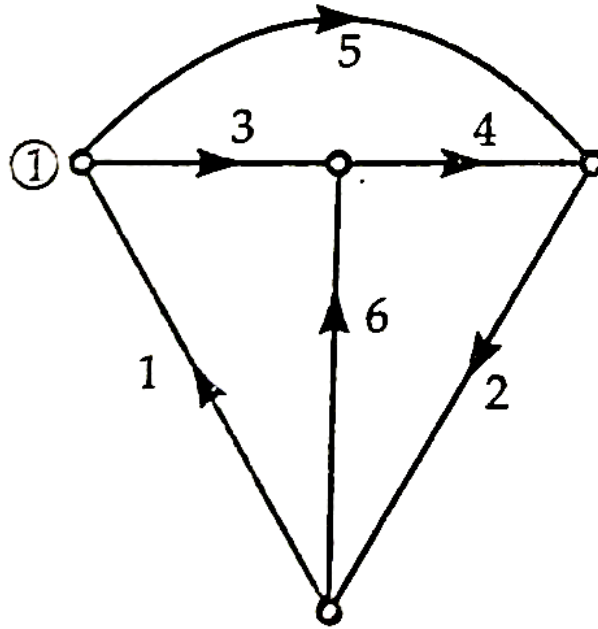
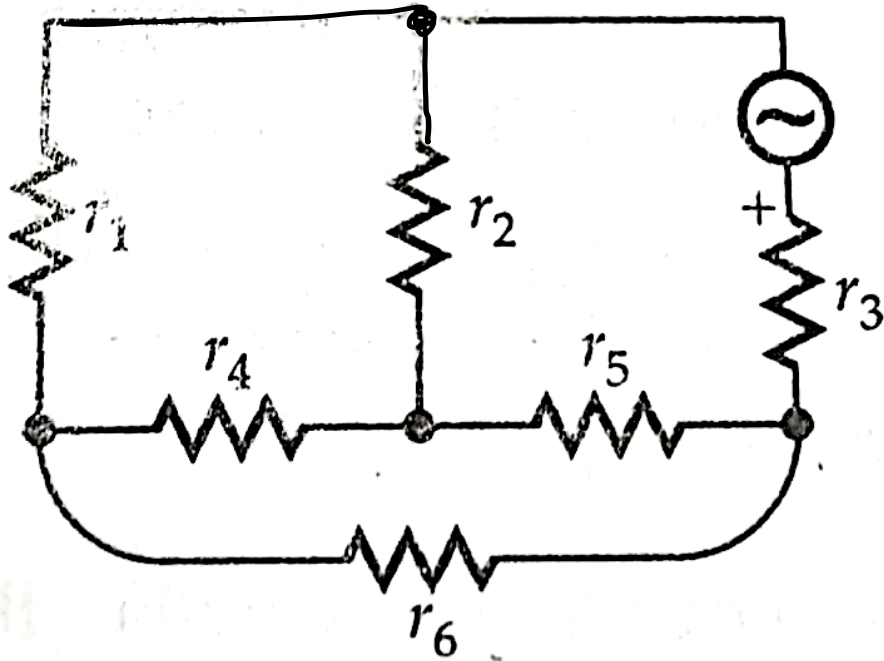
Example: Develop the fundamental CUT-SET matrix for the following circuit



Obtain the current balance equations?

Cut-sets	Branches					
	1	2	3	4	5	6
$C_1 [1, 6, 4]$	1	0	0	-1	0	1
$C_2 [2, 4, 5]$	0	1	0	-1	-1	0
$C_3 [3, 6, 4]$	0	0	+1	-1	0	+1

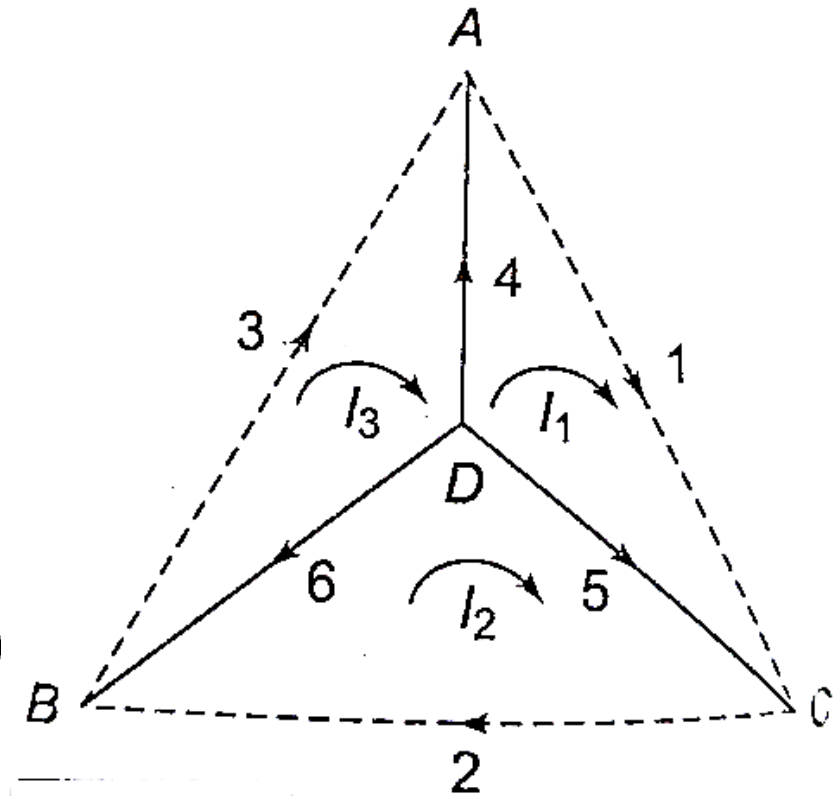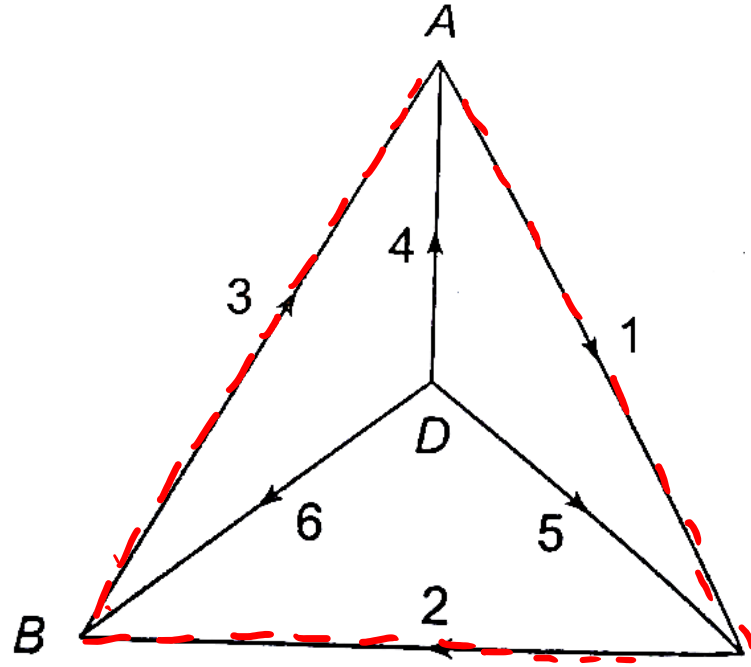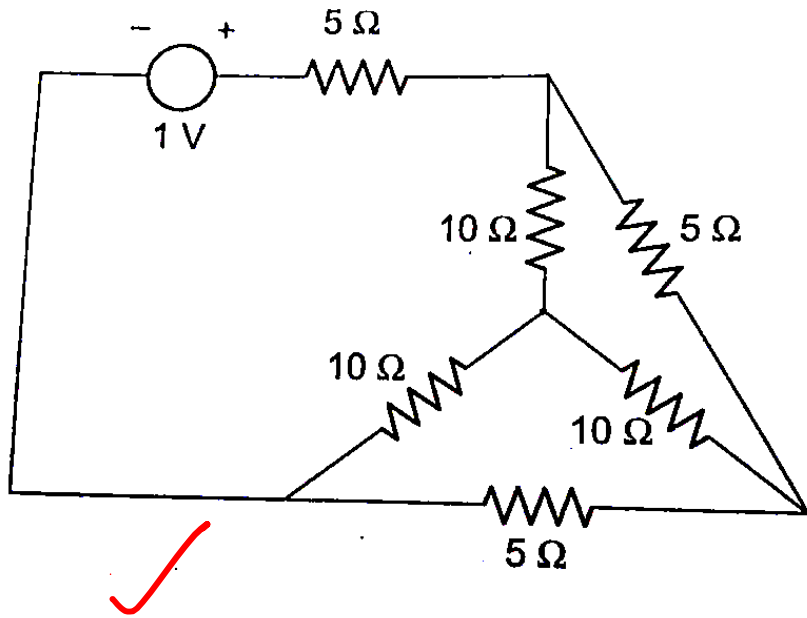Example: For the given network, draw the network graph. Select tree branches as 4, 5, 6. Write TIE-SET matrix and develop equilibrium equations and calculate the loop currents.



Links \rightarrow 1, 2, 3 Branches


Twigs \rightarrow 4, 5, 6 Branches

Loop 1 \rightarrow Link 1, Twigs 4 & 5

2 \rightarrow Link 2, Twigs 5, 6

3 \rightarrow Link 3, Twigs 6, 4

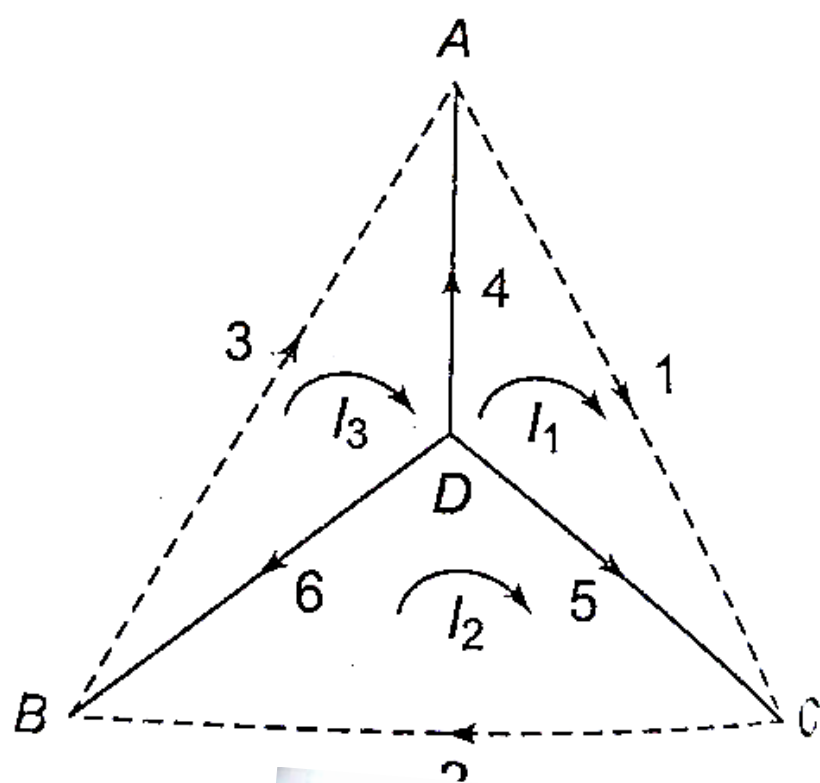The direction of $I_1 \rightarrow$ direction of link 1



Branch Currents

$$J_1 = I_1$$


$$J_2 = I_2$$

$$J_3 = I_3$$

$$J_4 = I_1 - I_2$$

$$J_5 = I_2 - I_1$$


$$J_6 = I_3 - I_2$$

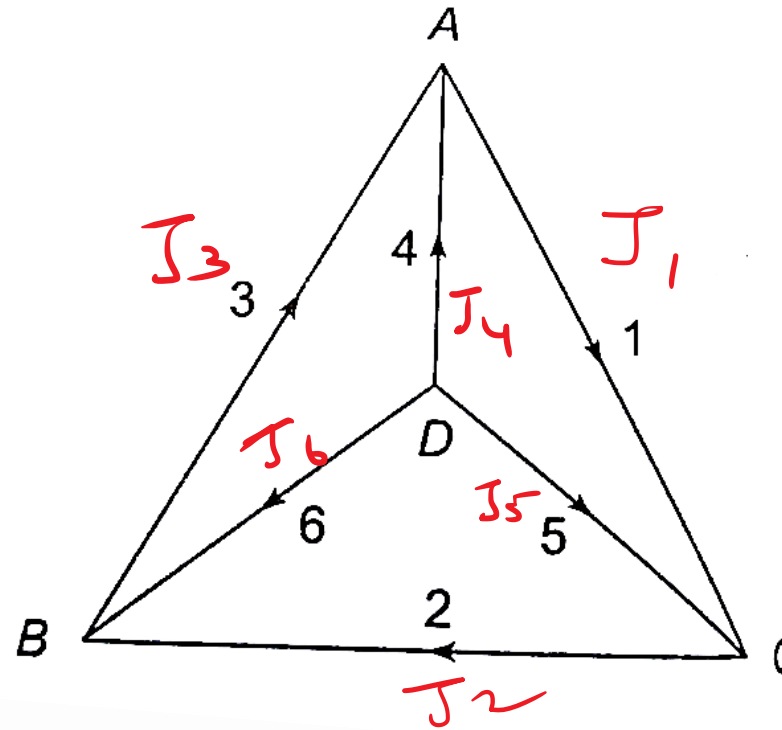

Link No.	Branch No.					
	1	2	3	4	5	6
$I_1(1, 5, 4)$	+1	0	0	+1	-1	0
$I_2(2, 6, 5)$	0	+1	0	0	+1	-1
$I_3(3, 4, 6)$	0	0	+1	-1	0	+1

Add columns

Branch Voltages

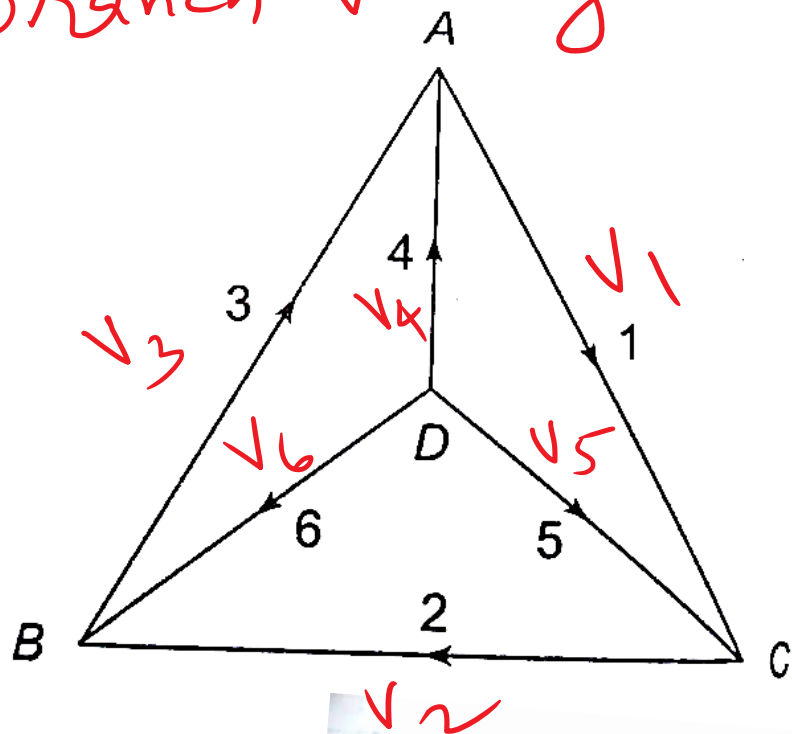

Add rows

$$V_1 + V_4 - V_5 = 0$$

$$V_2 + V_5 - V_6 = 0$$



$$V_3 - V_4 + V_6 = 0$$

Link No.	Branch No.					
	1	2	3	4	5	6
$I_1(1, 5, 4)$	+1	0	0	+1	-1	0
$I_2(2, 6, 1)$	0	+1	0	0	+1	-1
$I_3(3, 4, 5)$	0	0	+1	-1	0	+1

I_1, I_2, \dots, I_6 are the branch currents

Substitute
values of
 I_s & R_s

Link No.	Branch No.					
	1	2	3	4	5	6
$I_1(1, 5, 4)$	+1	0	0	+1	-1	0
$I_2(2, 6, 5)$	0	+1	0	0	+1	-1
$I_3(3, 4, 6)$	0	0	+1	-1	0	+1

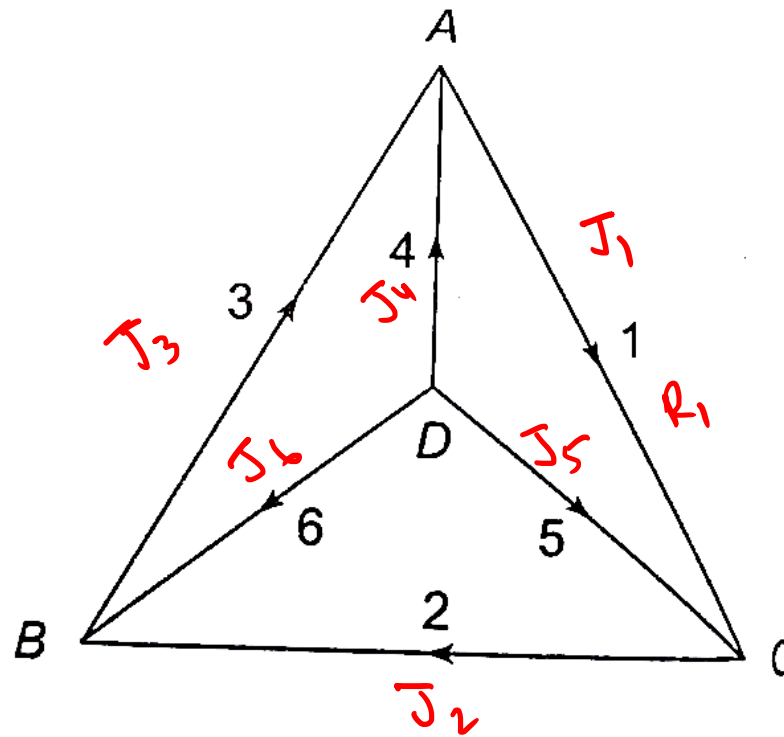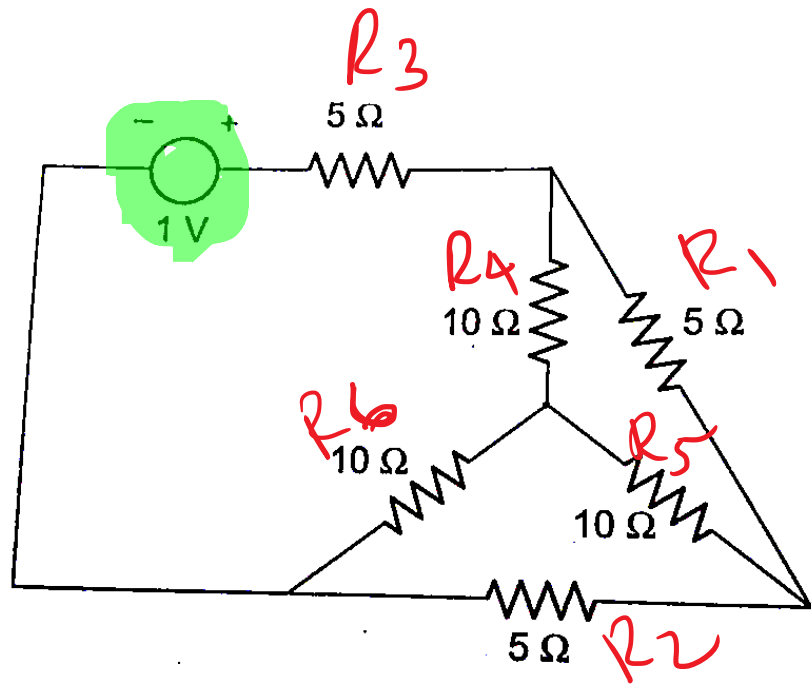

$$V_1 = J_1 R_1 = R_1 I_1 = 5I_1$$

$$V_2 = J_2 R_2 = R_2 I_2 = 5I_2$$

$$V_3 = J_3 R_3 \underline{-1} = 5I_3 - 1$$

$$V_4 = J_4 R_4 = (I_1 - I_3)10$$

$$V_5 = J_5 R_5 = (I_2 - I_1)10$$

$$V_6 = J_6 R_6 = (I_3 - I_2)10$$

$$5I_1 - 10(I_2 - I_1) + 10(I_1 - I_3) = 0$$

$$25I_1 - 10I_2 - 10I_3 = 0$$

$$10(I_2 - I_1) + 5I_2 - 10(I_3 - I_2) = 0$$

$$-10I_1 + 25I_2 - 10I_3 = 0$$

$$(5I_3 - 1) - 10(I_2 - I_3) + 10(I_3 - I_2) = 0$$

$$-10I_1 + 10I_2 - 25I_3 = 1$$


$$\begin{bmatrix} 25 & -10 & -10 \\ -10 & 25 & -10 \\ -10 & -10 & 25 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 1 \end{bmatrix}$$



$$I_1 = \frac{1}{17.5} = 0.057 \text{ A}$$

$$I_2 = \frac{1}{17.5} = 0.057 \text{ A}$$


$$I_3 = \frac{3}{35} = 0.0857 \text{ A}$$

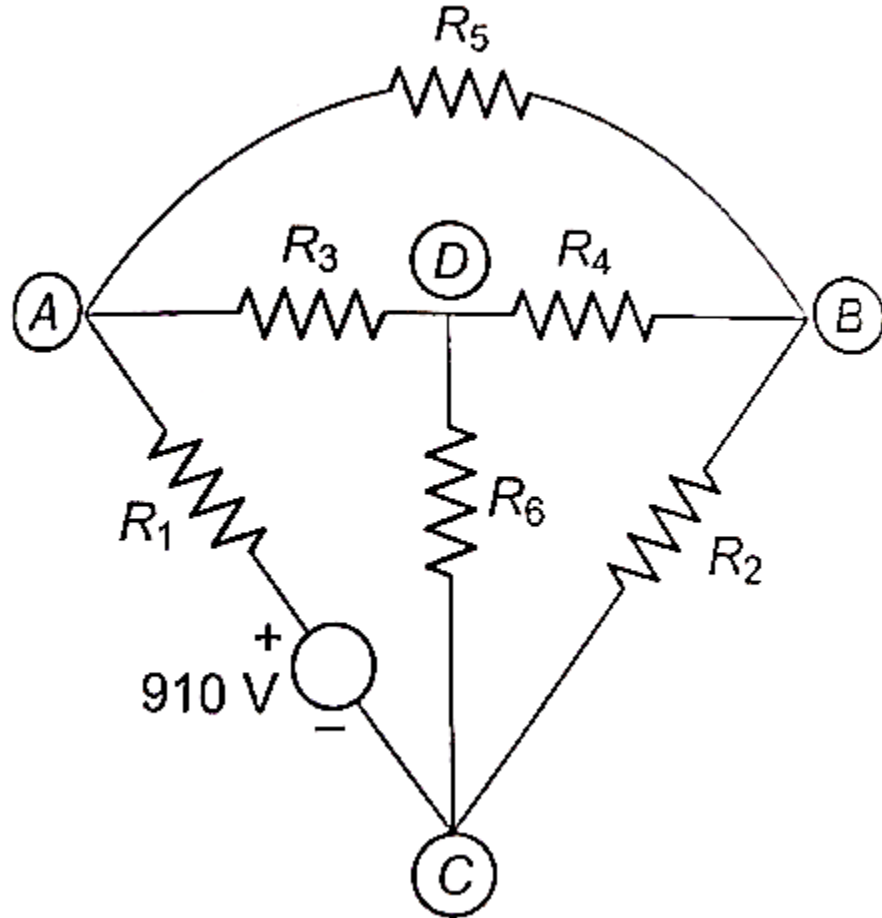Example: Write the cut-set matrix and equilibrium equation on voltage basis. Hence obtain the values of branch voltages and branch currents. Given, $R_1=R_2= 5 \text{ Ohm}$ and $R_3=R_4=R_5= 10 \text{ Ohm}$




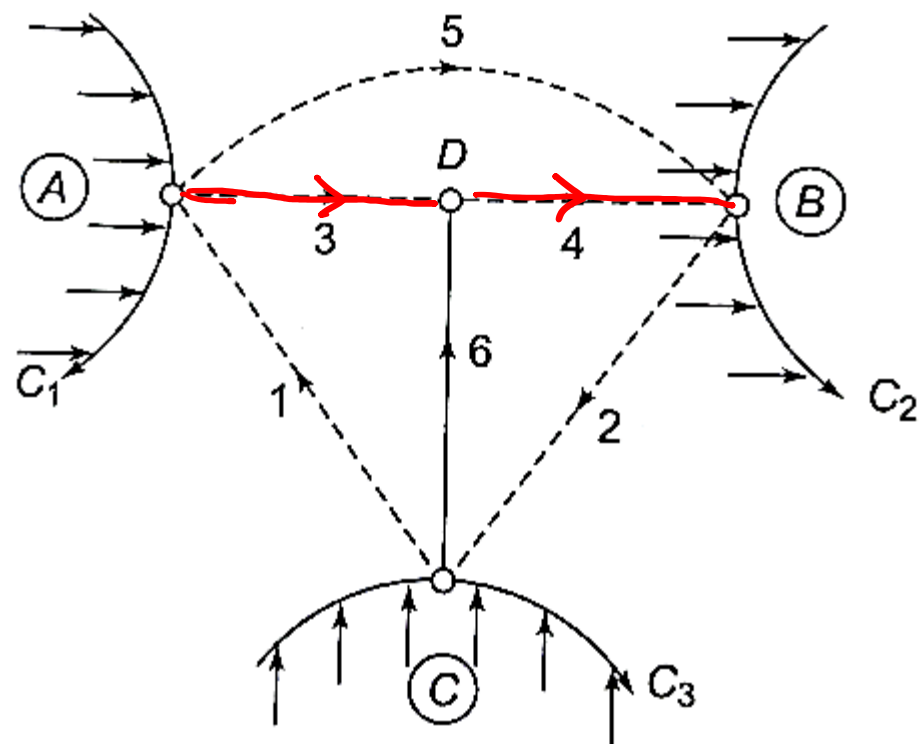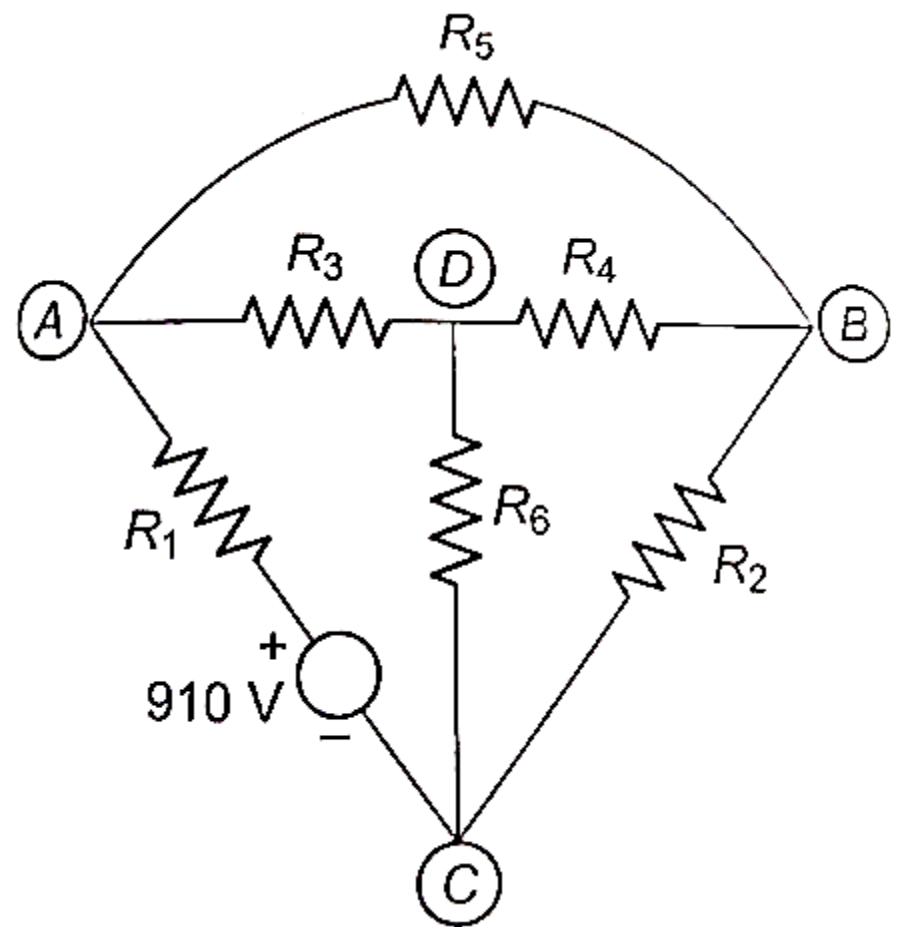

Tree branch	Basic cut-sets
3	1, 3, 5
4	2, 4, 5
6	1, 2, 6

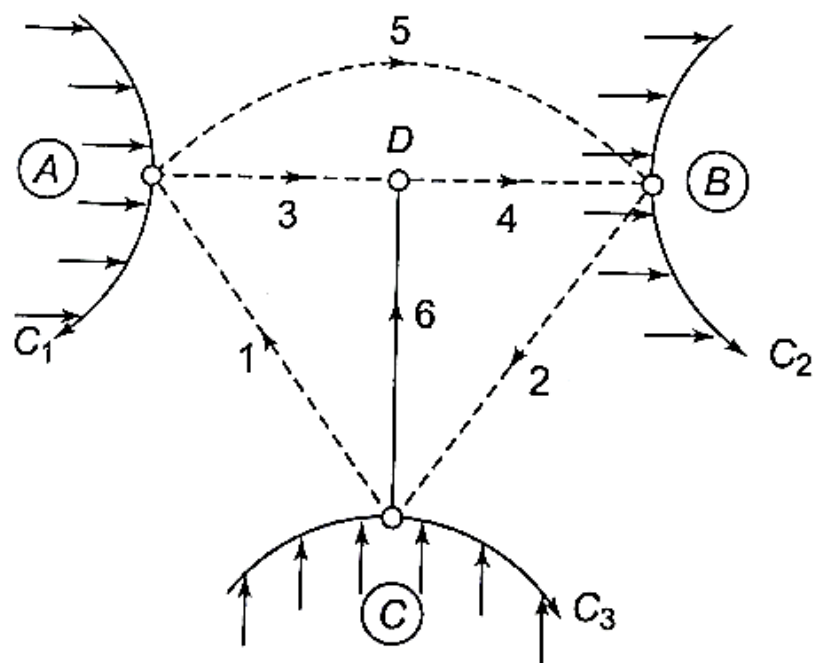

Basic cut-set tree branch	Elements					
	1	2	3	4	5	6
3 (1, 3, 5)	-1	0	+1	0	+1	0
4 (2, 4, 5)	0	-1	0	+1	+1	0
6 (1, 2, 6)	+1	-1	0	0	0	+1

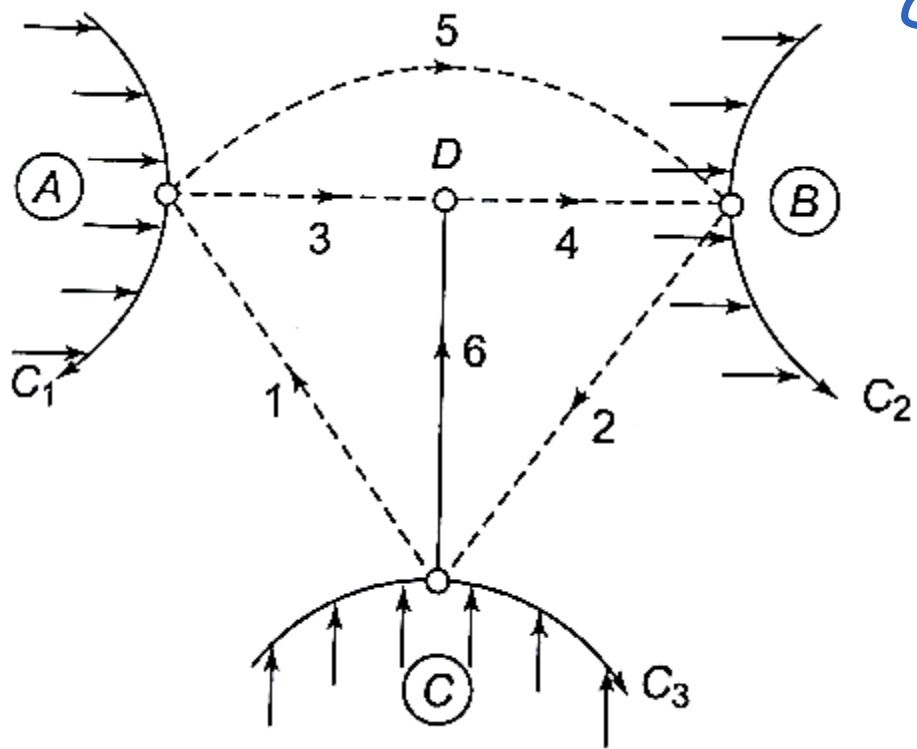

Columns give branch voltages

$$e_1 = e_6 - e_3$$

$$e_2 = -e_4 - e_6$$

$$e_3 = e_3$$

$$e_4 = e_4$$

$$e_5 = e_3 + e_4$$

$$e_6 = e_6$$


rows give nodal Eqs

$$-j_1 + j_3 + j_5 = 0$$

$$-j_2 + j_4 + j_5 = 0$$

$$+j_1 - j_2 + j_6 = 0$$

Basic cut-set tree branch	Elements					
	e_1 1	e_2 2	e_3 3	e_4 4	e_5 5	e_6 6
3 (1, 3, 5) e_3	j_1 -1	j_2 0	j_3 +1	j_4 0	j_5 +1	j_6 0
4 (2, 4, 5) e_4	0	-1	0	+1	+1	0
6 (1, 2, 6) e_6	+1	-1	0	0	0	+1

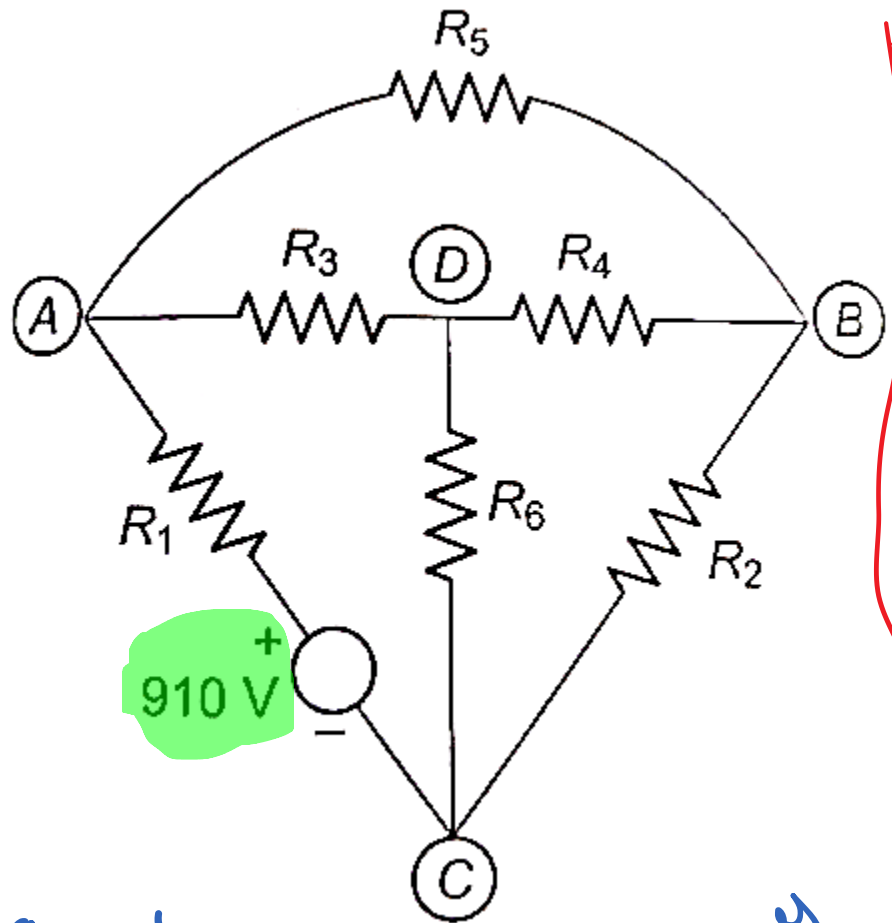

$$e_1 = e_6 - e_3$$

$$e_2 = -e_4 - e_6$$

$$e_3 = e_3$$

$$e_4 = e_4$$

$$e_5 = e_3 + e_4$$

$$e_6 = e_6$$

Branch current (I)
= Branch voltage
Branch resistance

$$j_1 = g_1 (e_1 - 910) = 0.2 (e_6 - e_3 - 910)$$

$$j_2 = g_2 (e_2) = 0.2 (-e_4 - e_6)$$

$$j_3 = g_3 (e_3) = 0.1 e_3$$

$$j_4 = g_4 (e_4) = 0.1 e_4$$

$$j_5 = g_5 (e_5) = 0.5 (e_3 + e_4)$$

$$j_6 = g_6 (e_6) = 0.1 e_6$$

$g_1 = 1/R_1$
 $g_2 = 1/R_2$
 \vdots
 $g_6 = 1/R_3$ } Conductance

Include the
voltage source
in branch 1
to obtain
branch voltages
of the graph

$$\left. \begin{aligned} -j_1 + j_3 + j_5 &= 0 \\ -j_2 + j_4 + j_5 &= 0 \\ +j_1 - j_2 + j_6 &= 0 \end{aligned} \right\}$$

Substitute branch
currents (j_1, j_2, j_3, \dots)
in v. del eqns

Check the steps

$$-0.2(e_6 - e_3 - 910) + 0.1e_3 + 0.5(e_3 + e_4) = 0$$

$$0.8e_3 + 0.5e_4 - 0.2e_6 = -182$$

$$0.2(e_4 + e_6) + 0.1e_4 + 0.5(e_3 + e_4) = 0$$

$$0.5e_3 + 0.8e_4 + 0.2e_6 = 0$$

$$0.2(e_6 - e_3 - 910) + 0.2(e_4 + e_6) + 0.1e_6 = 0$$

$$-0.2e_3 + 0.2e_4 + 0.5e_6 = 182$$

$$\begin{bmatrix} 0.8 & 0.5 & -0.2 \\ 0.5 & 0.8 & 0.2 \\ -0.2 & 0.2 & 0.5 \end{bmatrix} \begin{bmatrix} e_3 \\ e_4 \\ e_6 \end{bmatrix} = \begin{bmatrix} -182 \\ 0 \\ 182 \end{bmatrix}$$

Use Cramer's rule

Solving above matrix for e_3 , e_4 , and e_6 :

$$e_3 = -200 \text{ V}, e_4 = 60 \text{ V}, e_6 = 260 \text{ V}$$

The branch voltages and branch currents are:

$$e_1 = e_6 - e_3 = 460 \text{ V}$$

$$e_2 = -e_4 - e_6 = -320 \text{ V}$$

$$e_3 = e_3 = -200 \text{ V}$$

$$e_4 = 60 \text{ V}$$

$$e_5 = e_3 + e_4 = -140 \text{ V}$$

$$e_6 = 260 \text{ V}$$

*Solve for
branch voltages*

Solve for branch currents

Branch currents are:

$$j_1 = 0.2 (460 - 910) = -90 \text{ A}$$

$$j_2 = 0.2 (-320) = -64 \text{ A}$$

$$j_3 = 0.1 (-200) = -20 \text{ A}$$

$$j_4 = 0.1 (60) = 6 \text{ A}$$

$$j_5 = 0.5 (-140) = -70 \text{ A}$$

$$j_6 = 0.1 (260) = 26 \text{ A}$$