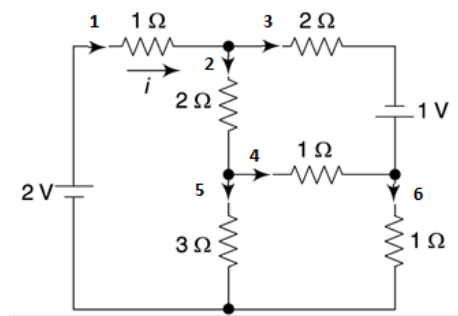


Assignment 2 (Due date: Monday, 31/09/22)


Submission mode: Hard copy with your name and reg no (cabin no #7, 607A Annexure)

1. For the given circuit in Figure, find the following.


- (a) Network graph of the circuit.
- (b) Incidence and reduced incidence matrix
- (c) How many trees are possible
- (d) Tie-set & cut-set matrix with branches 2,4,5 as twigs
- (e) Current flowing through 1Ω resistor and voltage across 3Ω resistor using both tie-set and cut-set equilibrium equations



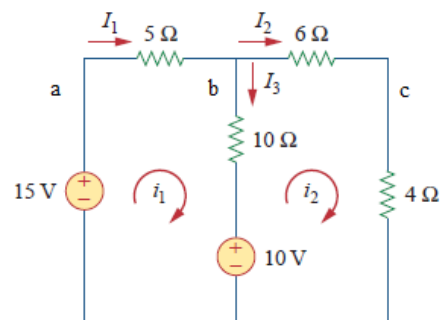2. For the circuit shown in Fig. 3 find the branch currents I_1 , I_2 and I_3 using Tie set matrix.



(B) Previously given questions

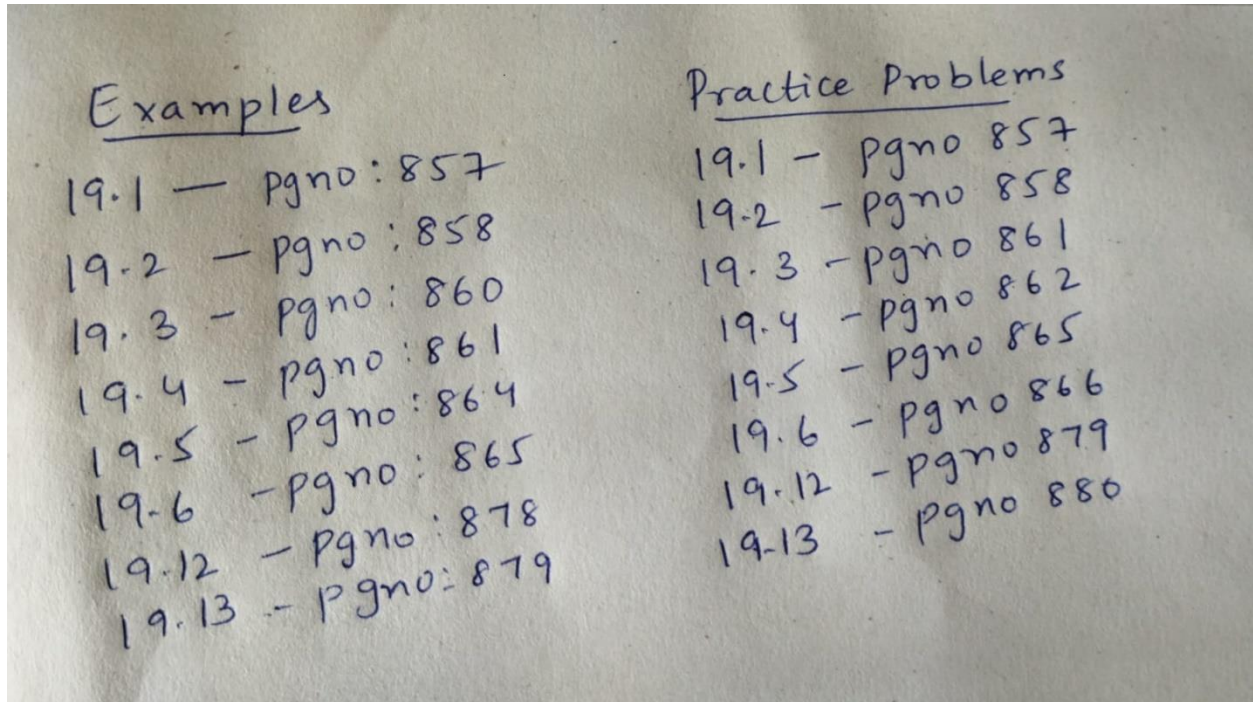

(Ref material: Fundamentals of Electric circuits by Charles K. Alexander and Matthew N.O. Sadiku)

(C) Use the attached tutorial sheets and do at least 5 problems from it

- Odd Number registration numbers attempt the odd numbered problems
- Even Number registration numbers attempt the even numbered problems